

EE671: VLSI DESIGN

SPRING 2024/25


LAXMEESHA SOMAPPA
DEPARTMENT OF ELECTRICAL ENGINEERING
IIT BOMBAY
laxmeesha@ee.iitb.ac.in



LECTURE – 34

SRAM CONTINUED

SRAM: FULL PICTURE

 


- ❑ We have looked at the Row decoder (logical effort design)
- ❑ Looked at design of individual bit-cell
- ❑ Next, we will look at the pre-charge circuit, column decoders, sense amplifiers



COLUMN PULL-UPS: PRE-CHARGE

 - ❑ To remove all history → perform pre-charge before every read and write
- ❑ The nature of pre-charge (PC) circuit depends on the amplification (also called sense amplifier (SA)) topology



Suitable for voltage based amplifiers


❑ Sequence:

- ❑ PC is low by default (Pre-charging bit lines)
- ❑ PC goes high
- ❑ After some finite time → WL goes high
- ❑ Read operation starts
- ❑ Bitlines start developing delta voltage
- ❑ Sense amplifier (SA) enabled after finite time to amplify this delta voltage
- ❑ Once logic levels are obtained at the output, disable WL, SA and enable PC




COLUMN DECODER (COLUMN MUX)

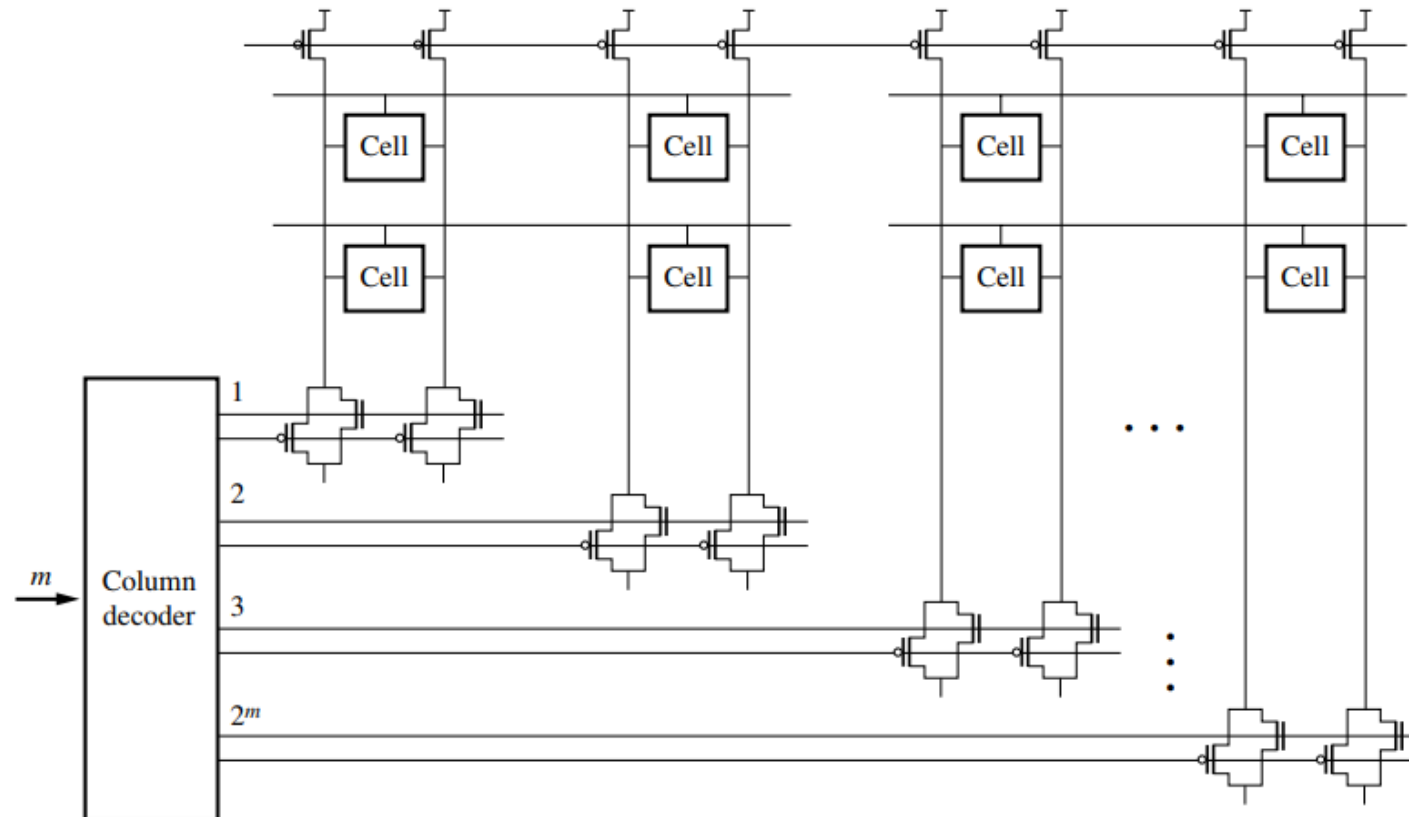- ❑ After PC, the columns involved in read/write are to be enabled using MUX
- ❑ Usually this MUX is a simple TG (we looked at implementing MUX using TG earlier)





COLUMN DECODER (COLUMN MUX)

 - ❑ The read and write operation paths can be separated as shown below
- ❑ SA is enabled during read and write driver is enabled are enabled during write after selecting the required columns





COLUMN DECODER (COLUMN MUX)

 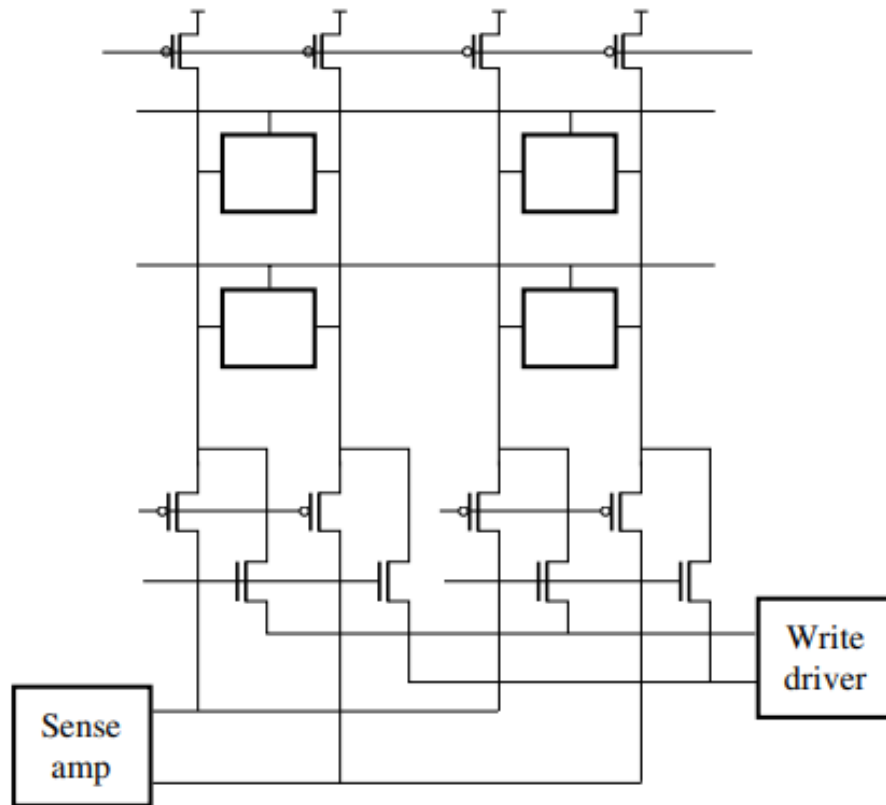- Note that, during read all lines are V_{DD} (pre-charge), so we only really need PMOS devices during read operation
- During write, essentially, we are discharging bitlines to ground \rightarrow we need NMOS
- This automatically provides the enabling of read/write using the same column decoder




COMPLETE READ CIRCUIT (ONE COLUMN)

  Read column mux (PMOS only implementation)






COMPLETE WRITE CIRCUIT (ONE COLUMN)

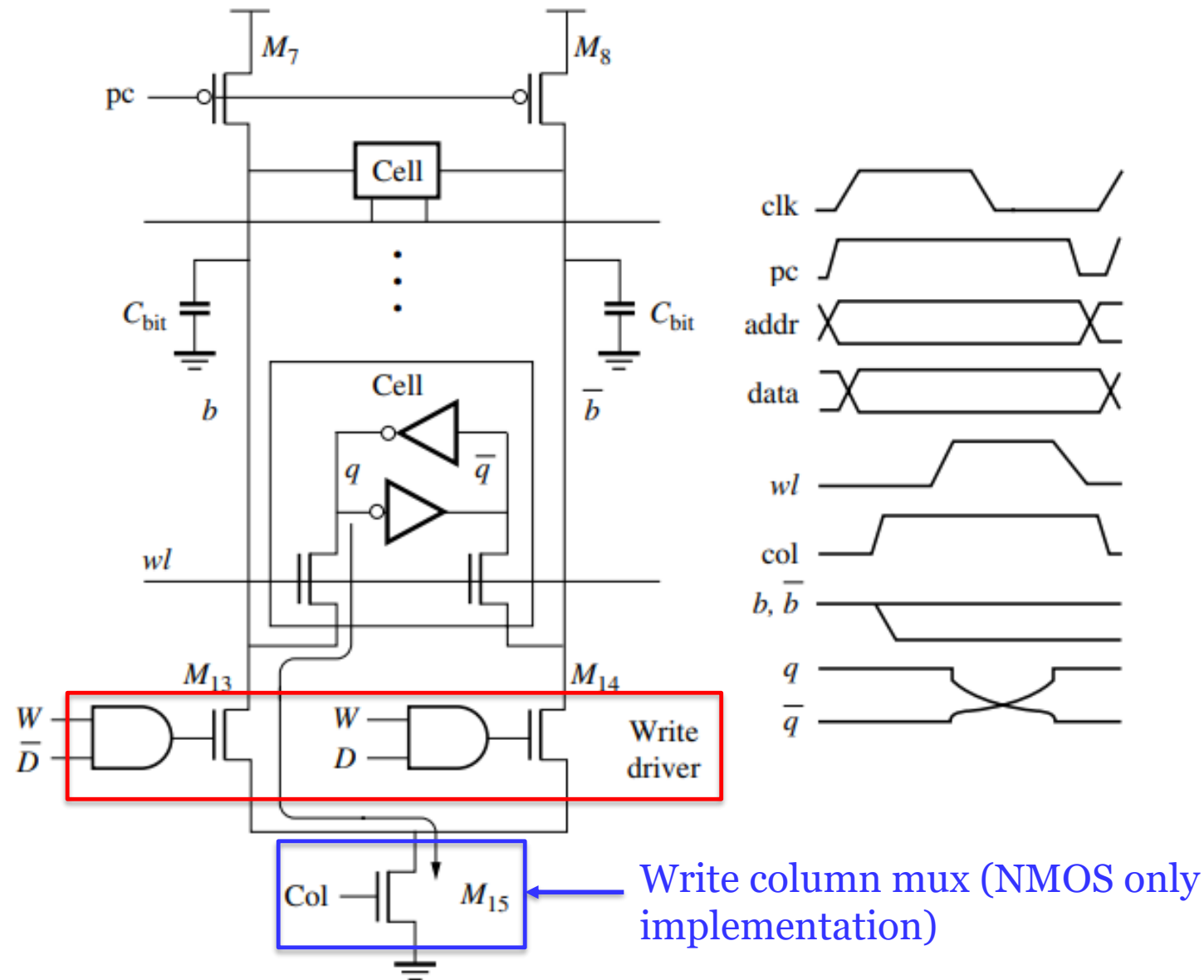



SENSE AMPLIFIER

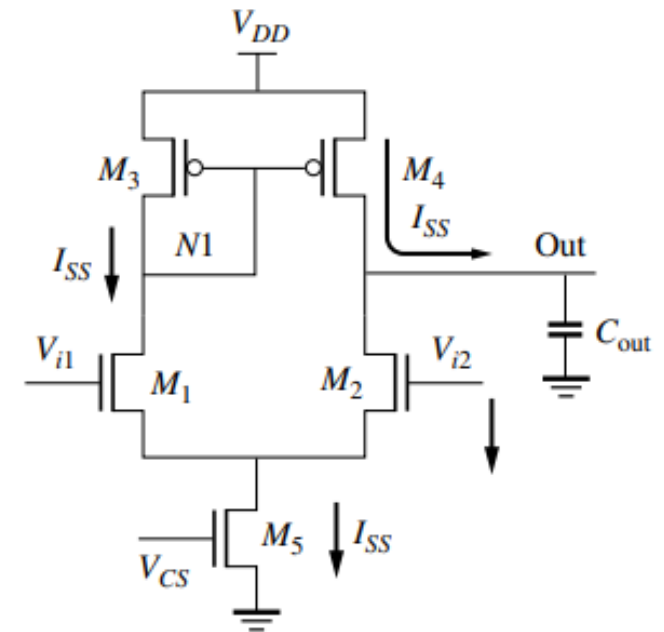  - ❑ Option-1: A simple differential amplifier
 - ❑ Provides good common-mode rejection (common-mode noise)
 - ❑ Typical: 100 mV to 200 mV input voltage required
 - ❑ Static power consumption!





SENSE AMPLIFIER

 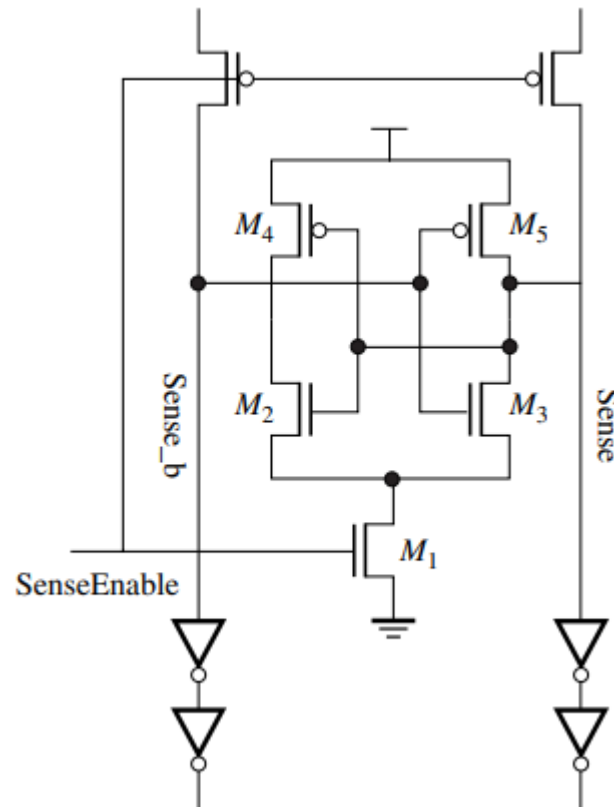- ❑ Option-2: Latch based amplifier (positive-feedback)
 - ❑ Cross-coupled inverter
 - ❑ Inverters reset to VDD in off state (switches not shown in diagram below)
 - ❑ Also used as comparators in ADCs



SENSE AMPLIFIER

 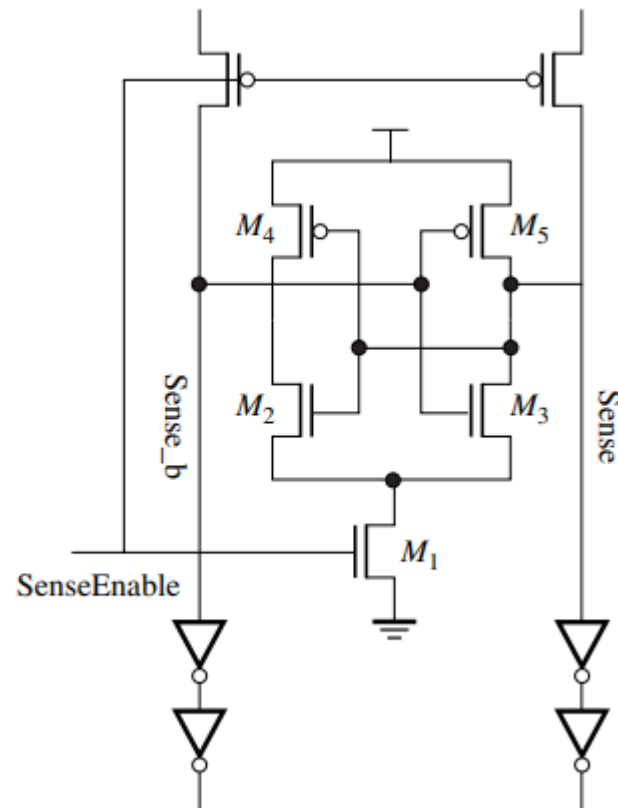- ❑ Option-2: Latch based amplifier (positive-feedback)
 - ❑ Critical that SenseEnable is fired at the right moment
 - ❑ If SenseEnable fired early: The latch will flip in a different direction due to noise
 - ❑ If SenseEnable fired late: unnecessary read delay (slower memory)




SENSE AMPLIFIER

- ❑ Option-2: Latch based amplifier (positive-feedback)
 - ❑ Critical that SenseEnable is fired at the right moment
 - ❑ The fabrication process corner (Transistors faster or slower post fabrication) – recall our discussion on the Process-Voltage-Temperature (PVT) corners in .lib
 - ❑ All signals associated with read must internally track the change in process !!
 - ❑ i.e., say the MOSFETs are slower post fabrication → row decoder circuits are slower than expected → WL is fired later than expected → the sense amplifier input might not have enough to amplify → sense amplifier enable must also be delayed
 - ❑ Similar effects can take place if the individual bit cell itself is slower or faster!
 - ❑ Therefore, while generating all control signals (WL, SenseEnable, etc.), we must design a process **dependant** circuit



REPLICA DECODER

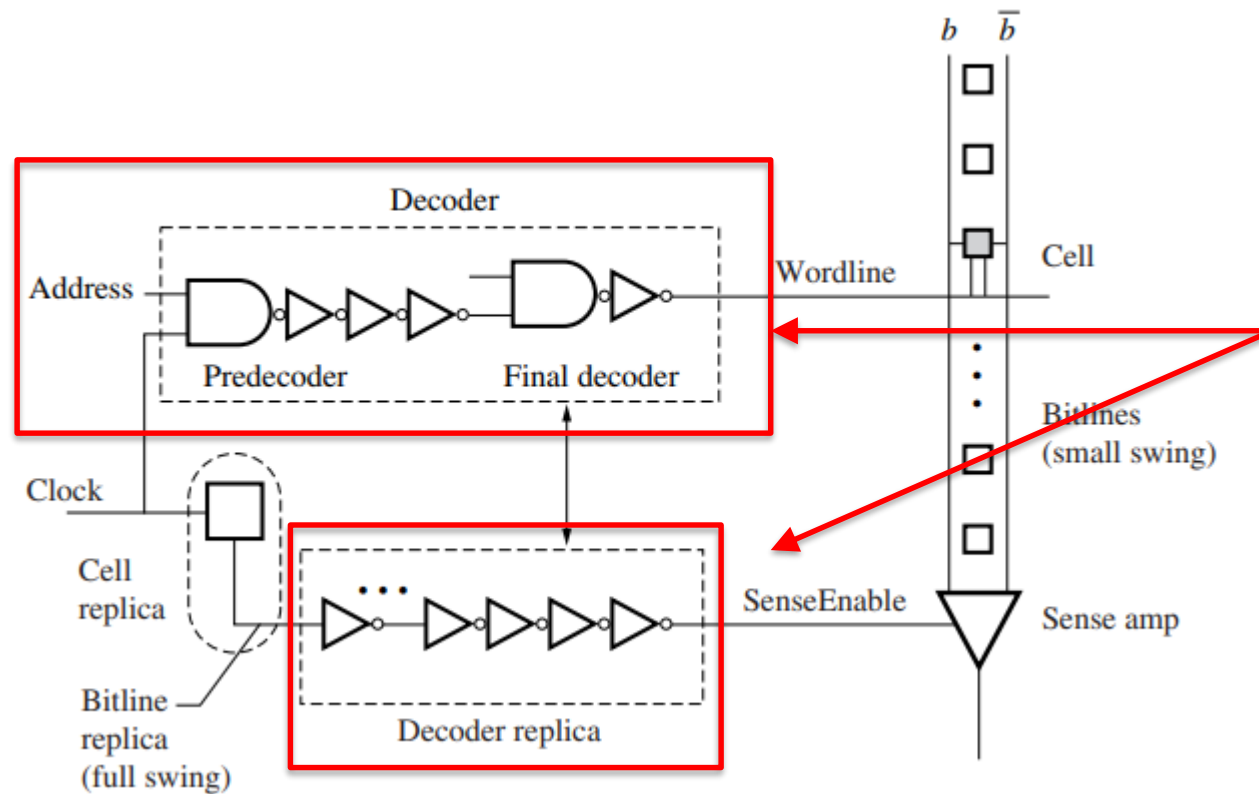- ❑ Process variation handled through a replica decoder circuit
 - ❑ A replica of one path in the address decoder




-
- The diagram illustrates the internal structure of a 1T1R1C1 SRAM array. It shows a wordline decoder and its replica. The decoder consists of a predecoder and a final decoder. The predecoder takes an address and produces a wordline signal. The final decoder takes the wordline signal and produces a sense enable signal. The replica consists of a cell replica and a decoder replica. The cell replica is connected to the wordline and a bitline replica (full swing). The decoder replica is connected to the sense enable signal and the bitline replica. The bitline replica is connected to the bitline (small swing). The bitline is connected to the sense amp. The sense amp is connected to the bitline and the sense enable signal. The sense amp output is connected to the bitline. The sense amp is connected to the bitline and the sense enable signal. The sense amp output is connected to the bitline.

□ However, note that the replica of the bit-cell has to swing to logic levels but actual bit-cells only have to swing 100 mV ~ 200 mV depending on the SenseAmp → how to match timing in this case?


REPLICA BIT-CELL

 - Process variation handled through a replica decoder circuit
 - Typically a redundant bit-cell column is placed in the array (left and right side of the layout) to account for edge effects in the fabrication




REPLICA BIT-CELL

 - Process variation handled through a replica decoder circuit
 - Replica bit-line has to swing to logic levels but actual bit-cells only have to swing 100 mV ~ 200 mV depending on the SenseAmp → Cut the replica bitline (example below 26 cells) to produce logic levels with the same ΔT required for the main bitline to produce ΔV




SRAM: FULL PICTURE

 

- ❑ Row Decoder: WL firing
- ❑ Col Decoder: Column Mux enable (Col)
- ❑ Precharge: to precharge bit-lines (PC)
- ❑ Sense Amplifiers: to read logic levels from bit lines (in a small time ΔT)
- ❑ Internally, need to generate SenseEnable signals (using replica)



SRAM: FULL PICTURE

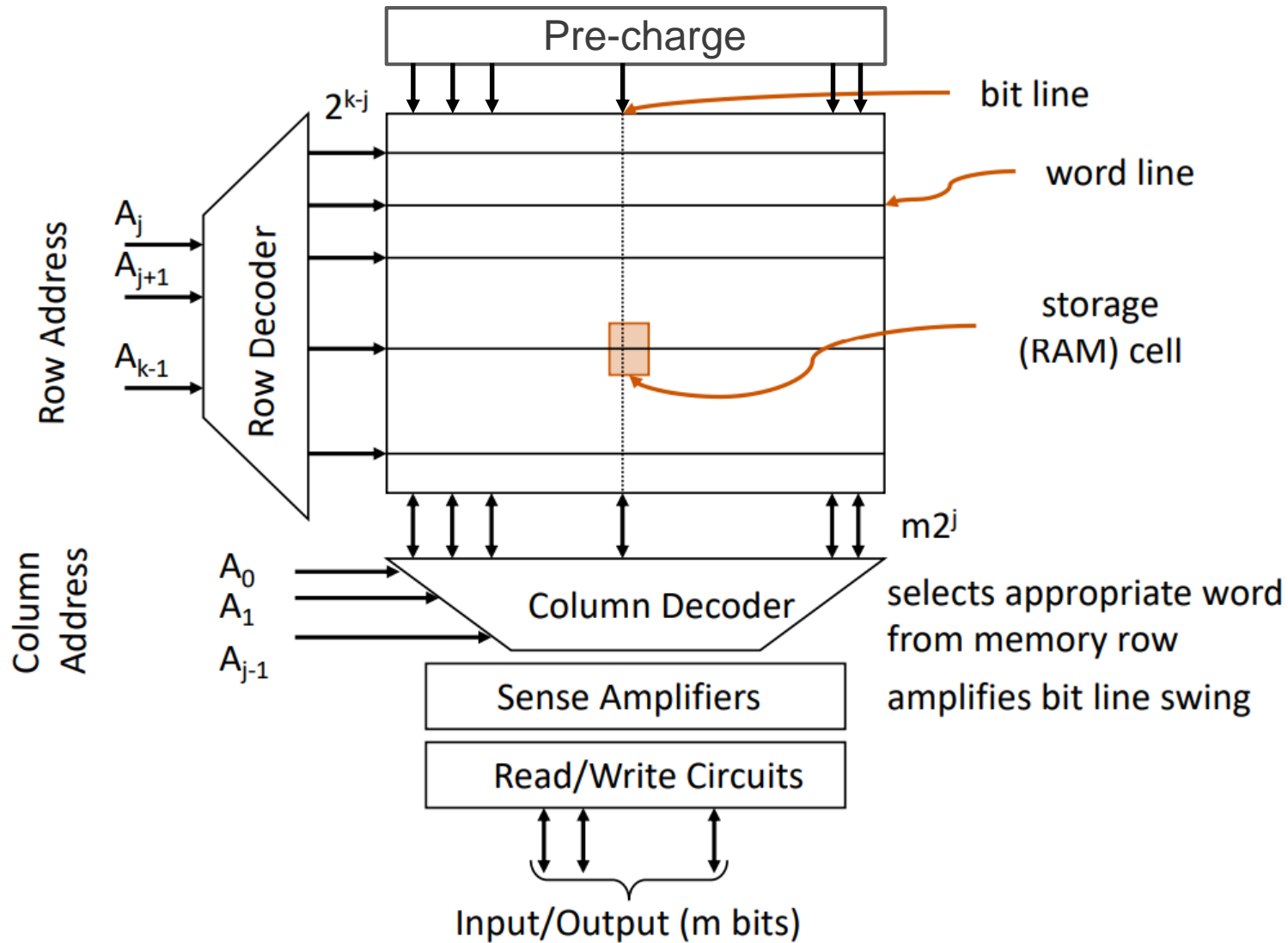


Write:

- Apply address and Data to be written into registers
- Address decoder → WL and Col fires
- Appropriate BL and BLb are tied to VDD/GND
- Write ensured due to bit-cell sizing
- Disable WL, COL signals → operation done




SRAM: FULL PICTURE

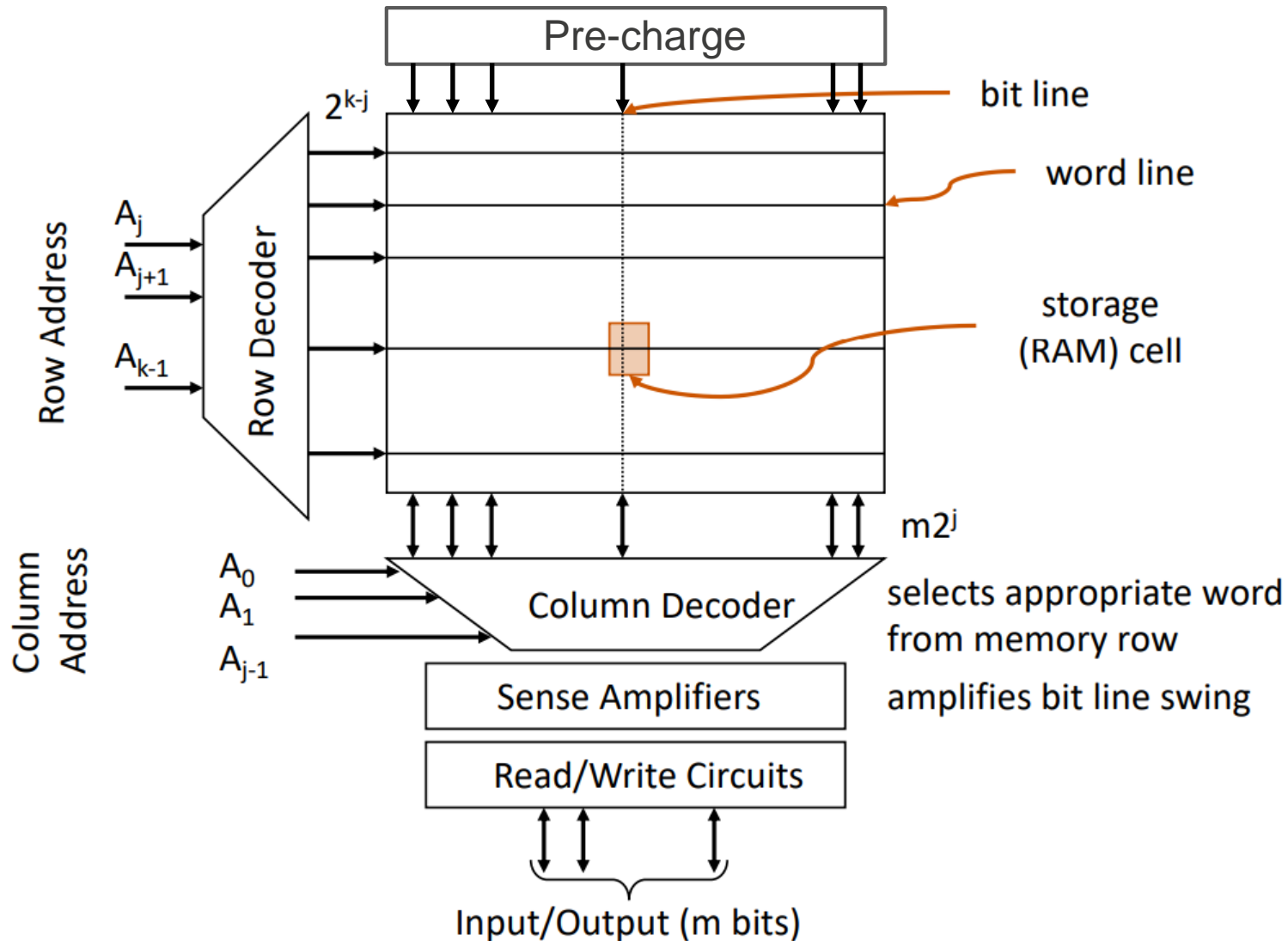

- ❑ **Read:**
- ❑ Pre-charge all BL & BLb
- ❑ Apply address
- ❑ Address decoder \rightarrow WL fires
- ❑ Corresponding BL and BLb start generating ΔV in ΔT
- ❑ COL mux and SenseEnable fires
- ❑ SenseAmplifier amplifies and puts data into output register
- ❑ Remove all signals \rightarrow operation done



EXAMPLE TYPICAL SRAM: FULL PICTURE

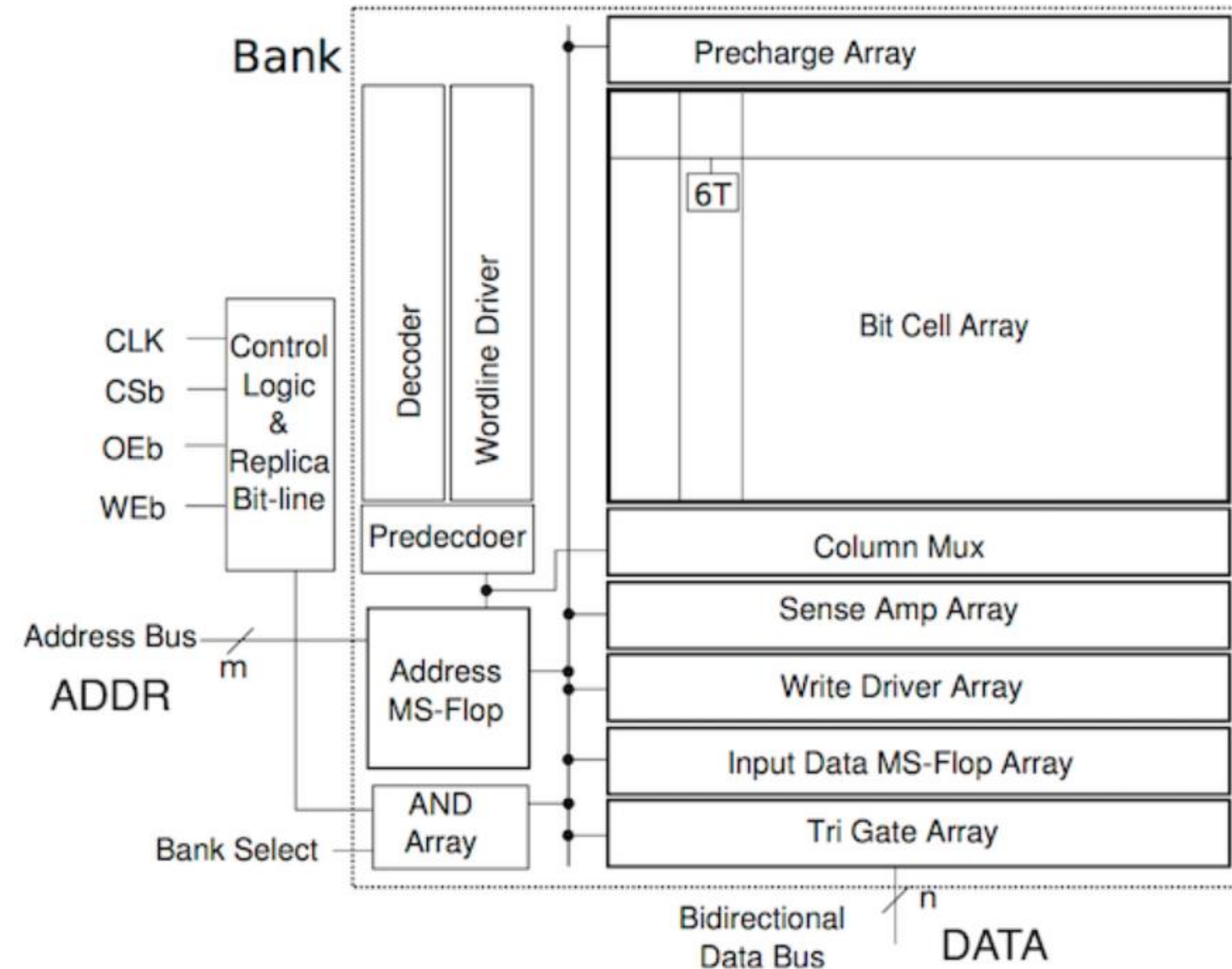

- CLK
- CSb: Chip Select (active-low)
- OEb: Output Enable (active-low)
- WEb: Write Enable (active-low)
- ADDR: input bus
- DATA: In/Out bus



EXAMPLE TYPICAL SRAM: LAYOUT

