
 

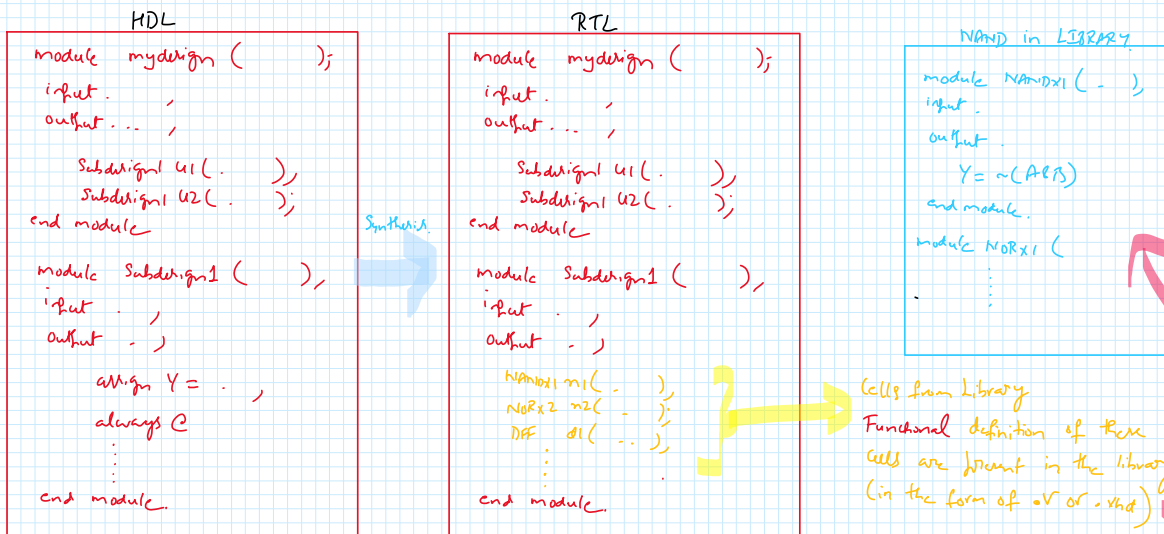
## Lecture - 8 -

- Review
- I'll now looked at NMOS, PMOS characteristics (plots and equations)
  - Built a CMOS inverter, analysed and characterized (static & dynamic) using simulations, equations and intuition.
  - with INVx1, other logic gates like NANDx1, NORx1, NANDx2, etc. can be designed.
  - Given any new "device" (other than an NMOS or PMOS), the same set of steps can be used to design, analyse and characterize logic gates in a given technology



Eg



∴ Library [also called standard cell library] will contain functional definition (.v or .vhd) of all the logic gates (also called standard cells)


↳ The .v/.vhd views of the standard cells provide functional definition for simulation at the higher abstraction level (compared to MOSFET level simulation).


- ↳ This enables faster debugging (we don't have to fix bugs at the MOSFET level ~10 billion MOSFETS)
- ↳ This enables faster simulation (MOSFET level spice simulation for billion gates is VERY VERY VERY VERY VERY... VERY SLOW)

\* However, remember that for final fabrication, we need the physical MOSFET and interconnect geometries. This detail is incorporated in the spice netlist and layout.

\* The transformation from RTL to physical geometry is performed by the "Physical Design" tool. The tool needs access to individual spice netlist & layout of the logic gates (standard cells).

Eg.

 

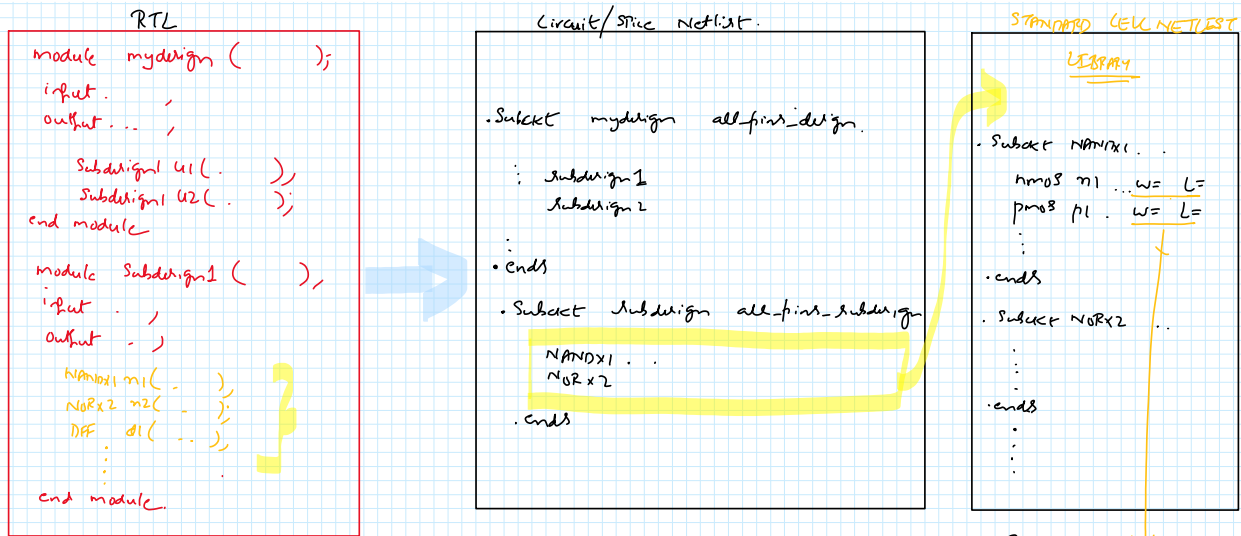

\* We also need physical layout of the circuit defined in the netlist for fabrication. This layout is saved in .gdsII format

∴ In a "Standard Cell Library", we need to have atleast the following "views" of the standard cells (logic cells)

.v or .vhd      .cir/.spc/.sp/.cal      .gdsII


\* .v/.vhd can be easily written and verified


\* Assignment - I covers the creation of spice netlist for logic cells.

\* We will now discuss the creation of the layout


\* Layout is done using the top-view of the chip since the design parameters W & L are better observed from the top-view than the side view

Top-view of a MOSFET.

 


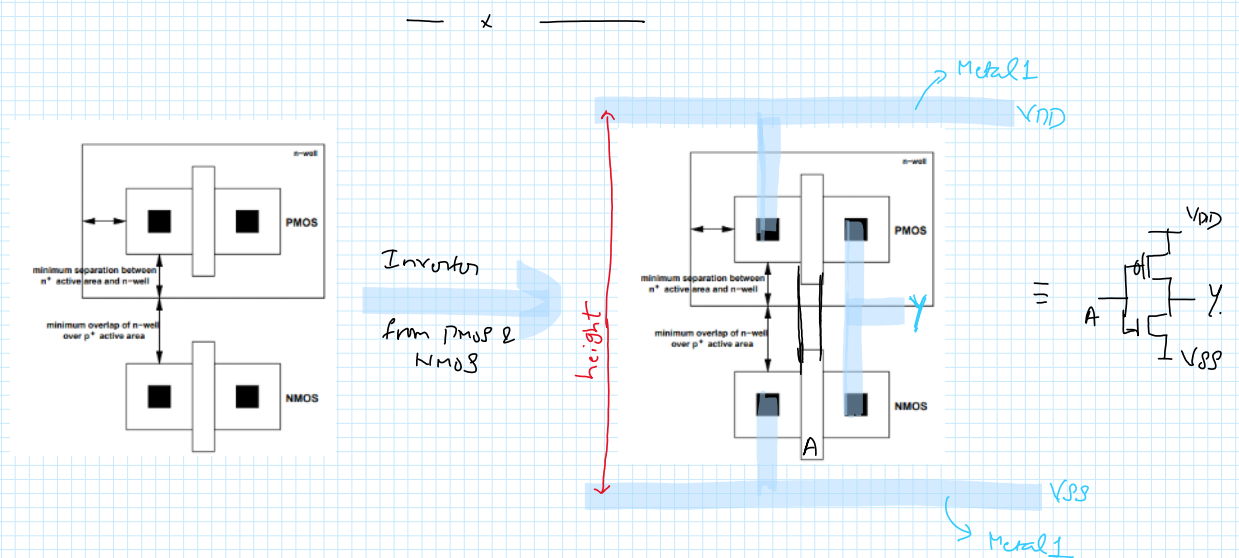

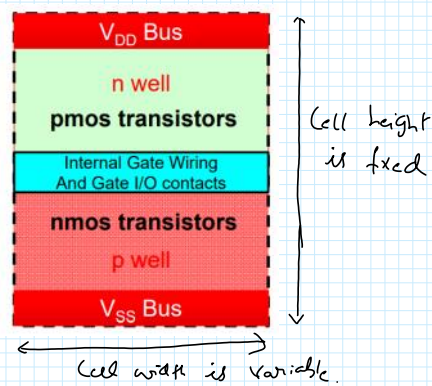\* The height of a standard cell is fixed for a given technology (optimized). The height must be fixed to allow the physical design tool to make connections between cells and converge in a faster way.



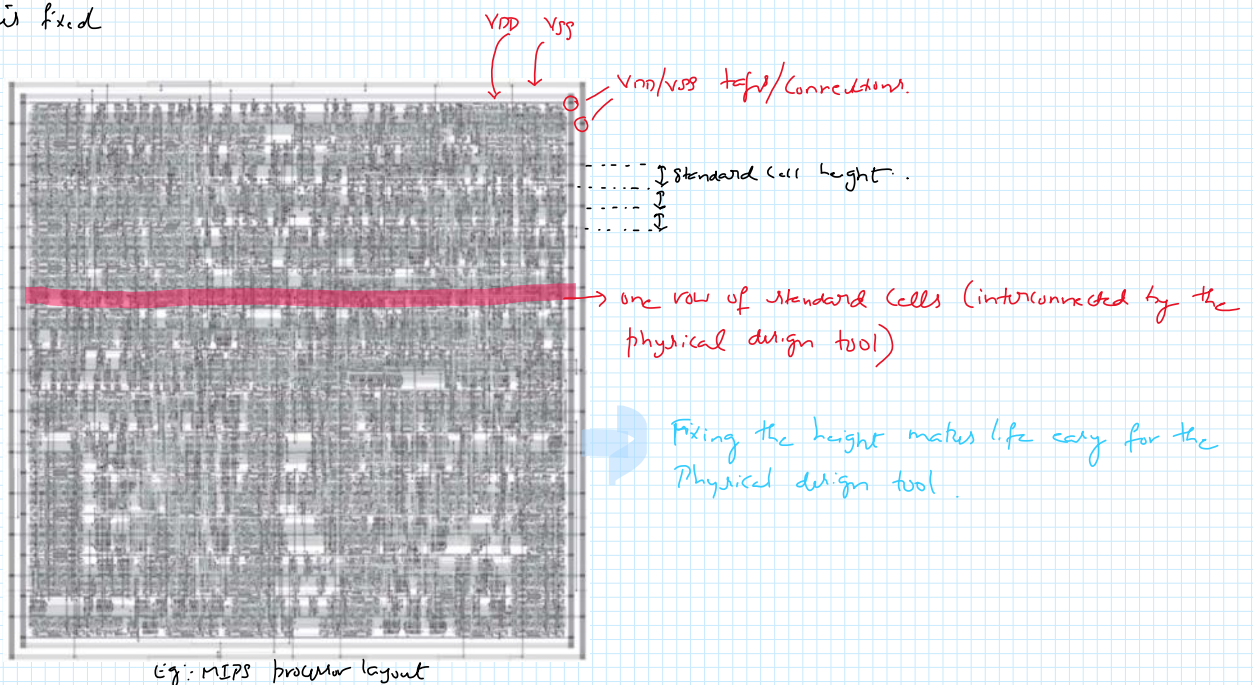i.e. the cell height of all cells/gates (eg- NAND2, NOR2, INV2, DFF, 3-i/p gate, 4-i/p gate) etc is fixed.



eg: MIPS processor layout


\* Before drawing a standard cell on a software, it is usually visualized on pen & paper.

\* Before drawing standard cell on a software, it is usually visualized on pen & paper using "STICK DIAGRAM".


Consider the following colour coding:

- Metal 1
- P diffusion
- N diffusion
- Poly silicon
- x Contact


(a) Inverter

 

(b) 2-i/p NAND

 

(c) 2 i/p NOR

 

d) h-i/p NAND & h-i/p NOR :- try it by yourself