 


Lecture-6


* Re-evaluate Noise Margin

* In the class, we discussed NM_H & NM_L as

$$NM_H = V_{DD} - V_{IH} \quad \& \quad NM_L = V_{IL} - 0 \quad \text{considering a single inverter.}$$



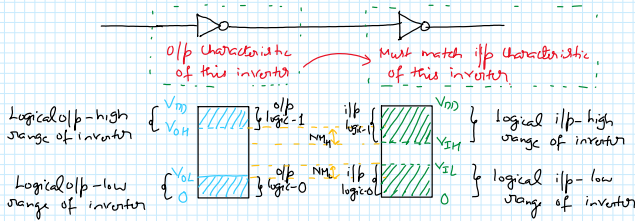* But practically, each inverter drives another inverter (or other logic)



* The next stage inverter will consider any voltage below V_{IL} @ its input as logic-low & will consider any voltage above V_{IH} @ its input as logic-high.

* The previous stage can o/p any voltage between V_{DD} & V_{OH} as output-high (depending on its i/p) & it can o/p any voltage between 0 & V_{OL} as output-low (depending on its i/p)

* When the previous stage outputs V_{OH} as o/p (it is still a valid logic-high voltage), the amount of margin we have for the noise is reduced (i.e. an addition of noise can make the i/p to the next inverter below V_{IH} or $(V_{OH} - \text{Noise}) < V_{IH}$, leading to wrong o/p).

∴ The worst case Noise margins are:

$$NM_H = V_{OH} - V_{IH}$$

$$\& \quad NM_L = V_{IL} - V_{OL}$$


But Gate:-

$$NM_H = V_{DD} - V_{IH}$$

$$NM_L = V_{IL} - 0$$

Capacitance of MOSFET:

a) Due to channel:-

 

* When the MOSFET is ON (linear or saturation), there exists a capacitance between gate & source (C_{GS})


i.e. top-plate of cap → Gate Metal
dielectric → Gate oxide

& bottom-plate of cap → Channel Connected to source



* When the MOSFET is in linear region, there also exists a capacitance b/t gate & drain (C_{GD})


(Remember, in saturation, the channel does not extend to the drain because of depletion, hence no capacitance b/t gate & drain)

∴ Effectively -

 

b) Due to junctions (P-N):-

  

 

* There is a P-N junction on the bottom side of the source (and corresponding top surface of substrate)

If C_j is the junction cap/unit-area, $C_{bottom} = C_j \times W \times L_s$

* There are P-N junctions on three sides of the source (except for the fourth side towards the Gate)

The depth x_j is fixed for a given process. If C_{sw} is the side-wall cap/unit area,

If C_{jsw} is the side-wall capacitance,

$$C_{jsw} = C_{sw} \times \left[\underbrace{(x_j \times L_s)}_{\text{Sidewall 1 area}} + \underbrace{(x_j \times L_s)}_{\text{Sidewall 2 area}} + \underbrace{(x_j \times W)}_{\text{Sidewall 3 area}} \right]$$

$$= \underbrace{C_{sw} x_j}_{C_{jsw}} [2L_s + W]$$

Depends on the technology

$$C_{jsw} = C_{jsw} [2L_s + W]$$

- Capacitance due to junctions, also called diffusion capacitance is

$$C_{diff} = C_{bottom} + C_{jsw}$$

$$= C_j \times \text{AREA} + C_{jsw} \times \text{PERIMETER}$$

$$C_{diff} = C_j L_s W + C_{jsw} [2L_s + W]$$


* Look out for "as, ad, ps, pd" spice parameters in your assignment-1

Power Consumption -

Three main factors contribute for power.


(a) Dynamic power consumption (P_{dyn}) :-

* Consider the inverter circuit :-

 

 a) when $IN = \text{Logic-0}$, PMOS \rightarrow ON & NMOS OFF.
Acting like switches

Any 'ON' switch has a finite resistance & the equivalent model.



The energy supplied by the source is computed by integrating source power

$$E_{\text{source}} = \int_0^{\infty} V_{DD} \cdot I(t) dt$$

For a switching RC circuit, $I(t) = \frac{V_{DD}}{R} [e^{-t/\tau}]$

[Assuming zero charge on C initially]
i.e. cap was discharged previously

$$\therefore E_{\text{source}} = V_{DD} \cdot \frac{V_{DD}}{R} \int_0^{\infty} (e^{-t/\tau}) dt$$

(c.c. cap was discharged previously)


$$\begin{aligned} \therefore E_{\text{switch}} &= V_{DD} \cdot \frac{V_{DD}}{R} \int_0^{\infty} (e^{-t/\tau_{RC}}) dt \\ &= \frac{V_{DD}^2}{R} \left[-\tau_{RC} e^{-t/\tau_{RC}} \right]_0^{\infty} = \boxed{V_{DD}^2 C} \end{aligned}$$

Energy from source

The energy stored on a capacitor is $\boxed{\frac{1}{2}CV^2}$ $\Rightarrow \frac{1}{2}CV^2$ is lost on the resistor (dissipated as heat)

Energy on cap

 * Now consider the case when input is logic high and the cap was previously charged to V_{DD} by the PMOS switch. The equivalent model is:-



At the end of this, the total charge on the capacitor is zero (i.e. V_0 is 0, & the cap is fully discharged, i.e. logic-low output)

Since all the charges on the capacitor are lost, the energy of cap ($\frac{1}{2}CV^2$) must be dissipated on the resistor.

$\therefore \frac{1}{2}CV^2$ is lost on the switch, this time on the NMOS side!!
(dissipated as heat)

* At the end of the operation, a total of CV^2 ($\frac{1}{2}CV^2$ on PMOS side & $\frac{1}{2}CV^2$ on NMOS) energy is lost/dissipated in the circuit [this energy is provided by the supply V_{DD}]



\therefore Energy dissipation $\propto CV^2$

$$\text{Power} = \frac{\text{Energy}}{\text{Time}}$$

* Assuming that the NMOS & PMOS (in our circuit above) are periodically switching with period T (or frequency f),



$$\therefore P_{\text{dyn}} = \frac{CV_{DD}^2}{T} = CV_{DD}^2 f$$

 
 
(b) Power due to short-circuit path (P_{SC}):-




$$\begin{aligned} P_{SC} &= V_{DD} I_{SC, \text{avg}} = V_{DD} \left[\frac{\frac{1}{2} \times t_{sc} \times I_{SC, \text{peak}} + \frac{1}{2} t_{sc} \times I_{SC, \text{peak}}}{T} \right] \rightarrow \text{assuming current profile is perfect triangle (Area} = \frac{1}{2} \times b \times h) \\ &= \frac{V_{DD} I_{SC, \text{peak}} t_{sc} f}{2} \end{aligned}$$

  (c) Static power consumption (P_{stat}) (due to leakage current) \therefore



  

 (Source-drain diode will have zero potential & it is 'ignored')



$$P_{stat} = V_{DD} \times I_{stat}$$


Total Power Consumption,

$$P_{tot} = P_{dyn} + P_{sc} + P_{static}$$

Note on the short-circuit current :-


For a given input transition consider two cases.

(a) Very small capacitance :-

 

* This case, the PMOS will be in saturation majority of the transition time
 \Rightarrow Higher short-circuit current

(b) Very large capacitance :-

 

* This case, the PMOS will be in saturation only for a small interval of transition time
 \Rightarrow Reduced short-circuit current

\therefore Peak short-circuit current is a function of input AND output voltage transition times.