

EE671: VLSI DESIGN

SPRING 2024/25

LAXMEESHA SOMAPPA
DEPARTMENT OF ELECTRICAL ENGINEERING
IIT BOMBAY
laxmeesha@ee.iitb.ac.in



LECTURE – 17


ARITHMETIC IP: MULTIPLIERS

Acknowledgement: Prof. D.K.S

laxmeesha@ee.iitb.ac.in



BINARY MULTIPLIER: BASICS

 

- ❑ Rules: a) bit-wise multiplication (AND gate)
- b) Repeat bit-wise multiplication → generates partial product
- c) Shift & add all partial products → final product



BINARY MULTIPLIER: BASICS


- Say we want to perform $A \times B$ (A and B are binary numbers)

$$A = \sum_{i=0}^{n-1} 2^i a_i \quad B = \sum_{j=0}^{n-1} 2^j b_j$$

- We can generate any bit of a partial product using AND of (a_i, b_j)
- All bits of partial products can be computed using AND gates
- Use adders to add the partial products
- This architecture is called an Array Multiplier


ARRAY MULTIPLIER

- A 4-bit array multiplier structure

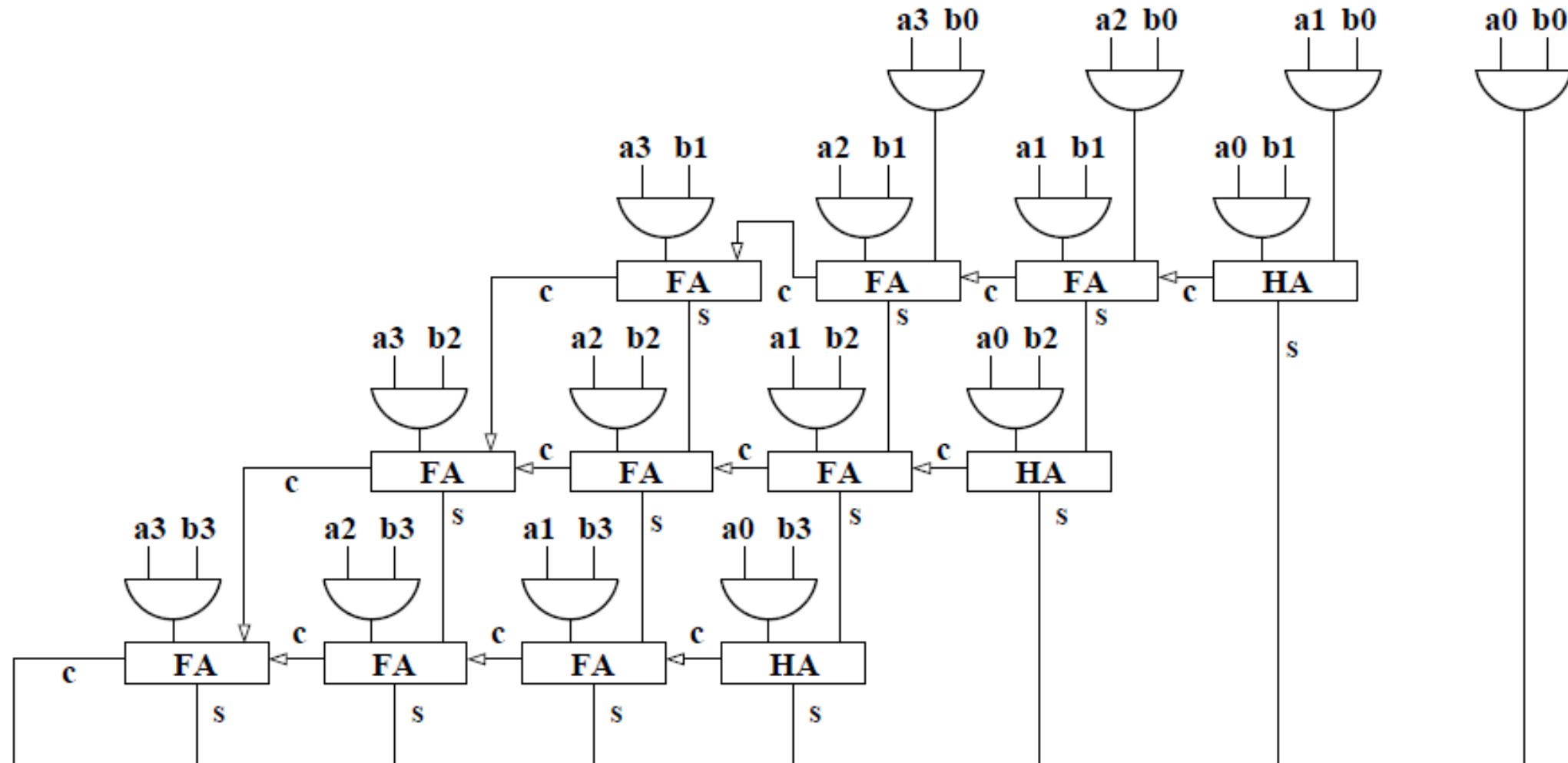

ARRAY MULTIPLIER

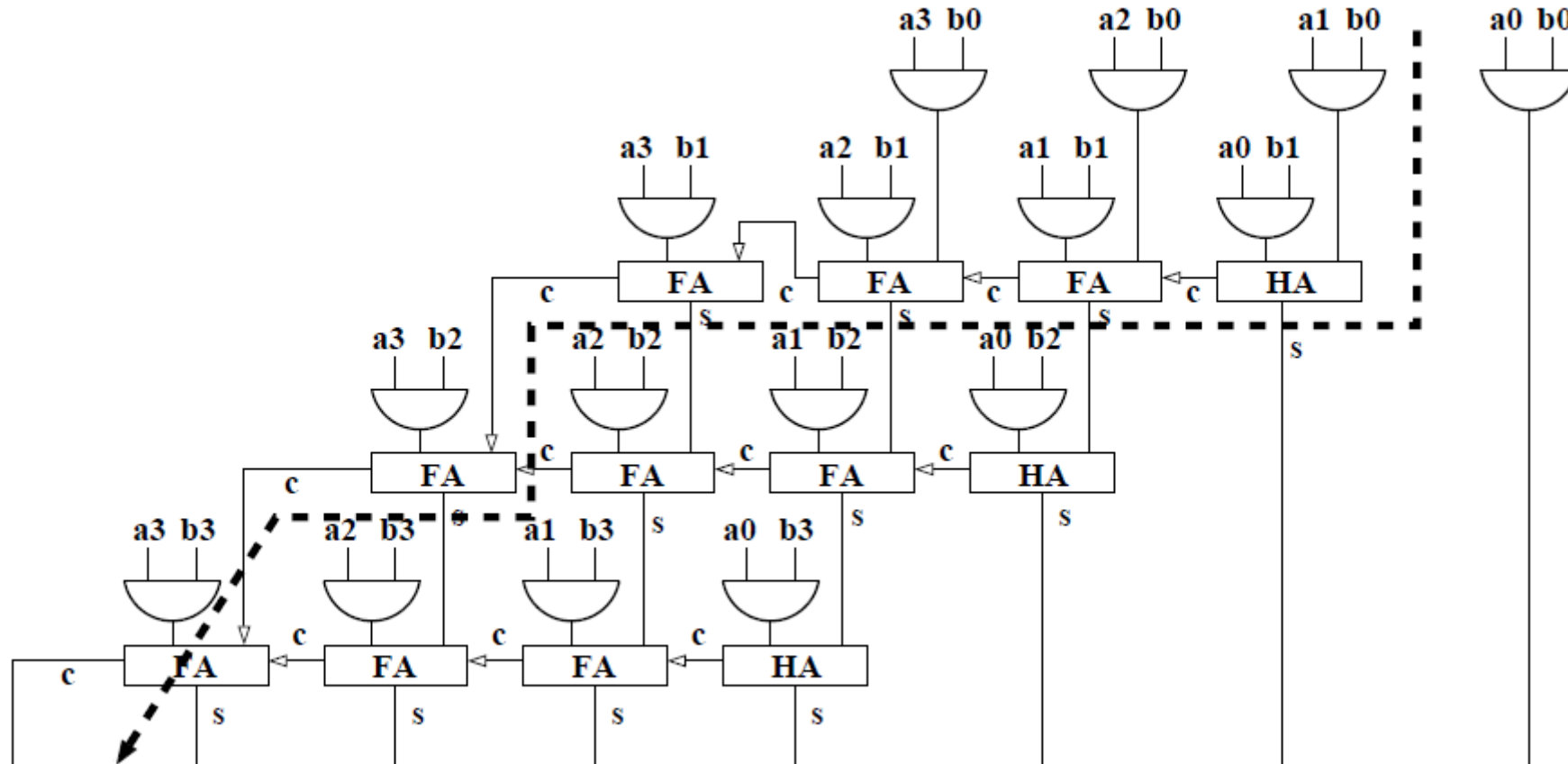- ❑ A 4-bit array multiplier: critical path \rightarrow adders in the path !



- ❑ Can we speed-up the multiplier further?
- ❑ Can we reduce number of partial products using a 2-bit multiplication instead ?

BOOTH ENCODING

- ❑ Consider $A \times B$, and we want to multiply two bits (of multiplier B) at a time
- ❑ If $B = 00 \rightarrow$ partial product will be 0
- ❑ If $B = 01 \rightarrow$ partial product will be A
- ❑ If $B = 10 \rightarrow$ partial product will be $2A$
 - ❑ Simple left shift operation
- ❑ If $B = 11 \rightarrow$ partial product will be $3A$

- ❑ How to perform $3A$ with a simple operation?
 - ❑ $3A = 4A - A$
 - ❑ What if $4A$ operation is shifted to next pair of bits?
 - ❑ The next pair already has higher binary weight (higher by factor 4)
 - ❑ $4A$ is as simple as adding 1 to the next pair of bits in B
 - ❑ $-A$ can be generated from a subtractor (2's complement adder)



MODIFIED BOOTH ENCODING

- ❑ To simplify the logic of “when to” generate $4A$
 - ❑ Generating $2A$ is done similar to $3A$
 - ❑ $3A = 4A - A$ (subtract A and tell next group to add 4)
 - ❑ $2A = 4A - 2A$ (subtract $2A$ and tell next group to add 4)

- ❑ In summary (look at group of 2 bits in B):
 - ❑ $00 \rightarrow$ No operation
 - ❑ $01 \rightarrow$ add A
 - ❑ $10 \rightarrow$ subtract $2A$ and ask next group to add $4A$
 - ❑ $11 \rightarrow$ subtract A and ask next group to add $4A$
 - ❑ Next group will see the MSB of previous group \rightarrow if “1”, add 1 to the multiplier bit group (current two bits in B)



MODIFIED BOOTH ENCODING

❑ Modified Algorithm:

- ❑ Look at 3 bits (with one bit overlap) in B (multiplier)
- ❑ Current 2 bits and MSB of the previous group of 2 bits (in B)
- ❑ For the first group of 2 bits, assume a 0 to the right
- ❑ Move from right to left
- ❑ After handling the previous group, A is shifted left by two positions → inherent multiplication by 4
 - ❑ This means adding $4A$ on behalf of previous group is same as adding +1 to the multiplier (bits of B) to the current group



MODIFIED BOOTH ENCODING

❑ Algorithm: to generate partial products

Current 2-bits	Multiplier for these	Previous MSBit	Pending Increment	Total Multiplier
00	0	0	0	0
01	+1	0	0	+1
10	-2	0	0	-2
11	-1	0	0	-1
00	0	1	+1	+1
01	+1	1	+1	+2
10	-2	1	+1	-1
11	-1	1	+1	0



MODIFIED BOOTH ENCODING

- ❑ Algorithm: say multiplying Y and X
 - ❑ Generate partial products with group of 2 bits



Y_{i+1}	Y_i	Y_{i-1}	Partial product
0	0	0	0
0	0	1	$+x$
0	1	0	$+x$
0	1	1	$+2x$
1	0	0	$-2x$
1	0	1	$-x$
1	1	0	$-x$
1	1	1	0

- ❑ Add partial products using any of the adders you have learnt before to get the final product – how many adders?




MODIFIED BOOTH ENCODING

  - ❑ Adding partial products:
 - ❑ Adders in critical path (array multiplier)
 - ❑ Speed up the partial production addition?
- ❑ We have already looked at tree adders for faster additions! – Similar idea



MODIFIED BOOTH ENCODING

 - ❑ We looked at 1-bit adders to implement 'N' bit adders
- ❑ Can we also have a 2-bit adder to add partial products?




- ❑ cy1 is the carry from the previous 2-bit group partial product addition
- ❑ No rippling of carry from right to left!!!



MODIFIED BOOTH ENCODING

 
- 2-bit adders to implement 'N' bit adders: for PP addition



- Save output in two registers
- Add these two registers using any adder that we have seen

MODIFIED BOOTH ENCODING

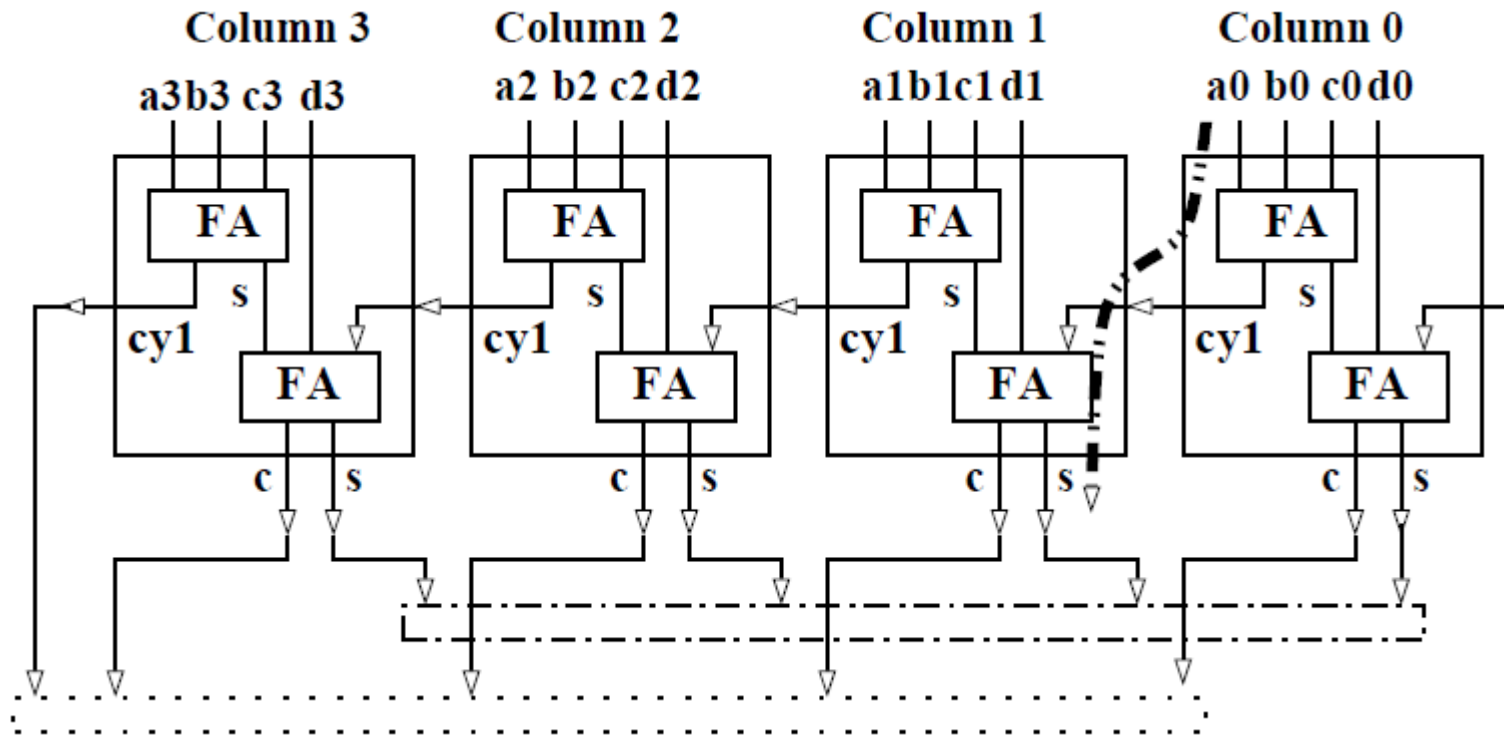- PP addition: critical path (no carry ripple except for the last 2-register addition)




					a3	a2	a1	a0	
					x	b3	b2	b1	b0
				a3.b0	a2.b0	a1.b0	a0.b0		
		a3.b1	a2.b1	a1.b1	a0.b1				
	a3.b2	a2.b2	a1.b2	a0.b2					
a3.b3	a2.b3	a1.b3	a0.b3						



A 4X4 WALLACE MULTIPLIER: FIRST REDUCTION

For wires within the top 3 rows:

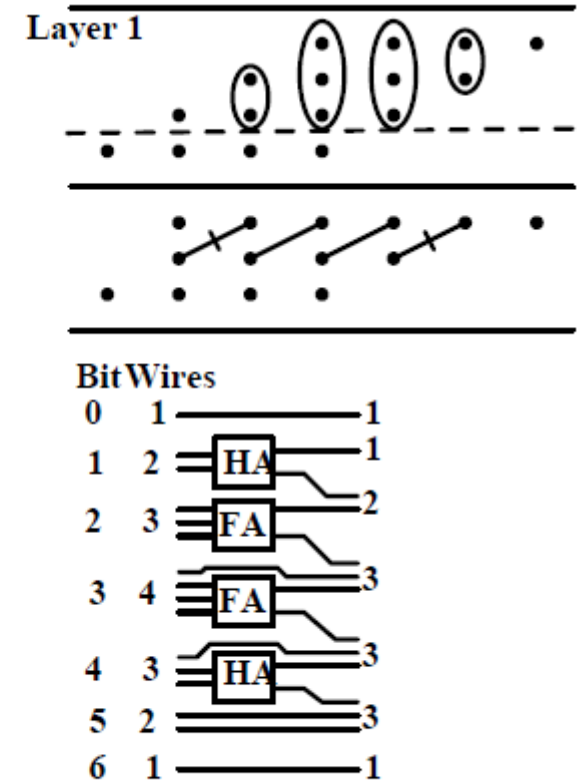
- Bit 0 has a single wire: passed through.
- Bit 1 has 2 wires: fed to a half adder.
- Bits 2 and 3 have 3 wires: fed to full adders.
- Bit 4 has 2 wires (in the group of 3): fed to a half adder.
- Bit 5 has 1 wire: passed through.



A 4X4 WALLACE MULTIPLIER: AFTER FIRST REDUCTION

After first reduction

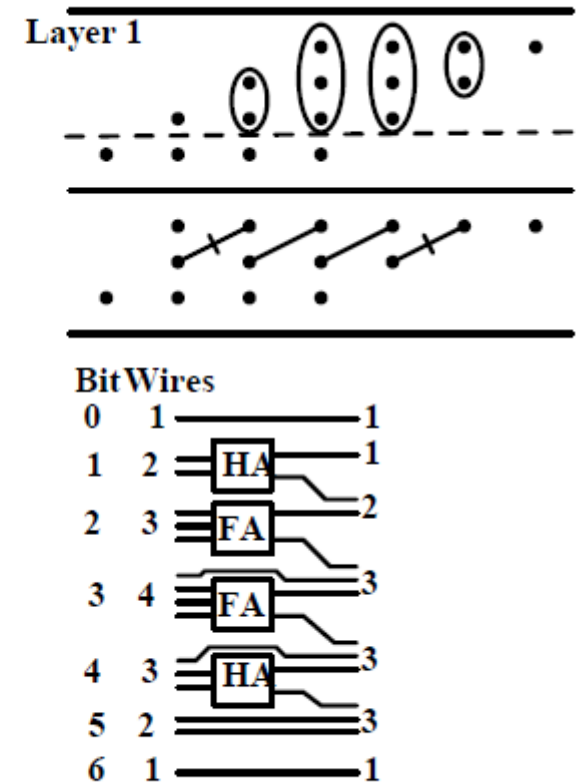
- Bits 0, 1 and 6 have a single wire.
- Bit 2 has 2 wires: carry of the half adder at bit 1 and the sum of full adder at bit 2.
- Bits 3 and 4 have 3 wires: carry of the full adder at lower weight, the sum wire from their full/half adder and a passed through wire.
- Bit 5 has 3 wires: carry of bit 4 plus 2 fed through wires.



A 4X4 WALLACE MULTIPLIER: SECOND REDUCTION

Since Bits 3, 4 and 5 have 3 wires each, we need another reduction layer. This will be the last reduction layer.

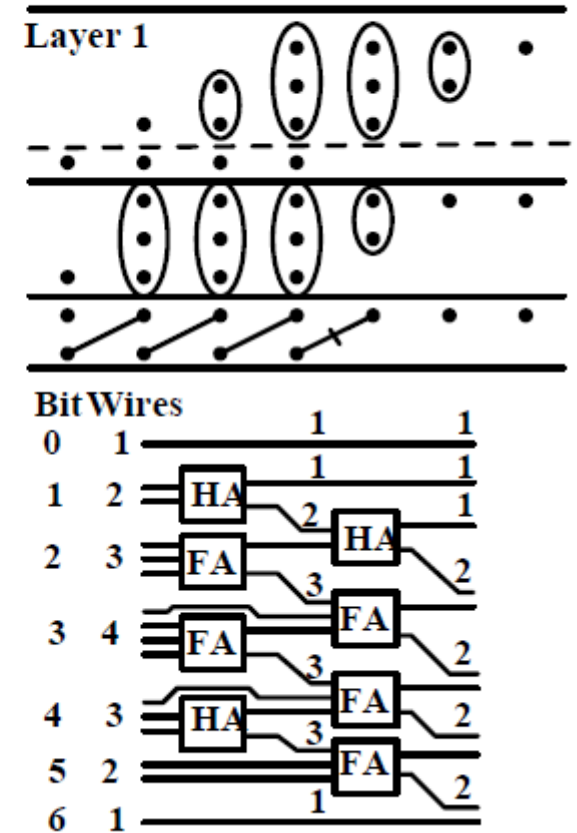
- Bits 0 and 1 have single wires. These are fed through.
- Bit 2 has 2 wires: these are fed to a half adder.
- Bits 3, 4 and 5 have 3 wires: These are fed to full adders.



A 4X4 WALLACE MULTIPLIER: AFTER SECOND REDUCTION

Bits 0, 1, and 2 have single wires which carry the final result.

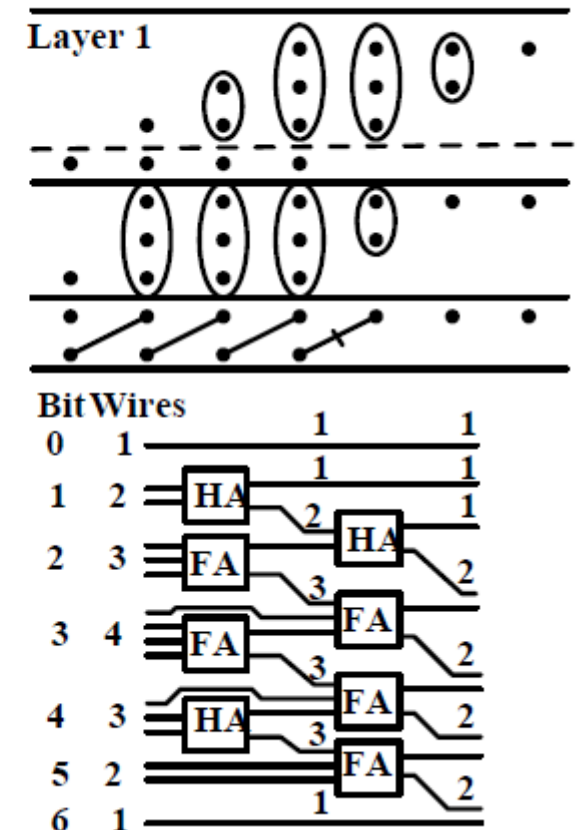
- Bit 3 has 2 wires: carry of the half adder at bit 2 and sum of the full adder at bit 3.
- Bit 4 has 2 wires: carry of the full adder at bit 3, and sum of the full adder at bit 4.
- Bit 5 has 2 wires, carry of bit 4 and sum of bit 5.
- Bit 6 has 2 wires, carry of bit 5 and 1 fed through wire.



A 4X4 WALLACE MULTIPLIER: FINAL ADDITION

After the second layer, no bit has more than 2 wires. Single wires at bits 0, 1 and 2 are fed through to the output.

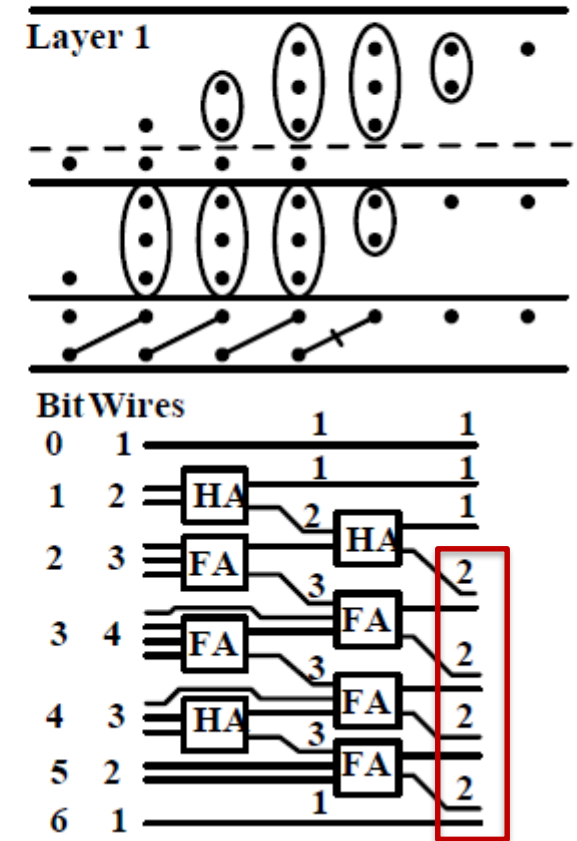- A fast conventional adder is used to add the 2 bits each at Bits 3, 4, 5 and 6.
- Notice that we do not need a full width fast adder.
- This is because the half adders at low weights have already rippled the carry while the rest of weights were being reduced.
- This makes the final adder smaller and faster.



A 4-bit adder



8x8 WALLACE MULTIPLIER

