

EE671: VLSI DESIGN

SPRING 2024/25

LAXMEESHA SOMAPPA
DEPARTMENT OF ELECTRICAL ENGINEERING
IIT BOMBAY
laxmeesha@ee.iitb.ac.in



LECTURE – 18


ARITHMETIC IP: MULTIPLIERS

Acknowledgement: Prof. D.K.S

laxmeesha@ee.iitb.ac.in



BINARY MULTIPLIER: BASICS

 


- ❑ Rules: a) bit-wise multiplication (AND gate)
- b) Repeat bit-wise multiplication → generates partial product
- c) Shift & add all partial products → final product



ARRAY MULTIPLIER

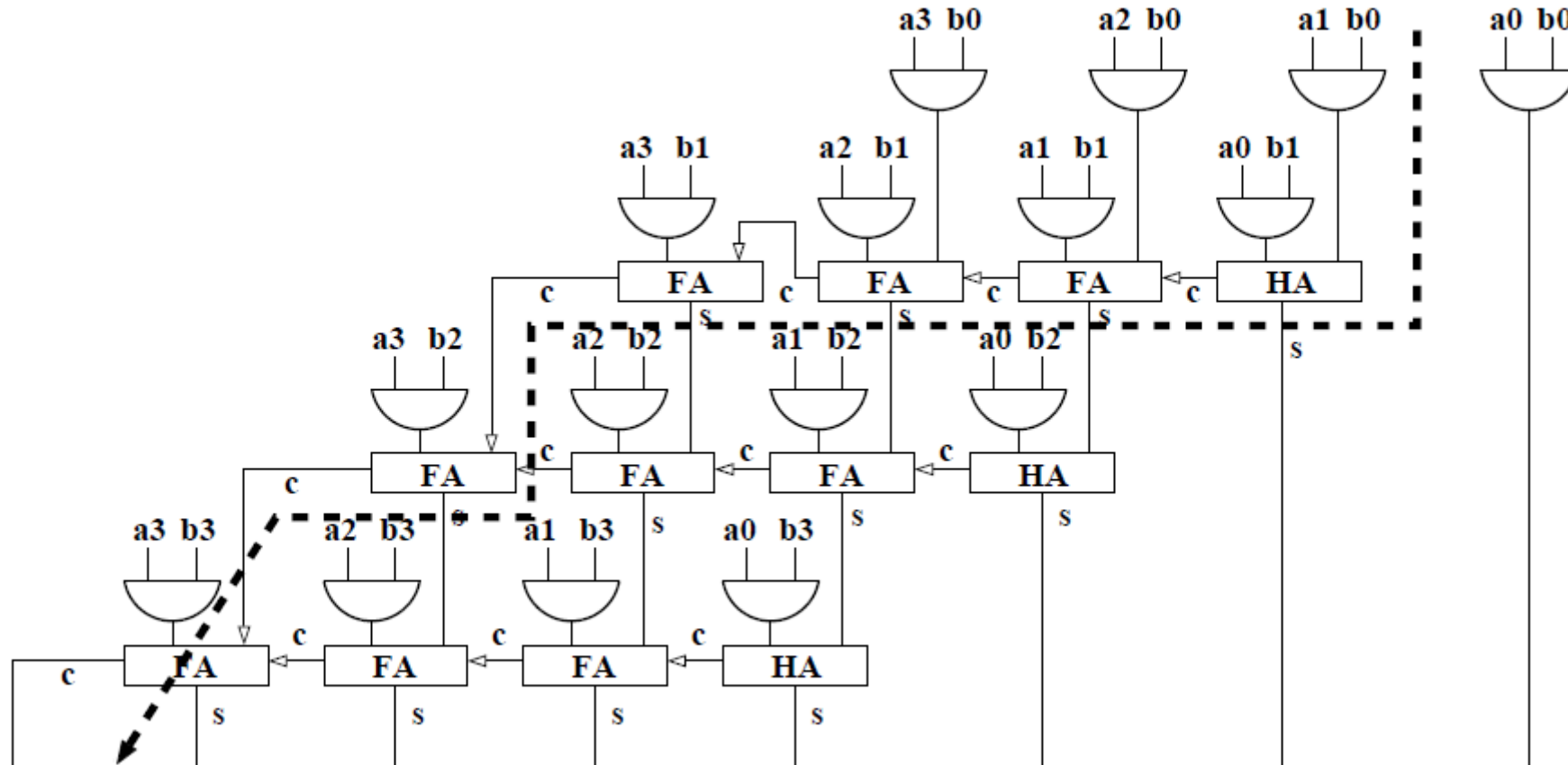- A 4-bit array multiplier: critical path \rightarrow adders in the path !



- Can we speed-up the multiplier further?
- Can we reduce number of partial products using a 2-bit multiplication instead ?

MODIFIED BOOTH ENCODING

❑ Modified Algorithm:

- ❑ Look at 3 bits (with one bit overlap) in B (multiplier)
- ❑ Current 2 bits and MSB of the previous group of 2 bits (in B)
- ❑ For the first group of 2 bits, assume a 0 to the right
- ❑ Move from right to left
- ❑ After handling the previous group, A is shifted left by two positions → inherent multiplication by 4
 - ❑ This means adding $4A$ on behalf of previous group is same as adding +1 to the multiplier (bits of B) to the current group



MODIFIED BOOTH ENCODING

- ❑ Same example: multiply $A = 229$ and $B = 222$
- ❑ $A = 11100101$, $B = 11011110$
- ❑ Booth Encoding Multiplier: Recall booth encoding table

B_{i+1}	B_i	B_{i-1}	PP
0	0	0	0
0	0	1	A
0	1	0	A
0	1	1	2A
1	0	0	-2A
1	0	1	-A
1	1	0	-A
1	1	1	0

MODIFIED BOOTH ENCODING

$$A = 0000000011100101$$

$$2A = 00000000111001010$$

$$-A = 1111111100011011$$

$$-2A = 11111111000110110$$

$$B = 11011110$$

$$B = 11|01|11|10$$

$$B = 00|11|01|11|100$$

$$PP = A|-A|2A|0|-2A$$

B_{i+1}	B_i	B_{i-1}	PP
0	0	0	0
0	0	1	A
0	1	0	A
0	1	1	2A
1	0	0	-2A
1	0	1	-A
1	1	0	-A
1	1	1	0



MODIFIED BOOTH ENCODING

$$A = 0000000011100101$$

$$-A = 1111111100011011$$

$$2A = 00000000111001010$$

$$-2A = 11111111000110110$$

$$PP = A|-A|2A|0|-2A$$


$$\begin{array}{r}
 1111111000110110 \\
 00000000000000xx \\
 \hline
 1111111000110110 \\
 000111001010xxxx \\
 \hline
 10001101011010110 \\
 1111111100011011xxxxxx \\
 \hline
 10000001110000110010110 \\
 0000000011100101xxxxxxxxx \\
 \hline
 010000011100011010010110
 \end{array}$$

$A \times B = 1100011010010110$ with only 5 partial products instead of 8 in an array multiplier



MODIFIED BOOTH ENCODING

 
- ❑ We looked at 1-bit adders to implement 'N' bit adders
- ❑ Can we also have a 2-bit adder to add partial products?



- ❑ cy1 is the carry from the previous 2-bit group partial product addition
- ❑ No rippling of carry from right to left!!!

MODIFIED BOOTH ENCODING


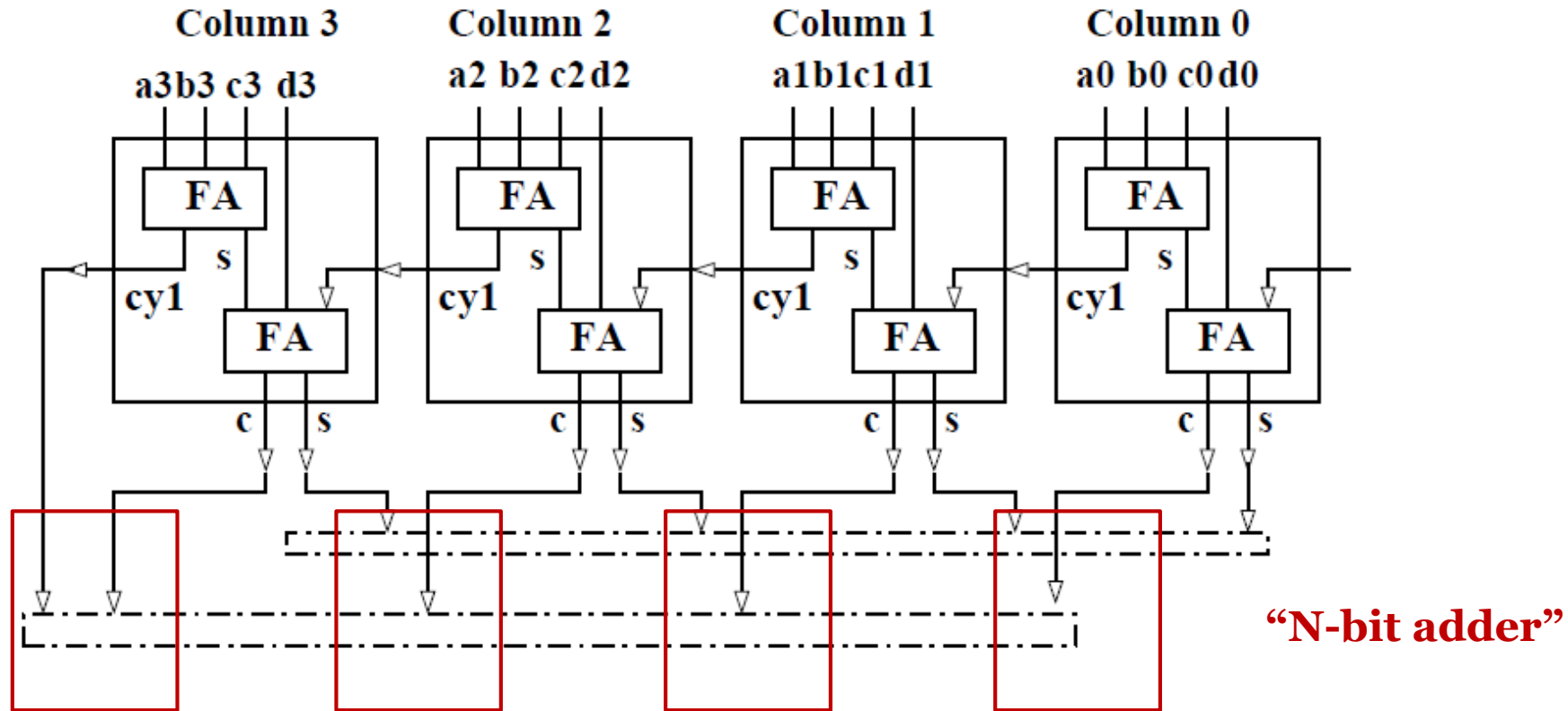
- 2-bit adders to implement 'N' bit adders: for PP addition



- Save output in two registers
- Add these two registers using any adder that we have seen

MODIFIED BOOTH ENCODING

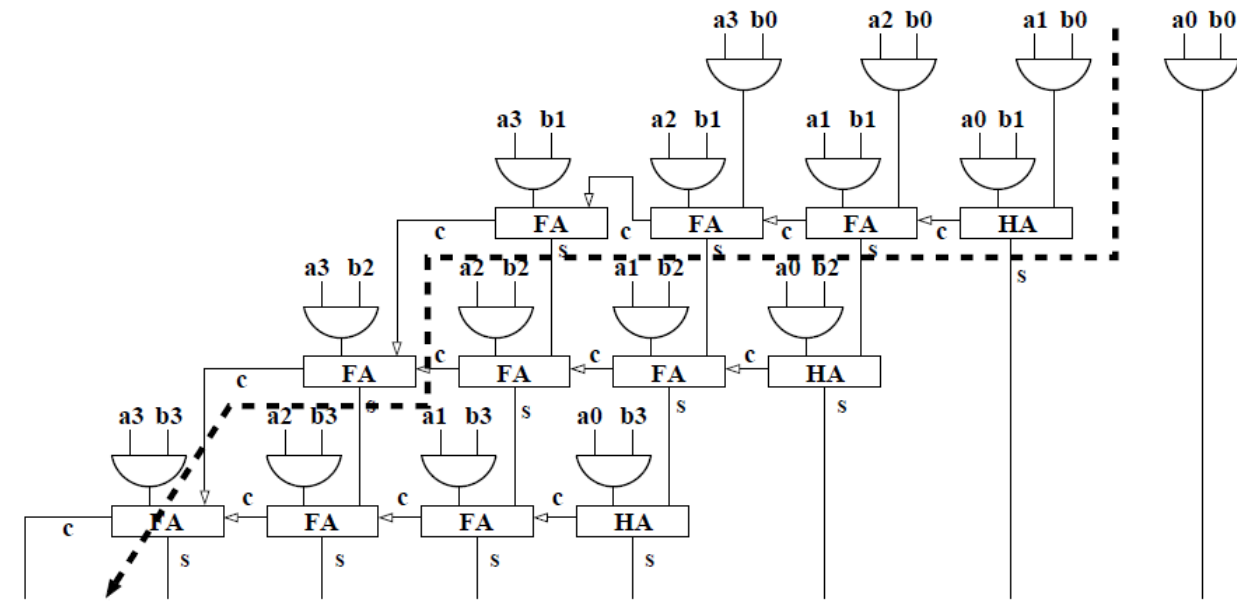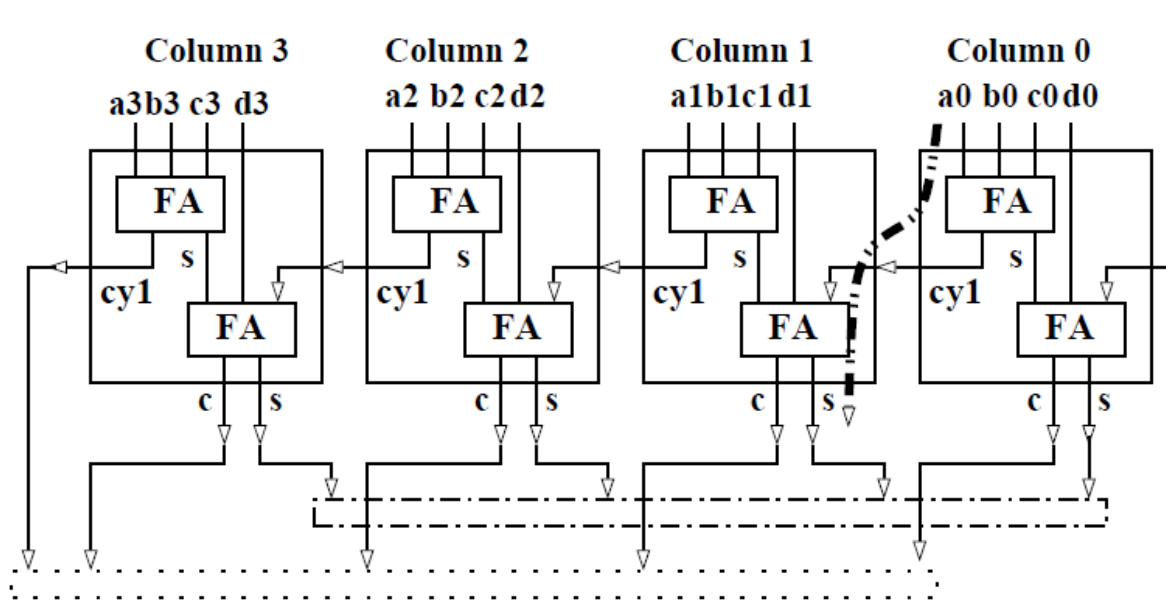- PP addition: critical path (no carry ripple except for the last 2-register addition) – compare with normal ripple adder!



WALLACE MULTIPLIERS

□ Consider 4x4 multiplication

				a3	a2	a1	a0	
				x	b3	b2	b1	b0
				a3.b0	a2.b0	a1.b0	a0.b0	
				a3.b1	a2.b1	a1.b1	a0.b1	
				a3.b2	a2.b2	a1.b2	a0.b2	
a3.b3	a2.b3	a1.b3	a0.b3					


Bit	Terms	Wires
0	a0b0	1
1	a0b1, a1b0	2
2	a0b2, a1b1, a2b0	3
3	a0b3, a1b2, a2b1, a3b0	4
4	a1b3, a2b2, a3b1	3
5	a2b3, a3b2	2
6	a3b3	1



A 4X4 WALLACE MULTIPLIER: AFTER FIRST REDUCTION

After first reduction

 
- Bits 0, 1 and 6 have a single wire.
- Bit 2 has 2 wires: carry of the half adder at bit 1 and the sum of full adder at bit 2.
- Bits 3 and 4 have 3 wires: carry of the full adder at lower weight, the sum wire from their full/half adder and a passed through wire.
- Bit 5 has 3 wires: carry of bit 4 plus 2 fed through wires.



A 4X4 WALLACE MULTIPLIER: AFTER SECOND REDUCTION

Bits 0, 1, and 2 have single wires which carry the final result.

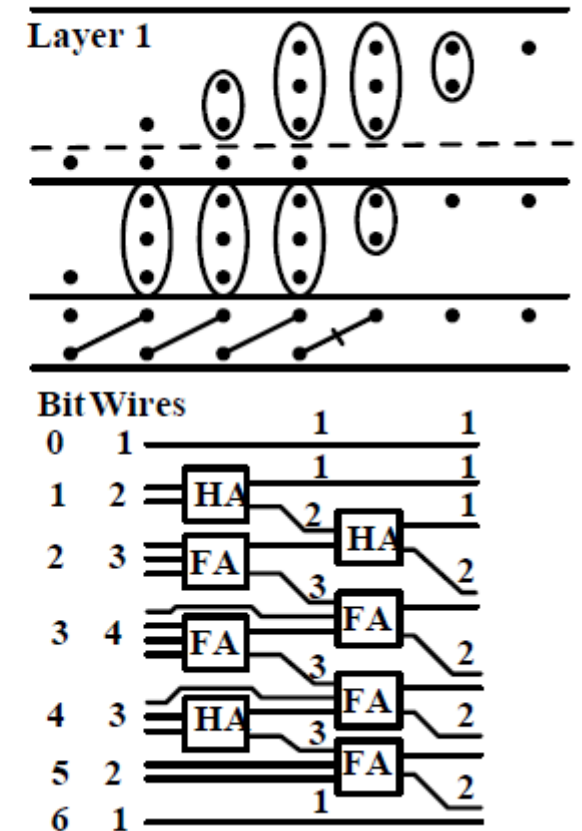
- Bit 3 has 2 wires: carry of the half adder at bit 2 and sum of the full adder at bit 3.
- Bit 4 has 2 wires: carry of the full adder at bit 3, and sum of the full adder at bit 4.
- Bit 5 has 2 wires, carry of bit 4 and sum of bit 5.
- Bit 6 has 2 wires, carry of bit 5 and 1 fed through wire.



A 4X4 WALLACE MULTIPLIER: FINAL ADDITION

After the second layer, no bit has more than 2 wires. Single wires at bits 0, 1 and 2 are fed through to the output.

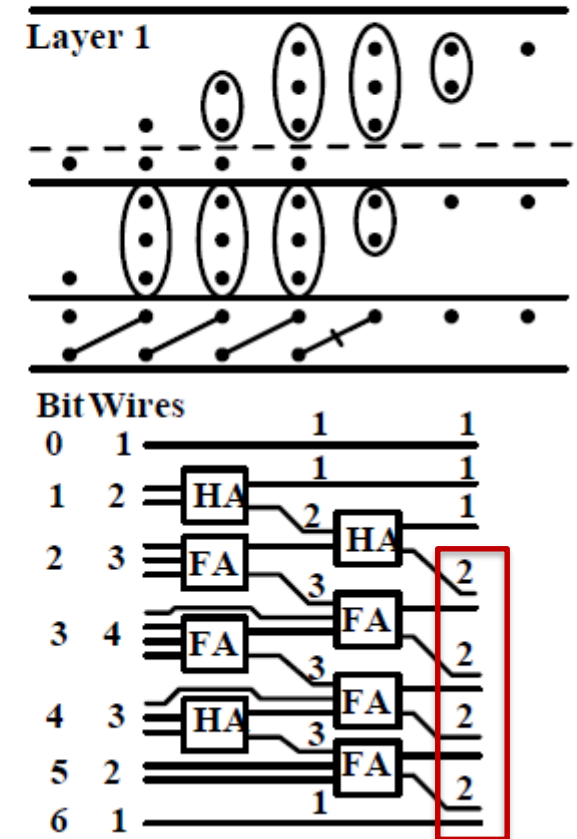
- A fast conventional adder is used to add the 2 bits each at Bits 3, 4, 5 and 6.
- Notice that we do not need a full width fast adder.
- This is because the half adders at low weights have already rippled the carry while the rest of weights were being reduced.
- This makes the final adder smaller and faster.



A 4-bit adder



8X8 WALLACE MULTIPLIER

 

First reduction:
HAs: 4, FAs: 12

Second reduction:
HAs: 3, FAs: 13

Third reduction:
HAs: 4, FAs: 6

Fourth reduction:
HAs: 4, FAs: 7

Final: 11-bit fast adder



DADDA MULTIPLIER

- ❑ Similar to Wallace: but,
 - ❑ Wallace: reduce the PP bits as soon as possible (i.e., moment you see more than or equal to 2 bits, put HA or FA)
 - ❑ Dadda: reduce the PP bits as late as possible, based on
$$d_{k+1} = \text{floor}(3/2 d_k) \text{ and } d_1 = 2$$
Possible $d = 2, 3, 4, 6, 9, 13, 19 \dots$
- ❑ For an $N \times M$ multiplier,
$$d < \min(N, M)$$
- ❑ Example: for 4×4 , $d = 3$, for 8×8 , $d = 6$
- ❑ At every stage, if there are **more than** d bits, we reduce using FA/HA
 - ❑ Reduce d after every reduction



DADDA MULTIPLIERS

□ Consider 4x4 multiplication

				a3	a2	a1	a0	
				x	b3	b2	b1	b0
				a3.b0	a2.b0	a1.b0	a0.b0	
				a3.b1	a2.b1	a1.b1	a0.b1	
				a3.b2	a2.b2	a1.b2	a0.b2	
a3.b3	a2.b3	a1.b3	a0.b3					


Bit	Terms	Wires
0	a0b0	1
1	a0b1, a1b0	2
2	a0b2, a1b1, a2b0	3
3	a0b3, a1b2, a2b1, a3b0	4
4	a1b3, a2b2, a3b1	3
5	a2b3, a3b2	2
6	a3b3	1

□ $d = 3$ for 4x4 multiplier



DADDA MULTIPLIERS: FIRST REDUCTION

□ First reduction, $d = 3$

 


- Wt.1 has the single wire which was fed through.
- Wt.2 has 2 fed through wires.
- Wt.4 has 3 wires: all passed through.
- Wt.8 has 3 wires: sum of the half adder at wt.4, and 2 passed through.
- Wt.16 has 3 wires: carry of wt. 8, sum of half adder at 16 and 1 passed through.
- Wt.32 has 3 wires: carry of wt. 16 and 2 passed through.
- Wt.64 has 1 fed through wire.



DADDA MULTIPLIERS: FIRST REDUCTION



□ Second reduction, $d = 2$

 


- 3 wires at Wt. 4 are reduced to 2 by a half adder: No carry in expected.
- Wt. 8 has 3 input wires. Carry will arrive from Wt. 4. Reduced using a Full adder.
- Wt. 16 has 3 input wires. Carry will arrive from Wt. 8. Reduced using a full adder.
- Wt. 32 has 3 input wires. Carry will arrive from Wt. 16. Reduced using a full adder.
- Wt. 64 has 1 input wire. Carry will arrive from Wt. 32, making it 2 output wires, which will be fed through.

4X4 COMPARISON

Wallace Multiplier

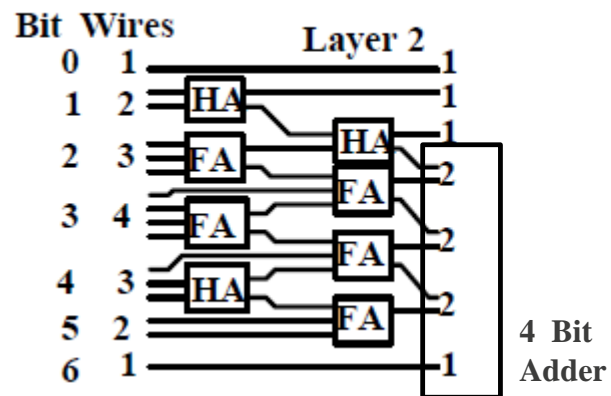 


Dadda Multiplier

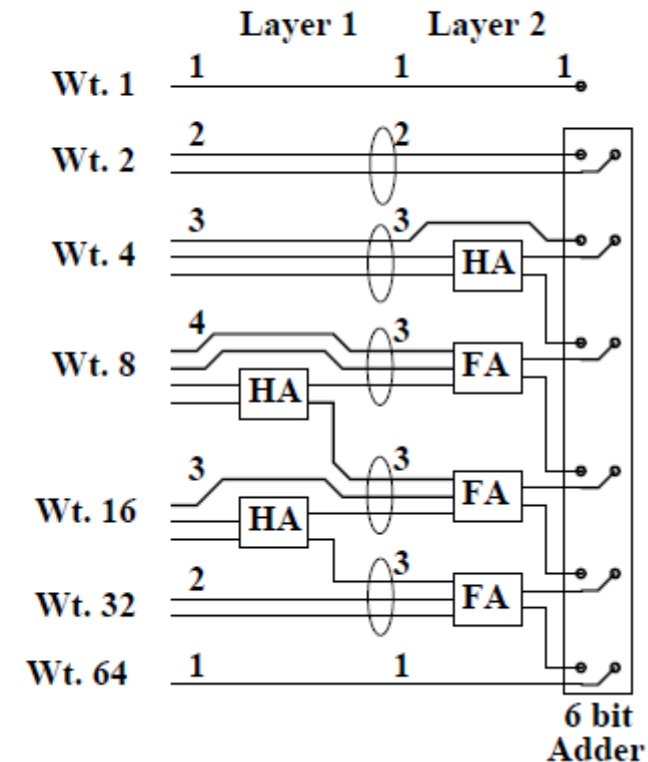


- ❑ Both use 2 layers of reduction
- ❑ Wallace: 3 HA + 5 FA, Dadda: 3 HA + 3 FA
- ❑ Wallace: 4-bit fast adder, Dadda: 6-bit fast adder

DADDA: 8x8

 


□ First reduction, $d = 6$

 


DADDA: 8x8

□ Second reduction, $d = 4$

 

DADDA: 8x8

□ Third reduction, $d = 3$

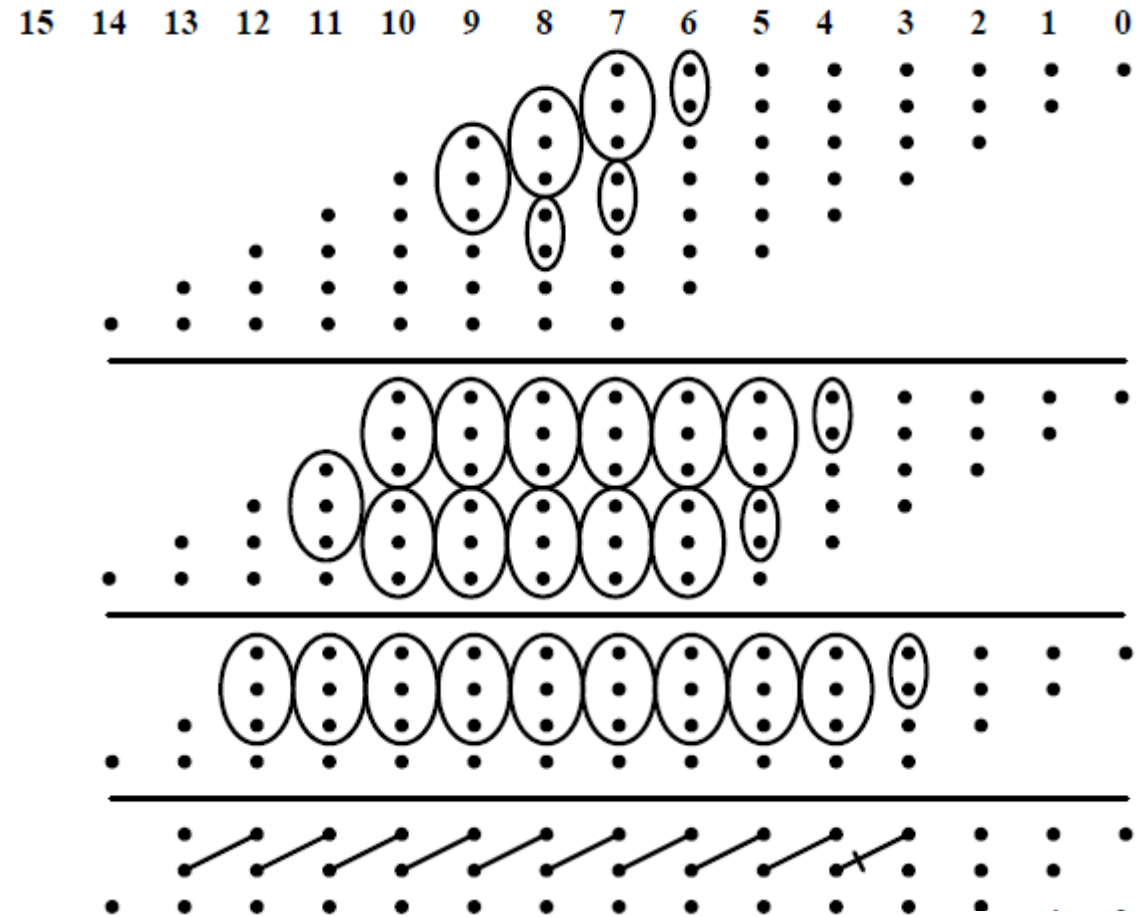

DADDA: 8x8

□ Final reduction, $d = 2$ (14-bit fast –adder)

