
 



Lecture-11

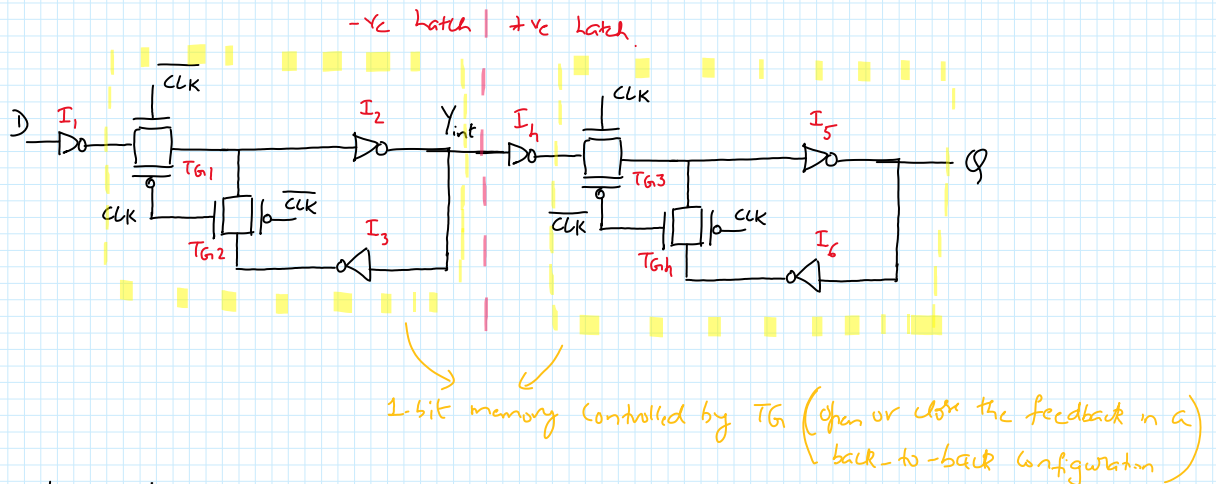

* We will redraw the +ve edge triggered FF as below.



 * We can push inverter I_h to the output Q . This will shield the memory element of the second latch from external capacitance. i.e.,




* Functionally, there is no change in the operation. (You can verify by passing input @ D and checking Q)

* Note that the T_s (setup time) is still the same, $T_s = t_{PI1} + t_{PTG1} + t_{PI2} + t_{PI3}$.

But the T_{ϕ} has increased, $T_{\phi} = t_{PTG3} + t_{PI5} + t_{PIh}$

* The above DFF that we implemented has a symbol \rightarrow

 
* This one of the basic cell in a standard cell library.



* A Verilog Code like below, will be synthesized by the tool to this DFF that we have designed.

```
always @ (posedge CLK)
begin
    Q <= D;
end.
```

 - * Another basic cell in any standard cell library is a DFF with reset
 - ↳ Reset can be asynchronous (i.e. $Q=0$ when $RST=1$)
 - ↳ Reset can be synchronous (i.e. $Q=0$ when $RST=1$ and there is a CLK edge.)
- * Let's look at DFF with asynchronous RST. Consider our previous DFF circuit.



- * A new logic has to be inserted for RST after all the TG's since asynchronous should be independent of CLK. Since $Q=0$, Node Q_1 must immediately go to 1 when RST arrives.


- * A logic gate that provides an o/p of 1 when one of the input is fixed as 0: NAND

i.e.


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


} If $A=0$, $Y=1$ (LOGIC-1)
 } If $A=1$, $Y=\bar{B}$ (INVERTER)

 - * A 2 i/p NAND can act as an inverter or fixed logic-1 o/p based on input.
 ∴ Let's replace I_5 inverter with a NAND gate.



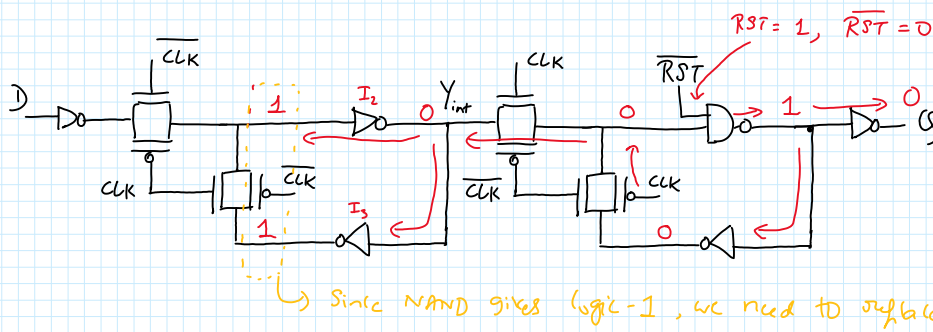- * Since there are two memory elements (i.e. 2 latches) in this FF, both memories need to be reset. ∴ I_2 or I_3 needs to be replaced by a NAND gate. To find out which, trace back from the output side as follows.



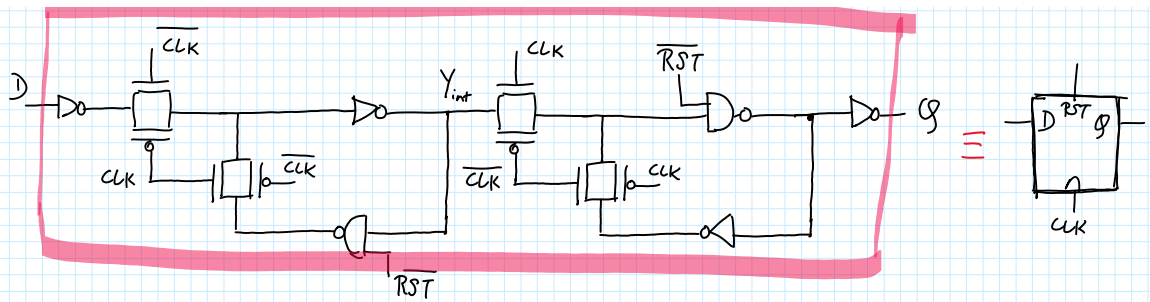


* A Verilog code like below, will be synthesised by the tool to this DFF that we have designed.

```

always @ (posedge CLK or RST)
begin
    if (RST)
        Q <= 0,
    else
        Q <= D,
end


```

 * Now, let's switch focus to a DFF with synchronous RST.



Additional tlu cannot be added here since change will be immediate!!
 We want RST to happen after CLK edge.
 => Latch-2 No change.

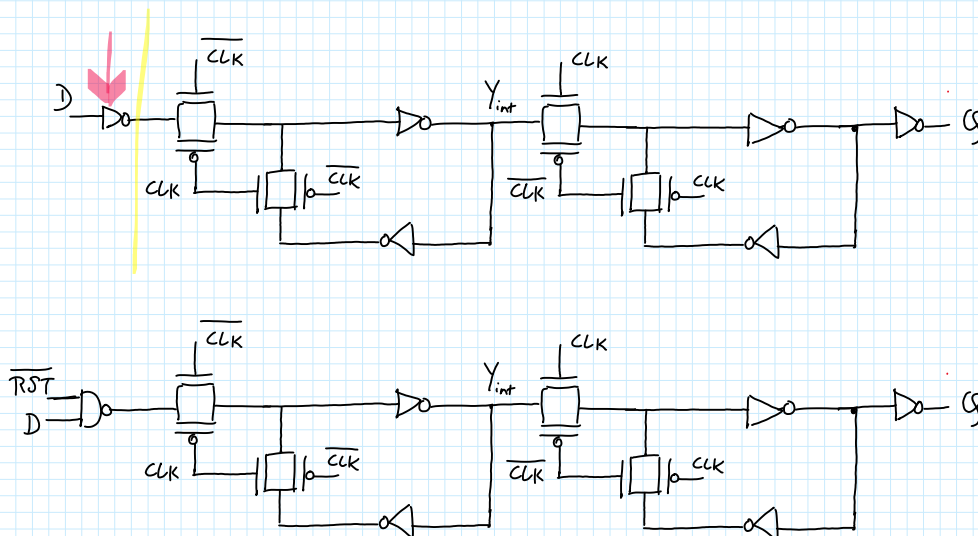* Since we cannot change latch-2, latch-1 cannot be changed as well. (since DFF is built using two similar latches) : Additional circuit must be added before latch-1.



i.e. if $RST=1$, the DFF latches 0 @ the edge!! (Synchronous RST)
 if $RST=0$, NAND gate acts like an inverter, which is our DFF

* A Verilog Code like below, will be synthesised by the tool to this DFF that we have designed.



```

always @ (posedge CLK)
begin
  if (RST)
    Q <= 0,
  else
    Q <= D,
end


```

* Another important cell to have is a DFF with asynchronous SET and RST.

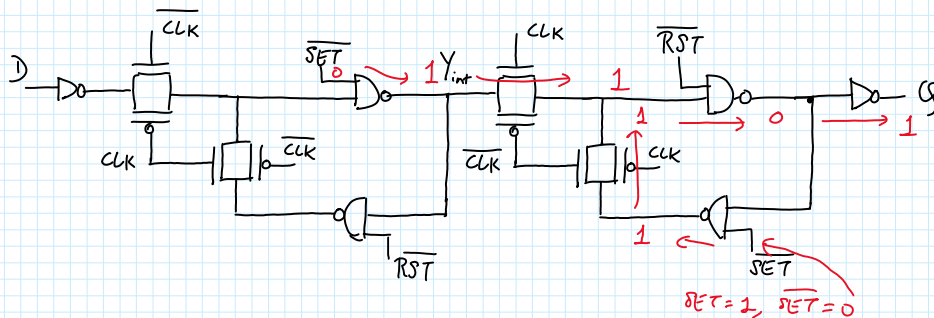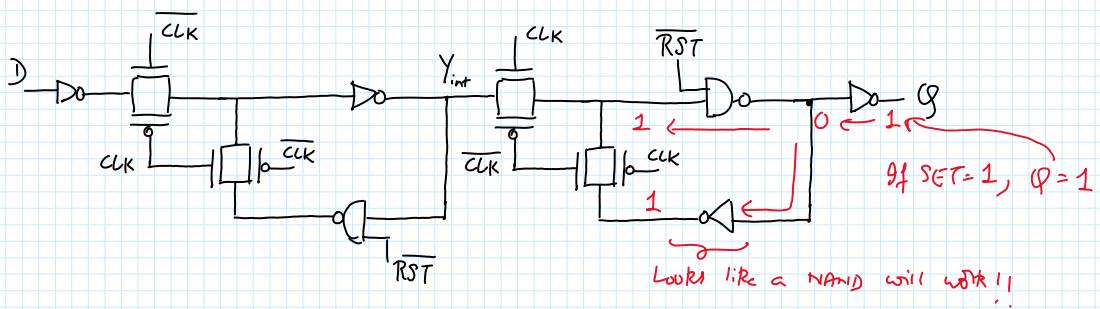
* If your Verilog Code has $Q \leftarrow 1$, we need to pick a DFF with SET



 * obtaining T_s , T_H and T_{CQ} from simulations.




a) T_s :-

 


b) T_H :-

b) T_H :-

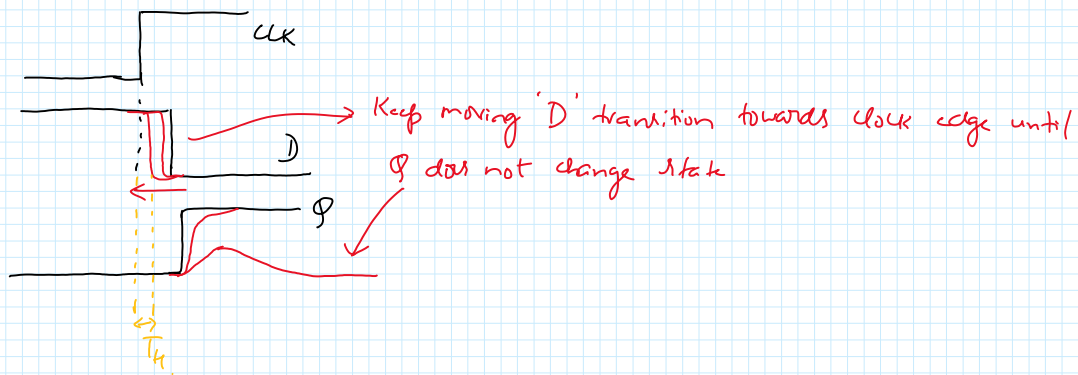

c) T_{cq} :- Having known T_S & T_H Apply D & CLK, without violating setup & hold criteria. Now find out 50% of CLK to 50% of Q delay.


* One final note on DFF

 

On a chip, it is imperative that you reduce the cap load on the clock line, to reduce power consumption. $P = CV^2f$ f is already high for clock

C: depends on how many MOSFETS it is driving.

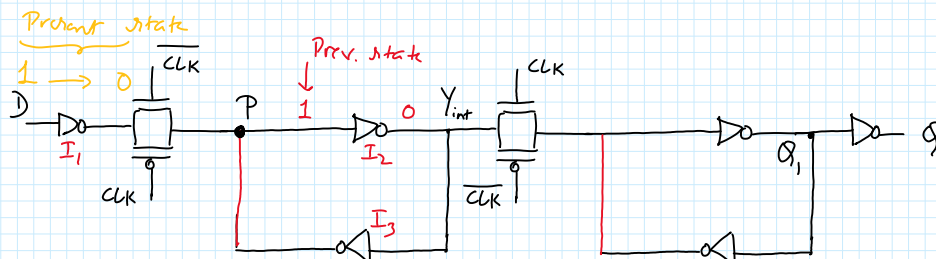The DFF above has total of 8 MOS with CLK or $\overline{\text{CLK}}$ drive. There are designs to reduce this clock load. One of the popular design is to remove two T₀'s.



* Assume Node P had logic 1 due to the previous state of the latch.


* Now, when $\text{CLK} = 0$, a new D input of logic-1 is applied.

* At node P, I_1 and I_3 are fighting for dominance.

- ↳ I_1 wants to enforce logic 0 on P
- ↳ I_3 wants to enforce logic 1 on P

* We want I_1 to win since we want to enforce the new input into the latch.

 + We want I_1 to win since we want to enforce the new input into the latch.
 ↳ To ensure this I_3 strength must be very small!!



I_3 and I_6 are weak inventors. i.e. $w_L < 1$ or L is increased for both PMOS & NMOS!!

* This kind of logic is called "Ratio'd logic" since we rely on ratio of strengths (strength of I_1 vs I_3) to ensure functionality

* Observe that the set-up time calculation is not straightforward since it depends on the sizing of I_1 & I_3 !!! ... Design is not straightforward

_____ x _____ x _____