

EE 618 (ZELE)

CMOS Analog VLSI Design: Question Bank

Note: Use the following wherever not specified explicitly, $V_{DD} = 3V$, $V_{Th} = 0.7V$ and $V_{Tp} = -0.8V$. Neglect body effect. Assume low frequency small signal model whenever required.

1. For the CS Amplifier in Figure 1 with diode connected load, find the $V_{in,max}$ (in V). Given $V_{DD} = 1.8V$, $g_{m1} = g_{m2}$, $V_{IN} = V_{OUT} = 0.6V$, $V_{TN} = |V_{TP}| = 0.4V$.

 


Figure 1

2. Given that M1 and M2 are in saturation, if the voltage at node Y is increased by a small value ΔV , then find the change in the voltage at node X.

 


Figure 2

3. Assuming all the transistors are in a saturation, find a small signal voltage gain for the following circuit:



 


Figure 4

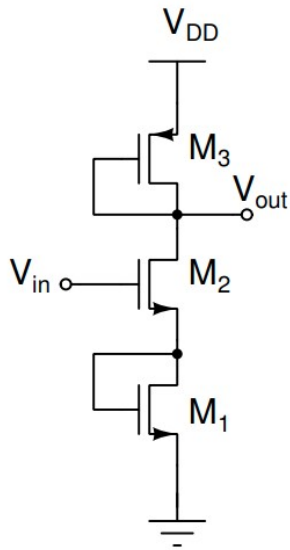
4. Assuming all transistors are in a saturation, find a small signal voltage gain for the following circuits:




a)

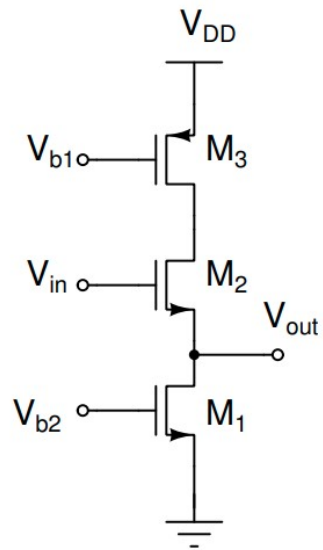


b)

 


c)

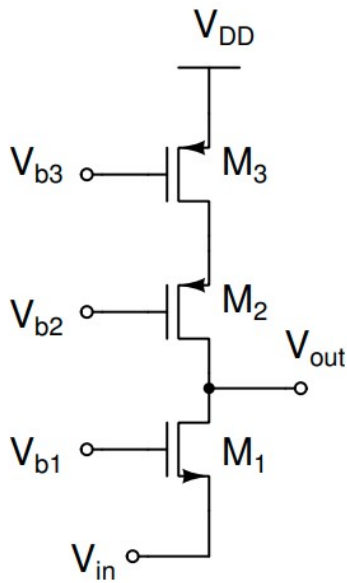

a)

 

b)

 

c)