

# EE671: VLSI DESIGN

## SPRING 2024/25

LAXMEESHA SOMAPPA  
DEPARTMENT OF ELECTRICAL ENGINEERING  
IIT BOMBAY  
[laxmeesha@ee.iitb.ac.in](mailto:laxmeesha@ee.iitb.ac.in)




# LECTURE – 32

## MEMORY: SRAM



# SRAM FULL PICTURE
 
## Implications:

- If  $n$  is very large (tall memory)  $\rightarrow$  the shared bitline per column is longer  $\rightarrow$  this is a long metal in the layout  $\rightarrow$  large bit-line capacitance  $\rightarrow$  memory will be slower
- If  $m$  is large (wide memory)  $\rightarrow$  the wordline per row is longer  $\rightarrow$  large wordline capacitance (because of routing and also the 2 access transistors gate cap per column)  $\rightarrow$  Address decoder will drive larger load  $\rightarrow$  delay limited by logical effort !!!!



# READ OPERATION

 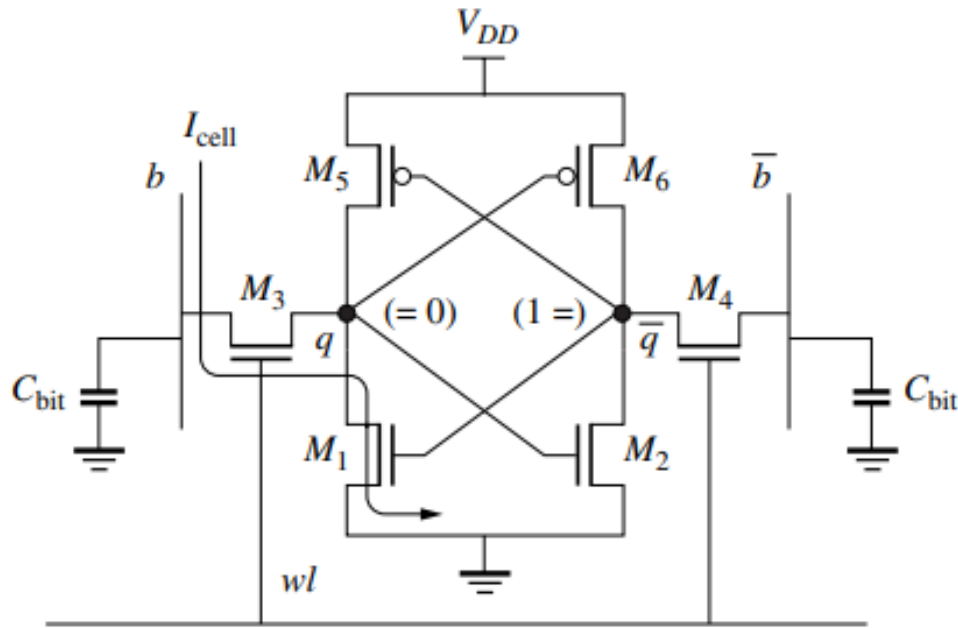

- ❑ M3 and M1 are actually fighting for node “q” → if M3 is strong it can turn on M2 !
- ❑ During read, we do not want to disturb the state of node “q”
  - ❑ i.e, change in node voltage “q” should not flip the previously stored data !
- ❑ To ensure the this, M3 and M1 will have to be sized accordingly
  - ❑ i.e., M1 should be stronger than M3 !! (M1 will have lower resistor than M3)







# DESIGN EXAMPLE: READ OPERATION

- ❑ Need to design SRAM bit cell in a technology with:
  - ❑  $L = 0.1 \mu\text{m}$ ,  $V_{\text{TN}} = |V_{\text{TP}}| = 0.4 \text{ V}$ ,  $V_{\text{DD}} = 1.2 \text{ V}$ ,  $\mu_n = 300 \text{ cm}^2/\text{V-s}$ ,  $\mu_p = 100 \text{ cm}^2/\text{V-s}$ , saturation velocity  $v_{\text{sat}} = 8 \times 10^6 \text{ cm/s}$ ,  $C_{\text{ox}} = 2 \mu\text{F}/\text{cm}^2$
- ❑ Design specifications of the SRAM bit cell are:
  - ❑ Total bit line capacitance = 1 pF
  - ❑ Amplifier needs minimum of  $\pm 200 \text{ mV}$  difference to amplify output to logic levels within 1 ns
  - ❑ The bit-cell inverter nodes can only tolerate a change of 100 mV during read
- ❑ Design equations:
  - ❑ MOS triode current,  $I_D \approx \mu C_{\text{ox}} \frac{W}{L} [(V_{\text{GS}} - VT)V_{\text{DS}} - \frac{V_{\text{DS}}^2}{2}]$
  - ❑ MOS saturation current,  $I_D \approx v_{\text{sat}} C_{\text{ox}} W (V_{\text{GS}} - VT)$ 
    - ❑ Under the assumption, for short channel MOSFETs, the velocity of the charges are saturated and hence the current will be lower than the current given by the quadratic equation







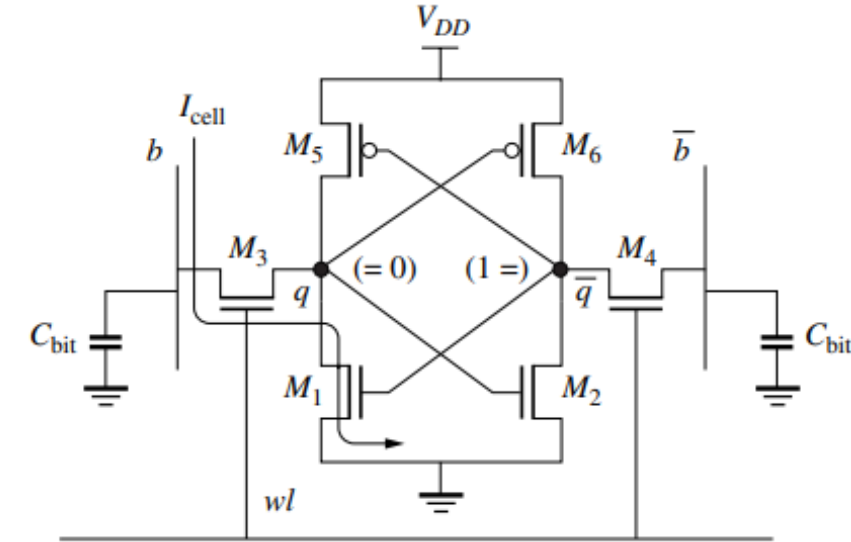
# DESIGN EXAMPLE: READ OPERATION

- ❑ Let us first consider the read operation
- ❑  $q = 0$  is stored in the bit-cell
- ❑ The bitlines ( $b$  and  $\bar{b}$ ) are pre-charged to  $V_{DD}$
- ❑ Consider the next spec, amplifier needs at least 200 mV
- ❑ Node  $b$  should discharge from  $V_{DD}$  to  $(V_{DD}-0.2)$  in 1 ns
- ❑ Difference voltage between  $b$  and  $\bar{b}$  will be 0.2 V
- ❑ We need to find out how much current is required to achieve this in 1 ns




$$I_{cell} = \frac{\Delta V}{\Delta T} C_{bit} \text{ (what other insights from this equation? } \rightarrow \text{ tall memory?)}$$

- ❑  $\Delta V = 0.2 \text{ V}$ ,  $\Delta T = 1 \text{ ns}$ ,  $C_{bit} = 1 \text{ pF}$  (all from the specs)
- ❑  $I_{cell} = 200 \mu\text{A}$
- ❑ Substitute current in sat equation,  $W_3 \approx 0.2 \mu\text{m}$ ,  $W_1 \approx 0.5 \mu\text{m}$
- ❑  $W_4 = W_3$  and  $W_2 = W_1$  and all  $L = 0.1 \mu\text{m}$


 
# DESIGN EXAMPLE: READ OPERATION

- ❑ To size  $M_6$  and  $M_5$ , let's look at the write operation
- ❑ Recall that to write a new data,
  - ❑ we need to flip the existing data in the bit cell
  - ❑ Remember  $M_1$  is stronger than  $M_3$  and will fight for node  $q$
  - ❑ Node  $\bar{q}$  must start discharging to logic 0 to write new data
  - ❑ For this to happen,  $M_2$  must start turning ON
    - ❑  $M_2$  will decisively turn ON when  $M_1$  is OFF
    - ❑  $M_1$  will turn OFF when node  $\bar{q}$  is just below  $V_T$  ( $M_1 V_{GS} = V_T$ )




- ❑ What MOSFETs are ON?
  - ❑  $M_4$  is in saturation
  - ❑  $M_6$  is in triode
- ❑ Equate the currents and set  $V_{q-} = V_T = 0.4 V$ 

$$\frac{W_4}{W_6} \approx 0.5$$
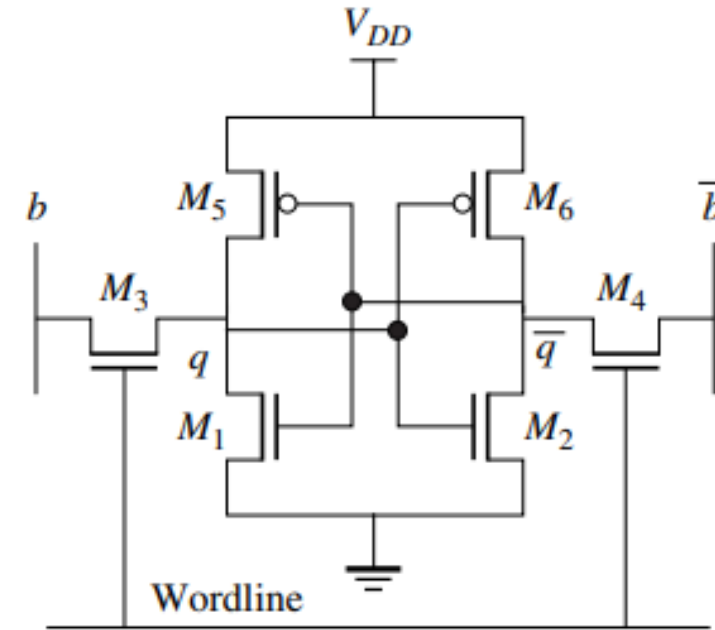
# DESIGN EXAMPLE

- $\frac{W_4}{W_6} \approx 0.5$
- $\frac{W_1}{W_3} \approx 2.5$
- $W_4 = W_3 = 0.2 \mu m$
- $W_2 = W_1 = 0.5 \mu m$
- $W_5 = W_6 = 0.4 \mu m$
- $L = 0.1 \mu m$




- M1, M2 strongest
- M3, M4 stronger than M5, M6 and weaker than M1, M2
- M5, M6 weakest (account for the mobility of devices when talking about strength) – in this example,  $\mu_n = 3 \mu_p$
- A rule of thumb in lower nodes: strength ratio is kept at 1.5


 
# TRANSFER CURVE


- For an SRAM bit cell, the transfer curve is also called as “Butterfly diagram”




- Now that we have sized the MOS, if we plot the butterfly of the back-to-back inverter, we get a plot similar to the one above
- However, we now have a series access transistor  $\rightarrow$  what is the impact of that?
- Let us look at the noise margin during read
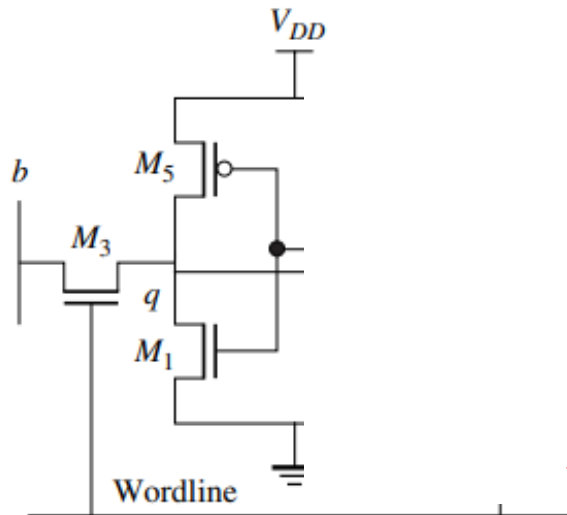
# STATIC READ NOISE MARGIN (SNM)




- ❑ Before a read, the bitlines are pre-charged to  $V_{DD}$
- ❑ Similar to an inverter, we sweep the input of the inverter from 0 to  $V_{DD}$  (to plot the transfer curve)
  - ❑ But, with bit line at  $V_{DD}$  and WL at  $V_{DD}$
- ❑ When input to the inverter is 0, output will be at  $V_{DD}$  → no issues
- ❑ When input to the inverter is  $V_{DD}$ , both  $M_1$  and  $M_3$  are ON
  - ❑ Even though  $M_1$  is stronger than  $M_3$ , the node  $q$  will never really reach 0 V !!! → the transfer curve of this combination (during read) will be different than that of only inverter



Voltages never go to zero

 


# READ SNM

   

- ❑ Addition of access transistors → reduced the noise margin (compared to inverter)
- ❑ To avoid read destruction → Static Noise Margin (SNM) must be increased
- ❑ Bigger the box you can fit inside the two transfer curves → better SNM !
- ❑ Design: start with the initial W values → keep optimizing to increase SNM
- ❑ But remember → entire idea behind SRAM is to reduce the area → we cannot size MOSFETs beyond a certain limit!



# SRAM: FULL PICTURE

 


- ❑ We have looked at the Row decoder (logical effort design)
- ❑ Looked at design of individual bit-cell
- ❑ Next, we will look at the pre-charge circuit, column decoders, sense amplifiers


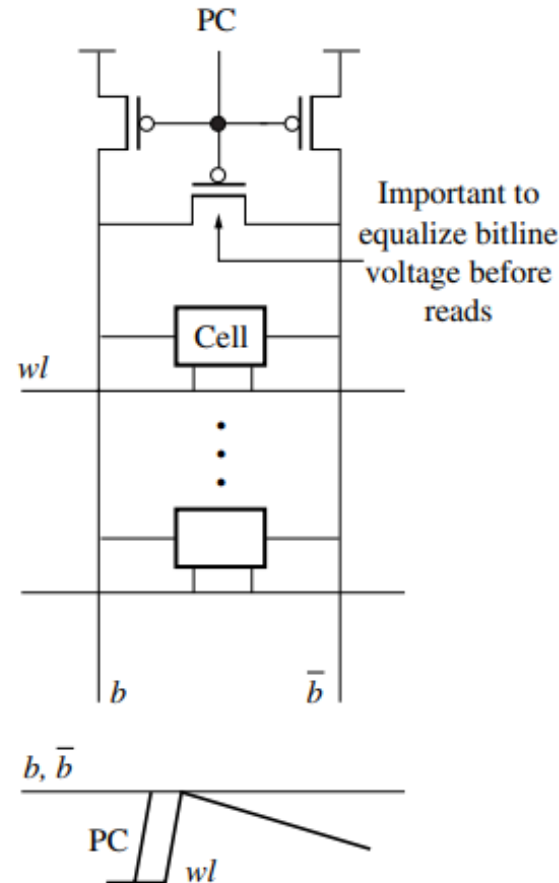
# COLUMN PULL-UPS: PRE-CHARGE

- ❑ To remove all history → perform pre-charge before every read and write
- ❑ The nature of pre-charge (PC) circuit depends on the amplification (also called sense amplifier (SA)) topology



Suitable for voltage based amplifiers

## ❑ Sequence:

- ❑ PC is low by default (Pre-charging bit lines)
- ❑ PC goes high
- ❑ After some finite time → WL goes high
- ❑ Read operation starts
- ❑ Bitlines start developing delta voltage
- ❑ Sense amplifier (SA) enabled after finite time to amplify this delta voltage
- ❑ Once logic levels are obtained at the output, disable WL, SA and enable PC

