 


## Lecture-2




Scaling of FETs in CMOS process:-

- 1) The No of MOSFETs on a chip  $\propto \frac{1}{WL} \Rightarrow$  Scales as  $k \times k = \boxed{k^2}$
- 2) The speed of MOSFETs  $\propto \frac{1}{L} \Rightarrow$  Scales as  $\boxed{k}$  Speed  $\uparrow k$
- 3) Gate-oxide capacitance,  $C = \frac{\epsilon A}{d} = \frac{\epsilon WL}{t_{ox}} \Rightarrow \propto \frac{k \times k}{k} \Rightarrow$  scales as  $\boxed{\frac{1}{k}}$  Gate cap  $\downarrow k$

 
4) Energy:-

\* Consider a switching circuit using CMOS



 a) When  $IN = \text{Logic-0}$ , PMOS  $\rightarrow$  ON & NMOS OFF.  
Acting like switches

Any 'ON' switch has a finite resistance & the equivalent model.



The energy supplied by the source is computed by integrating source power

$$i.e. \quad E_{\text{source}} = \int_0^{\infty} V_{DD} \cdot I(t) dt$$

For a switching RC circuit,  $I(t) = \frac{V_{DD}}{R} \left[ e^{-t/\tau_{RC}} \right]$

[ Assuming zero charge on C initially  
 i.e. cap was discharged previously ]

$$\therefore E_{\text{source}} = V_{DD} \cdot \frac{V_{DD}}{R} \int_0^{\infty} (e^{-t/\tau_{RC}}) dt$$

$$= \frac{V_{DD}^2}{R} e^{-t/\tau_{RC}} \Big|_0^{\infty} (-\tau_{RC}) = \boxed{V_{DD}^2 C}$$

Energy from source


$$= \frac{V_{DD}^2}{R} e^{-t/RC} \Big|_0 = \boxed{V_{DD}^2 C}$$

Energy from source

The energy stored on a capacitor is  $\boxed{\frac{1}{2}CV^2}$  Energy on cap

$\Rightarrow \frac{1}{2}CV^2$  is lost on the resistor (Dissipated as heat)

 \* Now consider the case when input is logic high and the cap was previously charged to  $V_{DD}$  by the PMOS switch. The equivalent model is:-



At the end of this, the total charge on the capacitor is zero (i.e.,  $V_o$  is 0, & the cap is fully discharged, i.e. logic-low output)


Since all the charges on the capacitor are lost, the energy of cap ( $\frac{1}{2}CV^2$ ) must be dissipated on the resistor.

$\therefore \frac{1}{2}CV^2$  is lost on the resistor, this time on the NMOS side!!  
(dissipated as heat)

\* At the end of the operation, a total of  $CV^2$  ( $\frac{1}{2}CV^2$  on PMOS side &  $\frac{1}{2}CV^2$  on NMOS) energy is lost/dissipated in the circuit [this energy is provided by the supply  $V_{DD}$ ]

$\therefore$  Energy dissipation  $\rightarrow \propto CV^2$

 \* Usually in a digital circuit every gate sees another gate as a load



$\therefore C$  is approximately same as the gate capacitance we computed and scales as  $1/K$ .

\* As we scale technology, the same Electric field can be maintained for the same performance as previous technology node

$$\text{Electric field (to create channel)} = \frac{V_{DD}}{t_{ox}}$$

Since  $t_{ox} \downarrow K$ ,  $V_{DD}$  can also be  $\downarrow K$

$\Rightarrow$  Inherent assumption that  $V_{TH}$  of MOSFETs also scale down (not proportionally) with technology.

with technology.

\* We go back to discussion on energy.

Energy dissipated is  $CV^2$ ,  $C \propto 1/K$  and  $V \propto 1/K$

$$\Rightarrow \text{Energy dissipated} \propto \boxed{1/K^3}$$

Energy dissipated  $\downarrow K^3$

5)  $\text{Power} = \frac{\text{Energy}}{\text{Time}}$

\* Assuming that the NMOS & PMOS (in our circuit above) are periodically switching with period  $T$  (or frequency  $f$ ),

$$\text{Power dissipated} = \frac{CV^2}{T} = CV^2 f.$$

\* In a digital circuit there are plenty of gates/flip-flops etc which are NOT all switching at the same time. We define an average switching factor called, activity factor ( $\alpha$ ) to compute average power consumption

$$\therefore P_{\text{diss}} = \overset{\alpha}{\downarrow} \propto CV^2 f$$

$$\therefore \text{Power dissipated} \propto \left. \begin{array}{ccc} \overset{\text{proportional}}{\downarrow} C & V_{\text{DD}}^2 & f \\ \downarrow & \downarrow & \downarrow \\ \propto 1/K & \propto 1/K^2 & \propto K \end{array} \right\} \Rightarrow P_{\text{dissipated}} \propto \boxed{1/K^2}$$

Power dissipation  $\downarrow K^2$  with scaling

i.e. For same functionality on chip, the power dissipation/heating of a digital IC  $\downarrow K^2$  with technology scaling

6) Power density.

with scaling, power dissipation  $\downarrow K^2$  &

$\nearrow$  More functionality on a chip  
 $\boxed{\text{No of transistors} \uparrow K^2}$

$$\Rightarrow \text{Power density} = \frac{1}{K^2} \times K^2 = \boxed{1}$$

Implying with scaling, the functionality can be increased on a chip with no additional power/heat dissipation !!

\* While these are true for traditional CMOS technology, below 65nm node,

(a) The  $V_{\text{DD}}$  does NOT scale down as  $K$

(b) Due to reduced control over the channel with scaling, the leakage current ↑ and adds more power dissipation.






Single Chip (Die)

Cross Section

goes to outside world


Metal 2

Via 1

Metal 1

MUSPETS are at the bottom

- \* Metals (used as wires) are used for signal & supply connections.


 package  
 chip/die  
 wirebond  
 PAD

PAD talks to outside world

below:-

\* The thickness of metal or any other layer is fixed for a process & not a design variable.

This is because the metals have finite routing (or wire) resistance

connected to highest metal and it has to distribute current to MOSFETs at lowest metal)

— x — x —————

This is due to what can be & cannot be fabricated in the foundry for a given technology.

Each process technology has a specific set of design rules to be strictly adhered to  
 This is due to what can be & cannot be fabricated in the foundry for a given technology

Table 3 Table 2 - Minimum CDs in Design or on Wafer, required by Technology

Layer Name	Feature Size	Space Size
Metal 1	0.14	0.14
Metal 1 - Cu	0.14	0.14
Via	0.15	0.17
Via - Cu	0.18	0.13
Capacitor MIM	2	0.84
Metal 2	0.14	0.14
Metal 2 - Cu	0.14	0.14
Via 2-TNV	0.28	0.28

→ Example design rule specification for CMOS 130nm Skywater.

→ Spacing between 2 metal-1 layers (space bit routes)

→ Minimum width of metal-1 layer (wire width can be higher than this but not lower)

→ Spacing between 2 via-1's (via-1 connects metal 1 to metal 2)

→ Minimum size of via-1

∴ etc for other layers

← checks all the design rules like there are not violated

\* Before chip fabrication a DRC (Design Rule Check) is performed before submitting the final design files to the foundry for fabrication