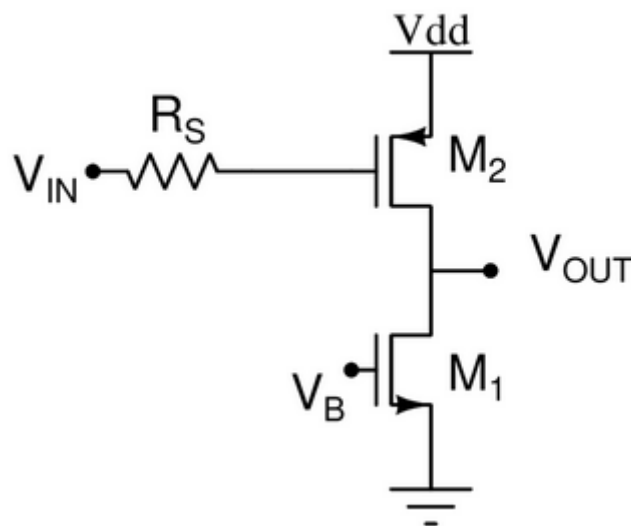


EE618 (ZELE)


CMOS ANALOG VLSI DESIGN

Question Bank

- 1) In this circuit shown, $R_S = 1\text{k}\Omega$ and both the transistors are identical. Assume the parasitic capacitances have the same values for both the transistors. $I_{d1} = I_{d2} = 1\text{mA}$, $C_{GS} = 250\text{fF}$, $C_{GD} = 80\text{fF}$, $g_{m2} = 1\text{mS}$, $\lambda_n = 0.1\text{V}^{-1}$, $\lambda_p = 0.2\text{V}^{-1}$. Consider channel length modulation. Find **input pole frequency** in **MHz**. Two decimal point accuracy is expected. ($1\text{M} = 10^6$)




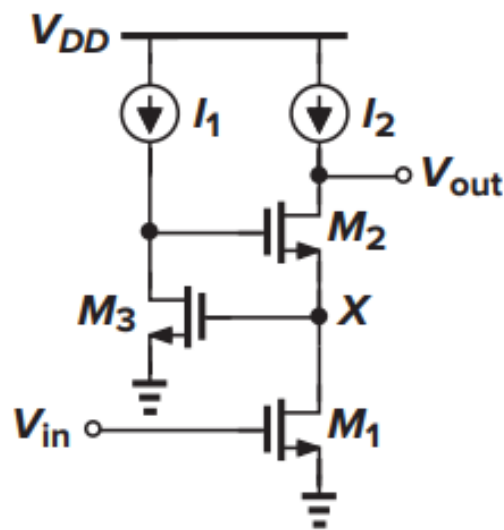2) Calculate the voltage gain A_v for the below circuit.




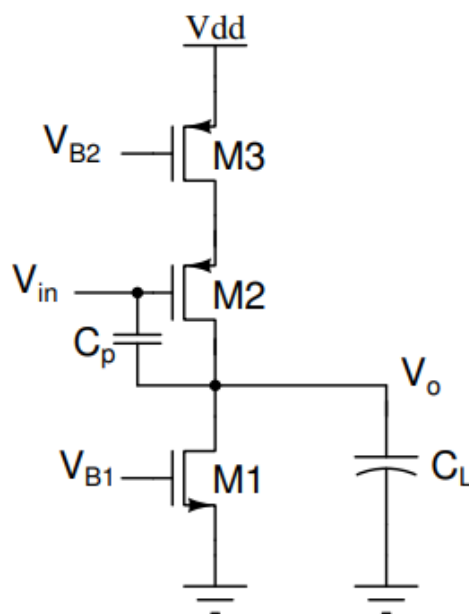3) All transistors have same g_m and g_{ds} . $g_m \gg 2 g_{ds}$. Ignore body effect and transistor capacitances.

- Calculate the DC gain.
- Derive the expression for transfer function (frequency response).
- Draw the bode plot for both magnitude and phase.



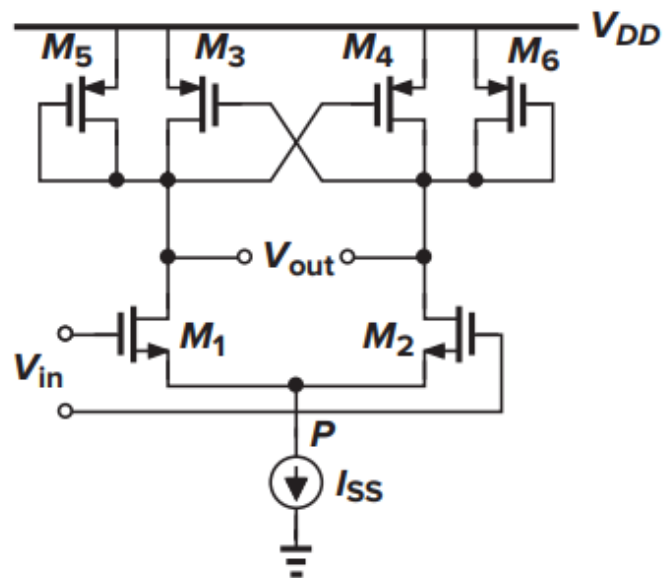4) Calculate input referred thermal noise voltage for below circuit.



5) Calculate input referred thermal noise voltage for below circuit.

