
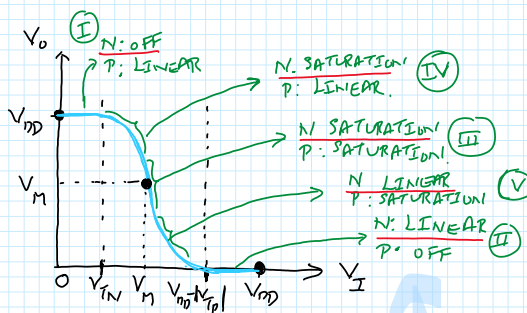

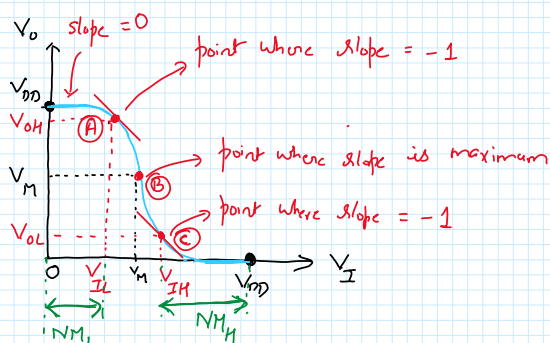
## Additional Notes on Noise Margin - (Not covered in the class)

\* We try to detail more on the Noise Margin mathematically. The notes as self explanatory & will not be covered in class.



\* We refer to the Lecture-5 notes for the Inverter transfer characteristics

\* Based on our discussion, At point (A), slope = -1,

Also, in region (A), NMOS is in saturation & PMOS is in linear (IV)

$$\text{Equate } I_{D,N} = I_{D,P} \text{ for solutions}$$

\* To find  $V_O$  ( $I_{D,N} = I_{D,P}$ )

$$\frac{1}{2} K_N [V_I - V_{TN}]^2 = K_P [(V_{DD} - V_I - |V_{TP}|)(V_{DD} - V_O) - \frac{(V_{DD} - V_O)^2}{2}]$$

\* Substitute  $V_x = V_{DD} - V_O$

$$\frac{1}{2} [V_I - V_{TN}]^2 = [2(V_{DD} - V_I - |V_{TP}|)V_x - V_x^2]$$

$$\dots V_x^2 - 2V_x(V_{DD} - V_I - |V_{TP}|) + \frac{(V_I - V_{TN})^2}{2} = 0$$

$$\dots V_x = \left[ 2(V_{DD} - V_I - |V_{TP}|) \pm \sqrt{4(V_{DD} - V_I - |V_{TP}|)^2 - \frac{(V_I - V_{TN})^2}{2}} \right] \times \frac{1}{2}$$

$$= (V_{DD} - V_I - |V_{TP}|) \pm \sqrt{(V_{DD} - V_I - |V_{TP}|)^2 - \frac{(V_I - V_{TN})^2}{2}}$$

$$\therefore V_O = V_I + |V_{TP}| + \sqrt{(V_{DD} - V_I - |V_{TP}|)^2 - \frac{(V_I - V_{TN})^2}{2}}$$

Not a solution.

$$\therefore V_O = V_I + |V_{TP}| + \sqrt{(V_{DD} - V_I - |V_{TP}|)^2 - \frac{(V_I - V_{TN})^2}{2}}$$

Re writing

$$V_O = V_I + |V_{TP}| + \sqrt{[(V_{DD} - V_I - |V_{TP}|) + \frac{(V_I - V_{TN})}{2}][V_{DD} - V_I - |V_{TP}| - \frac{(V_I - V_{TN})}{2}]} \quad (1)$$

To obtain  $V_{IL}$ ,  $\frac{\partial V_O}{\partial V_I} = -1$  (i.e. slope = -1)

$$\frac{\partial V_o}{\partial V_i} = 1 + \frac{\left[ (V_{DD} - V_i - |V_{TP}|) + (V_i - V_{TN})/\beta \right] \left[ -1 - 1/\beta \right] + \left[ V_{DD} - V_i - |V_{TP}| - (V_i - V_{TN})/\beta \right] \left[ -1 + 1/\beta \right]}{2 \left[ \left[ (V_{DD} - V_i - |V_{TP}|) + (V_i - V_{TN})/\beta \right] \left[ (V_{DD} - V_i - |V_{TP}|) - (V_i - V_{TN})/\beta \right] \right]} = -1$$

After simplification,

$$4V_i^2 \beta (\beta_{th}) + 8V_i (\beta_{th}) \left[ V_i - V_{TN}/\beta \right] - 12V_i^2 - \frac{8V_{TN}V_i}{\beta^2} + \frac{4V_{TN}^2}{\beta^2} \left( \frac{1}{\beta^2} + 1 \right) = 0$$

where,  $V_i = V_{DD} - |V_{TP}|$  and  $\beta = \frac{(1-\beta^2)}{\beta^2}$

$$\therefore V_i = V_{IL} = \frac{V_{TN}^2 \left[ \frac{1}{\beta^2} + 1 \right] / \beta^2 - 2V_{TN}(V_{DD} - |V_{TP}|) / \beta^2 - 3(V_{DD} - |V_{TP}|)^2}{- (\beta_{th}) [V_{DD} - |V_{TP}| - V_{TN}/\beta^2] \pm \sqrt{(\beta_{th})^2 [V_{DD} - |V_{TP}| - V_{TN}/\beta^2]^2 - \beta(\beta_{th}) \left[ \frac{V_{TN}^2 (\frac{1}{\beta^2} + 1)}{\beta^2} - \frac{2V_{TN}(V_{DD} - |V_{TP}|)}{\beta^2} - 3(V_{DD} - |V_{TP}|)^2 \right]}}$$

\* Under the special case,  $\beta = 1$  ( $\beta = \frac{1-\beta^2}{\beta^2} = 0$ )

$$V_{IL} = \frac{5V_{TN}^2 - 2V_{TN}(V_{DD} - |V_{TP}|) - 3(V_{DD} - |V_{TP}|)^2}{-4[(V_{DD} - |V_{TP}|) - V_{TN}] \pm 4[V_{DD} - |V_{TP}| - V_{TN}]}$$

with  $\beta = 1$ , the quadratic equation collapses to a linear eq<sup>n</sup> & there is only one solution

$$\therefore V_{IL} = \frac{3(V_{DD} - |V_{TP}|)^2 + 2V_{TN}(V_{DD} - |V_{TP}|) - 5V_{TN}^2}{8[(V_{DD} - |V_{TP}|) - V_{TN}]}$$

$$= \frac{[3(V_{DD} - |V_{TP}|) + 5V_{TN}][V_{DD} - |V_{TP}| - V_{TN}]}{8[(V_{DD} - |V_{TP}|) - V_{TN}]}$$

$$\therefore V_{IL} = \frac{3V_{DD} - 3|V_{TP}| + 5V_{TN}}{8}$$

\* Substituting the  $V_{IL}$  in (1) to get  $V_{OH}$ , we get

$$V_{OH} = \frac{7V_{DD} + V_{TN} + |V_{TP}|}{8} = V_{DD} - \frac{V_{DD} - (V_{TN} + |V_{TP}|)}{8}$$

\* Under the condition,  $\beta = 1$  and  $V_{TN} = |V_{TP}| = V_T$

$$V_{IL} = \frac{3V_{DD} + 2V_T}{8} \quad \text{and} \quad V_{OH} = \frac{7V_{DD} + 2V_T}{8}$$

\* Now, shift focus to  $V_{IH}$

\* Based on our discussion, At point (C), slope = -1,

Also, in region (C), PMOS is in saturation & NMOS is in linear (C) in the transfer curve

i.e.  $T_1 - T$  low solution

Also, in region (C), PMOS is in saturation & NMOS is in linear [V in the transfer curve]

Equation  $I_{D,N} = I_{D,P}$  for solution

\* To find  $V_O$  ( $I_{D,N} = I_{D,P}$ )

$$\frac{1}{2} K_N [V_I - V_{TN}]^2 = K_P [(V_{DD} - V_I - |V_{TP}|)(V_{DD} - V_O) - \frac{(V_{DD} - V_O)^2}{2}]$$

\* Substitute  $V_x = V_{DD} - V_O$

$$K_N [(V_I - V_{TN})V_O - \frac{V_O^2}{2}] = \frac{1}{2} K_P [(V_{DD} - V_I - |V_{TP}|)^2]$$

$$2(V_I - V_{TN})V_O - V_O^2 = \delta^2 [V_{DD} - V_I - |V_{TP}|]^2$$

$$V_O^2 - 2V_O(V_I - V_{TN}) + \delta^2 [V_{DD} - V_I - |V_{TP}|]^2 = 0$$

$$\therefore V_O = \frac{2(V_I - V_{TN}) \pm \sqrt{4(V_I - V_{TN})^2 - 4\delta^2 [V_{DD} - V_I - |V_{TP}|]^2}}{2}$$

$$V_O = (V_I - V_{TN}) \pm \sqrt{(V_I - V_{TN})^2 - \delta^2 [V_{DD} - V_I - |V_{TP}|]^2}$$

Rewrite  $V_O = (V_I - V_{TN}) - \sqrt{[V_I - V_{TN} + \delta(V_{DD} - |V_{TP}| - V_I)][V_I - V_{TN} - \delta(V_{DD} - |V_{TP}| - V_I)]}$  — (2)

To obtain  $V_{IH}$ ,  $\frac{\partial V_O}{\partial V_I} = -1$  (i.e. slope = -1)

(You can solve this yourself)

Under the special case of  $\delta = 1$

$$V_{IH} = \frac{5V_{DD} + 3V_{TN} - 5|V_{TP}|}{8}$$

\* Substituting  $V_{IH}$  in (2) to get  $V_{OL}$ , we get

$$V_{OL} = \frac{V_{DD} - (V_{TN} + |V_{TP}|)}{8}$$


\* Under the condition,  $\delta = 1$  and  $V_{TN} = |V_{TP}| = V_T$


$$V_{IH} = \frac{5V_{DD} - 2V_T}{8} \quad \text{and} \quad V_{OL} = \frac{V_{DD} - 2V_T}{8}$$

\* Re-evaluate Noise Margin


\* In the class, we discussed  $NM_H$  &  $NM_L$  as
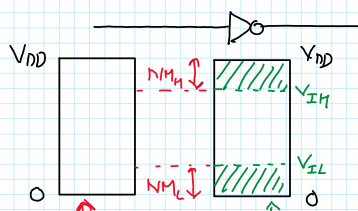
$$NM_H = V_{DD} - V_{IH} \quad \& \quad NM_L = V_{IL} - 0 \quad \text{considering a single inverter.}$$



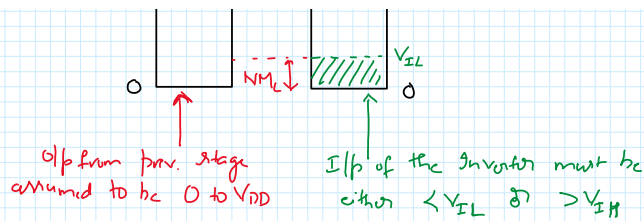

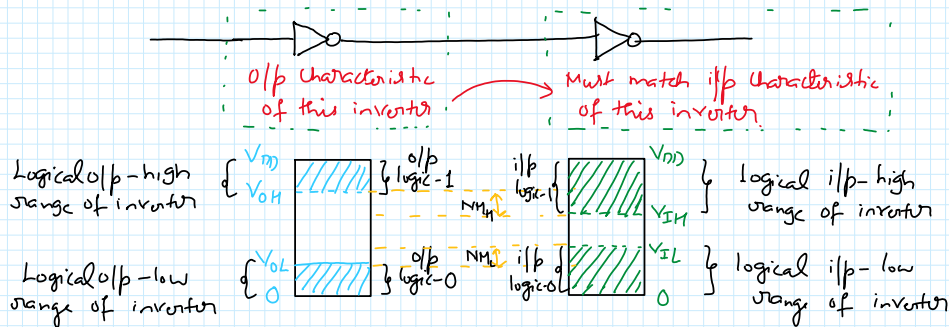\* But practically, each inverter drives another inverter (or other logic)



\* The next stage inverter will consider any voltage below  $V_{IL}$  @ its input as logic-low & will consider any voltage above  $V_{IH}$  @ its input as logic-high.

\* The previous stage can o/p any voltage between  $V_{DD}$  &  $V_{OH}$  as output-high (depending on its i/p) & it can o/p any voltage between  $0$  &  $V_{OL}$  as output-low (depending on its i/p)

\* When the previous stage outputs  $V_{OH}$  as o/p (it is still a valid logic-high voltage), the amount of margin we have for the noise is reduced (i.e. an addition of noise can make the i/p to the next inverter below  $V_{IH}$  or  $(V_{OH} - \text{Noise}) < V_{IH}$ , leading to wrong o/p).

∴ The worst case Noise margins are

$$NM_H = V_{OH} - V_{IH}$$

$$\& \quad NM_L = V_{IL} - V_{OL}$$

Best case:-

$$NM_H = V_{DD} - V_{IH}$$

$$NM_L = V_{IL} - 0$$

\* For the special case of  $\beta = 1$

$$NM_H = V_{OH} - V_{IH}$$

$$= \frac{7V_{DD} + 4|V_{TP}| + V_{TN}}{8} - \left( \frac{5V_{DD} - 5|V_{TP}| + 3V_{TN}}{8} \right)$$

$$= \frac{2V_{DD} + 6|V_{TP}| - 2V_{TN}}{8}$$

$$\therefore NM_H = \frac{V_{DD} + 3|V_{TP}| - V_{TN}}{4}$$

$$NM_L = V_{IL} - V_{OL}$$

$$= \frac{3V_{DD} - 3|V_{TP}| + 5V_{TN}}{8} - \left( \frac{V_{DD} - |V_{TP}| - V_{TN}}{8} \right)$$

$$= \frac{2V_{DD} - 2|V_{TP}| + 6V_{TN}}{8}$$

$$\therefore NM_L = V_{DD} - |V_{TP}| + 3V_{TN}$$

$$\therefore NM_L = \frac{V_{DD} - |V_{TP}| + 3V_{TN}}{8}$$

\* Under the special case,  $\beta=1$  &  $V_{TN} = |V_{TP}| = V_T$

$$NM_H = \frac{V_{DD} + 2V_T}{4} \quad \& \quad NM_L = \frac{V_{DD} + 2V_T}{4}$$

Summary of static parameters:

Parameter	$\beta=1$	$\beta=1$ and $V_{TN} =  V_{TP}  = V_T$
$V_M$	$\frac{V_{DD} -  V_{TP}  + V_{TN}}{2}$	$V_{DD}/2$
$V_{IL}$	$\frac{3V_{DD} - 3 V_{TP}  + 5V_{TN}}{8}$	$(3V_{DD} + 2V_T)/8$
$V_{IH}$	$\frac{5V_{DD} - 5 V_{TP}  + 3V_{TN}}{8}$	$(5V_{DD} - 2V_T)/8$
$V_{OH}$	$V_{DD} - \frac{V_{DD} -  V_{TP}  - V_{TN}}{8}$	$(7V_{DD} + 2V_T)/8$
$V_{OL}$	$\frac{V_{DD} -  V_{TP}  - V_{TN}}{8}$	$(V_{DD} - 2V_T)/8$
$NM_H$	$\frac{V_{DD} + 3 V_{TP}  - V_{TN}}{4}$	$(V_{DD} + 2V_T)/4$
$NM_L$	$\frac{V_{DD} -  V_{TP}  + 3V_{TN}}{4}$	$(V_{DD} + 2V_T)/4$