
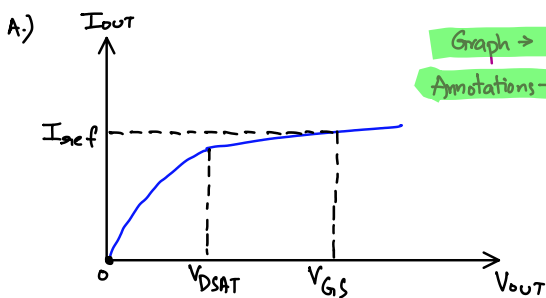


EE618 Quiz 1 Solutions

Q1.) Given: M_1 & M_2 are identical

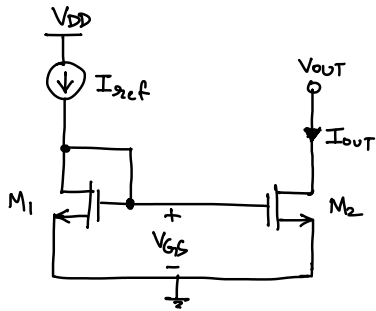

B.) given: $V_{OUT} = V_{DSAT} = V_{GS} - V_{TN}$

$$\text{from } M_1 : I_1 = I_{ref} = \frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_{TN}]^2 (1 + \lambda V_{GS}) \quad (1)$$

$$\text{from } M_2 : I_2 = I_{OUT} = \frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_{TN}]^2 (1 + \lambda V_{DSAT}) \quad (2)$$

\rightarrow 1 mark

$$(2) - (1) \Rightarrow I_{OUT} - I_{ref} = \left(\frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_{TN}]^2 \right) \lambda (V_{DSAT} - V_{GS})$$

$$= \left(\frac{I_D}{1 + \lambda V_{DS}} \right) \lambda (V_{DSAT} - V_{GS})$$


$$= \left(\frac{1}{g_{m0}} \right) (V_{DSAT} - V_{GS})$$

$$\Rightarrow \Delta I_{OUT} = I_{OUT} - I_{ref} = \frac{V_{DSAT} - V_{GS}}{g_{m0}}$$

\rightarrow 1 mark

ALTERNATE SOLUTION:

from the graph

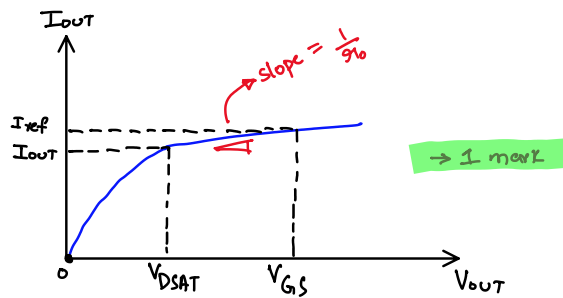

wkt $\text{slope} = g_o = \frac{1}{r_o}$

$$\Rightarrow \frac{1}{r_o} = \frac{\Delta y}{\Delta x} = \frac{I_{ref} - I_{out}}{V_{GS} - V_{DSAT}} \quad \rightarrow 1 \text{ mark}$$

$$\Rightarrow \Delta I_{OUT} = I_{OUT} - I_{ref} = \frac{V_{DSAT} - V_{GS}}{r_o}$$

C.) given:

$$V_{OUT} = V_{DSAT} = 0.2 \text{ V} \quad I_{ref} = 0.2 \text{ mA}$$

$$V_{TN} = 0.45 \text{ V} \quad r_o = 45 \text{ k}\Omega$$

$$V_{DSAT} = V_{GS} - V_{TN}$$

$$\Rightarrow V_{GS} = V_{DSAT} + V_{TN} = 0.65 \text{ V} \quad \rightarrow 0.5 \text{ marks}$$

$$\begin{aligned} \Delta I_{OUT} &= \frac{V_{DSAT} - V_{GS}}{r_o} = \frac{-0.45}{45 \text{ k}} \\ &= -10.4 \mu\text{A} \quad \rightarrow 1 \text{ mark} \end{aligned}$$


$$\begin{aligned} I_{OUT} &= I_{ref} + \Delta I_{OUT} = 190 \mu\text{A} \\ &= 0.19 \text{ mA} \quad \rightarrow 0.5 \text{ marks} \end{aligned}$$

D.)

Drawback: R_{out} of this current source is not very high.


$$(R_{out} = r_o) \quad \rightarrow 0.5 \text{ marks}$$

Modified schematic: (Use a cascode)

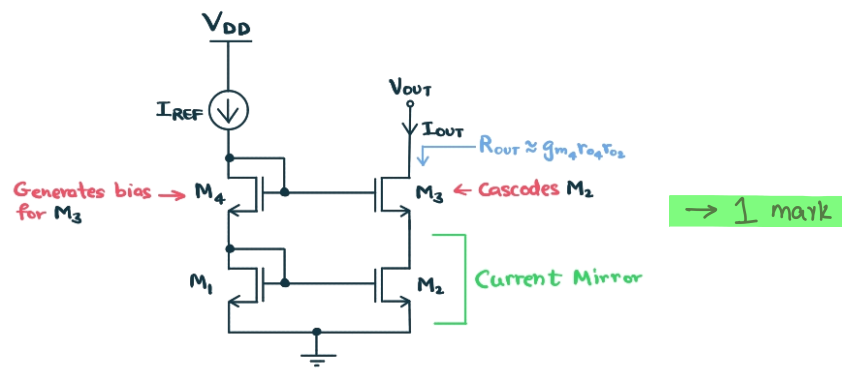

Trade-off: Voltage required at V_{OUT} to keep M_2 & M_3 in saturation is higher now. $\rightarrow 0.5$ marks

Q2]

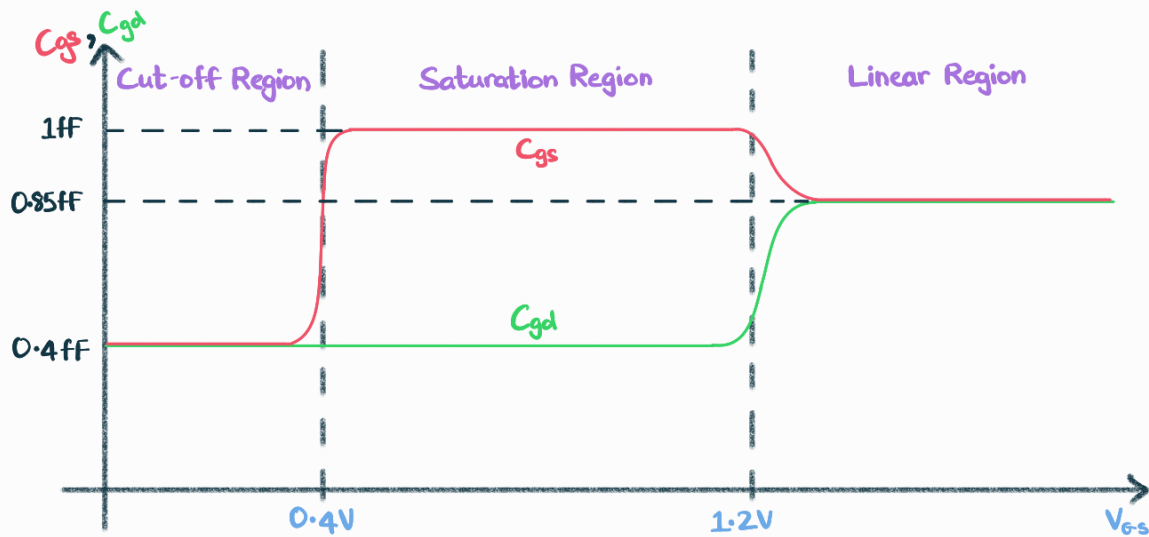

Cut-off region

$$C_{gd} = C_{ov} W = 0.4 \text{ fF}$$

— 0.5 mrks

$$C_{gs} = C_{ov} W = 0.4 \text{ fF}$$

— 0.5 mrks

Saturation region

$$C_{gd} = C_{ov} W = 0.4 \text{ fF}$$

— 0.5 mrks

$$C_{gs} = \frac{2}{3} W L C_{ox} + C_{ov} W = 1 \text{ fF}$$

— 0.5 mrks

Linear/Triode/Non-sat region

$$C_{gd} = \frac{1}{2} W L C_{ox} + C_{ov} W = 0.85 \text{ fF}$$


— 0.5 mrks

$$C_{gs} = \frac{1}{2} W L C_{ox} + C_{ov} W = 0.85 \text{ fF}$$

— 0.5 mrks

Q3] a) Note: Devices shown in green are providing effective G_m

(a)

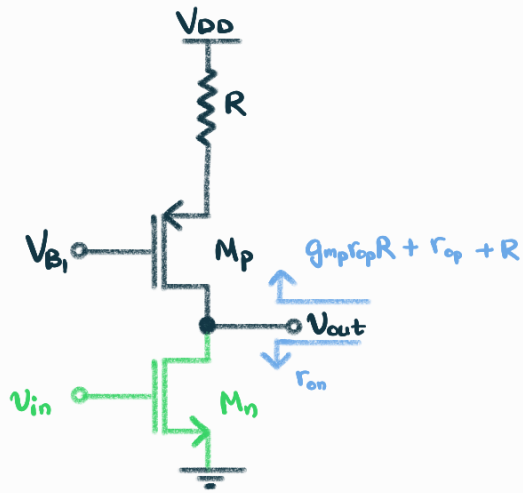

$$G_m = g_{mn}$$

— 0.5 mrks


$$R_{out} = r_{on} \parallel (g_{mp} r_{op} R + r_{op} + R)$$

— 0.5 mrks

$$A_v = -g_{mn} [r_{on} \parallel (g_{mp} r_{op} R + r_{op} + R)]$$

— 0.5 mrks

(b)

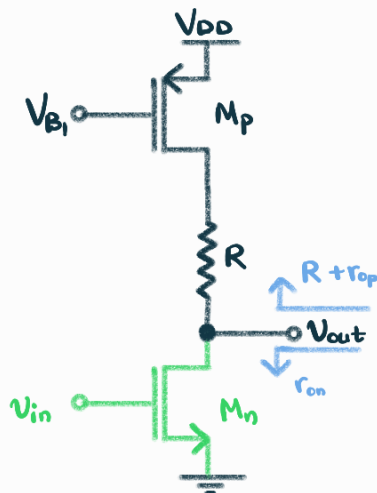

$$G_m = g_{mn}$$

— 0.5 mrks


$$R_{out} = r_{on} \parallel (R + r_{op})$$

— 0.5 mrks


$$A_v = -g_{mn} [r_{on} \parallel (R + r_{op})]$$

— 0.5 mrks

(c)

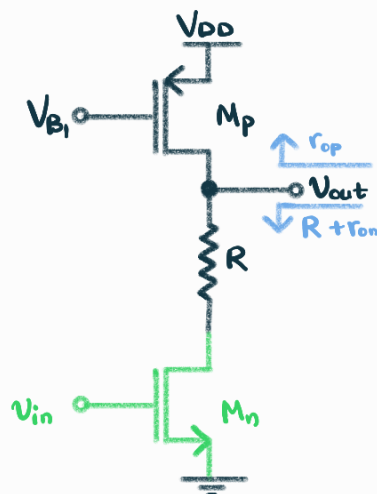

Calculating G_m

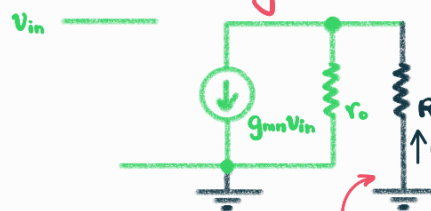

By Current Division

$$G_m V_{in} = g_{mn} V_{in} \left(\frac{r_{on}}{r_{on} + R} \right)$$

$$G_m = g_{mn} \left(\frac{r_{on}}{r_{on} + R} \right)$$

O/P shorted to GND

$$G_m = g_{mn} \left(\frac{r_{on}}{r_{on} + R} \right) \approx g_{mn}$$

— 0.5 mrks


$$R_{out} = r_{op} \parallel (R + r_{on})$$

— 0.5 mrks

$$A_v \approx -g_{mn} [r_{op} \parallel (R + r_{on})]$$

— 0.5 mrks

d)

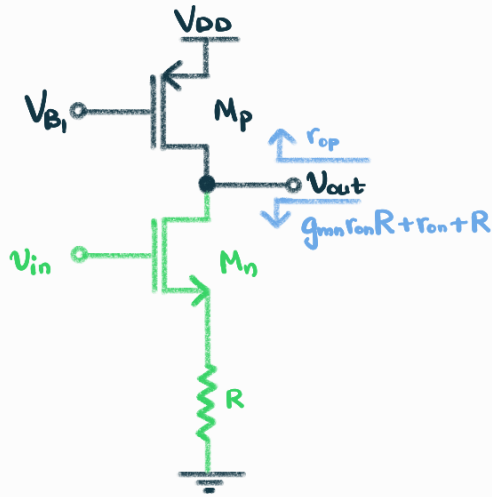

(Source Degeneration)

$$G_m = \frac{g_{mn} r_{on}}{r_{on} + R + g_{mn} r_{on} R} \approx \frac{g_{mn}}{1 + g_{mn} R} \quad - 0.5 \text{ mrks}$$

$$R_{out} = r_{op} \parallel (g_{mn} r_{on} R + r_{on} + R) \quad - 0.5 \text{ mrks}$$

$$A_v \approx - \frac{g_{mn}}{1 + g_{mn} R} [r_{op} \parallel (g_{mn} r_{on} R + r_{on} + R)] \quad - 0.5 \text{ mrks}$$

Q3] b) For $r_{op} = r_{on} = r_o$, $g_{mp} = g_{mn} = g_m$, $r_o \gg R$

$$|A_a| \approx g_m r_o$$

$$|A_b| \approx g_m r_o / 2$$

$$|A_c| \approx g_m r_o / 2$$

$$|A_d| \approx r_o / R$$

Descending Order

$$|A_a| > |A_b| = |A_c| > |A_d|$$


- 2 mrks

Only if order fully correct


Q4]

(a)

Output Characteristics

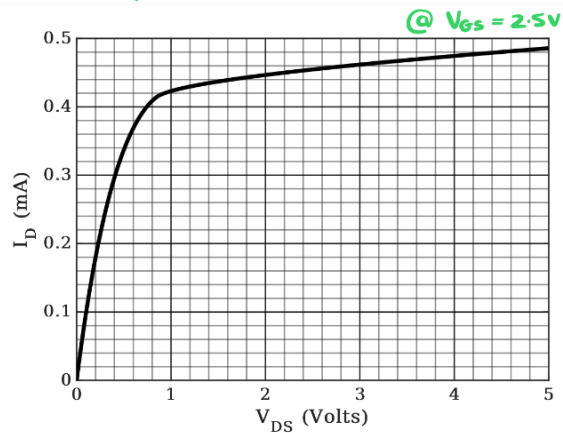


Transfer Characteristics

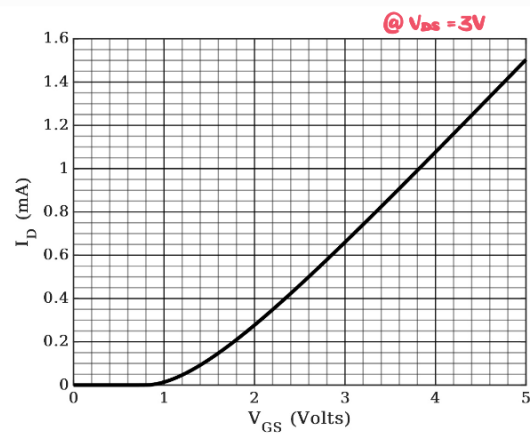

Clearly from the above plots, $I_D > 0$ for $V_{GS} > 0$ and $V_{DS} > 0$
 \therefore 'G' & 'D' at higher potential than 'S' \Rightarrow **NMOS** - 1 mrks

(b) For $V_{DS} = 3V$, $V_{GS} = 2.5V$:


I_D & r_o calculation:

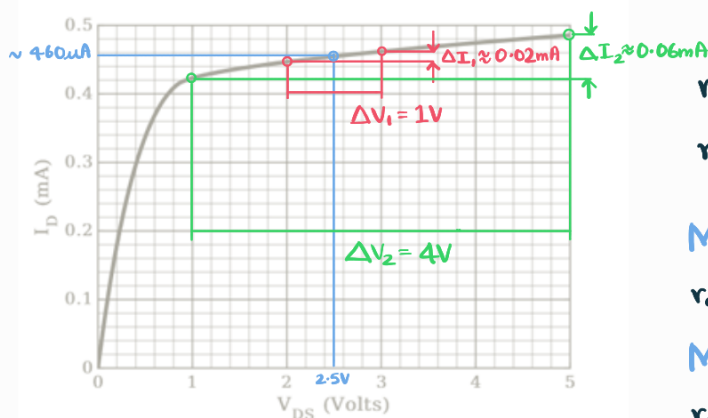


$r_o = 50K\Omega$ to $70K\Omega$

- 1 mrks

g_m calculation:

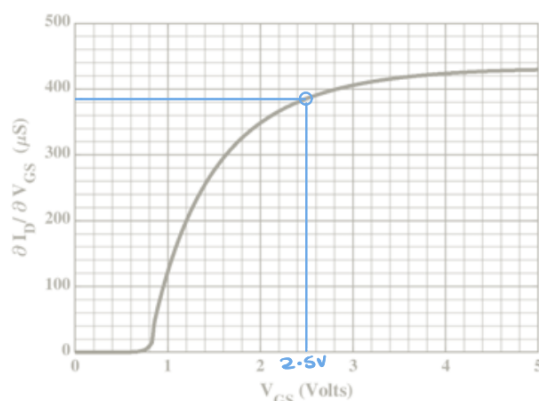

V_{TH} calculation:

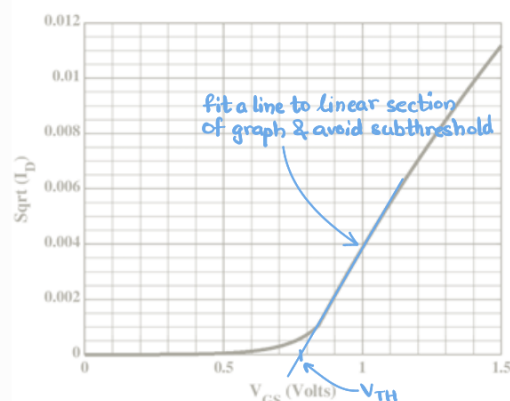

③ $r_o = \frac{1}{\lambda I_D} \Rightarrow \lambda = \frac{1}{r_o I_D}$ $I_D = 0.46 \text{ mA}$ @ $V_{GS} = 2.5 \text{ V}$, $V_{DS} = 3 \text{ V}$

$\lambda = 0.03 \text{ V}^{-1}$ to 0.045 V^{-1}

— 1 mrks

$\mu_n C_{ox} = \frac{I_D}{\frac{W}{2L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})}$ or $\mu_n C_{ox} = \frac{g_m}{\frac{W}{L} (V_{GS} - V_{TH}) (1 + \lambda V_{DS})}$

$\mu_n C_{ox} = 40 \mu\text{A/V}^2$ to $60 \mu\text{A/V}^2$

— 1 mrks

The End