

EE671: VLSI DESIGN

SPRING 2024/25




LAXMEESHA SOMAPPA
DEPARTMENT OF ELECTRICAL ENGINEERING
IIT BOMBAY
laxmeesha@ee.iitb.ac.in



LECTURE – 33

SRAM CONTINUED


READ SNM

   

- ❑ Addition of access transistors → reduced the noise margin (compared to inverter)
- ❑ To avoid read destruction → Static Noise Margin (SNM) must be increased
- ❑ Bigger the box you can fit inside the two transfer curves → better SNM !
- ❑ Design: start with the initial W values → keep optimizing to increase SNM
- ❑ But remember → entire idea behind SRAM is to reduce the area → we cannot size MOSFETs beyond a certain limit!



SRAM: FULL PICTURE

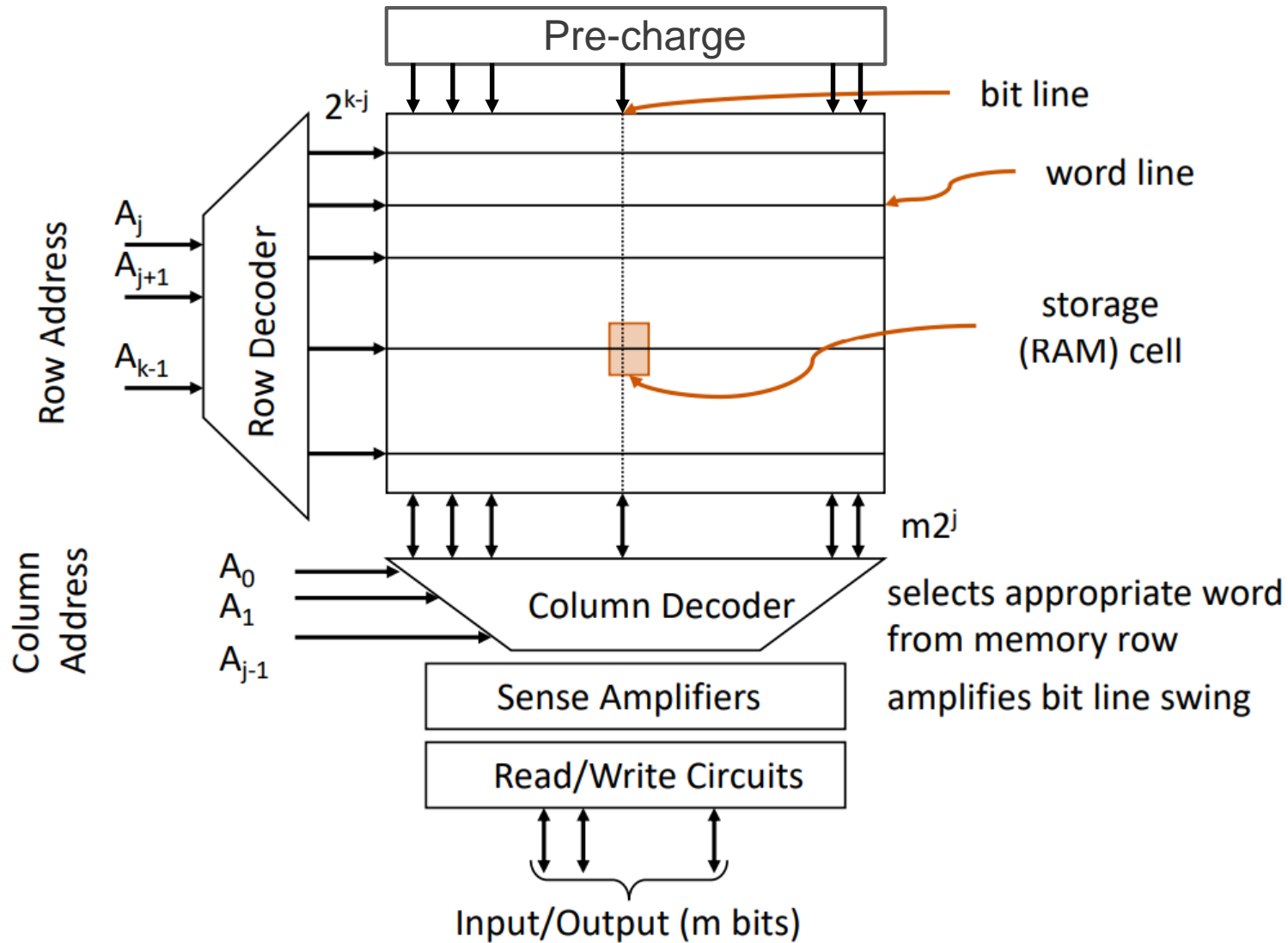


- ❑ We have looked at the Row decoder (logical effort design)
- ❑ Looked at design of individual bit-cell
- ❑ Next, we will look at the pre-charge circuit, column decoders, sense amplifiers



COLUMN PULL-UPS: PRE-CHARGE

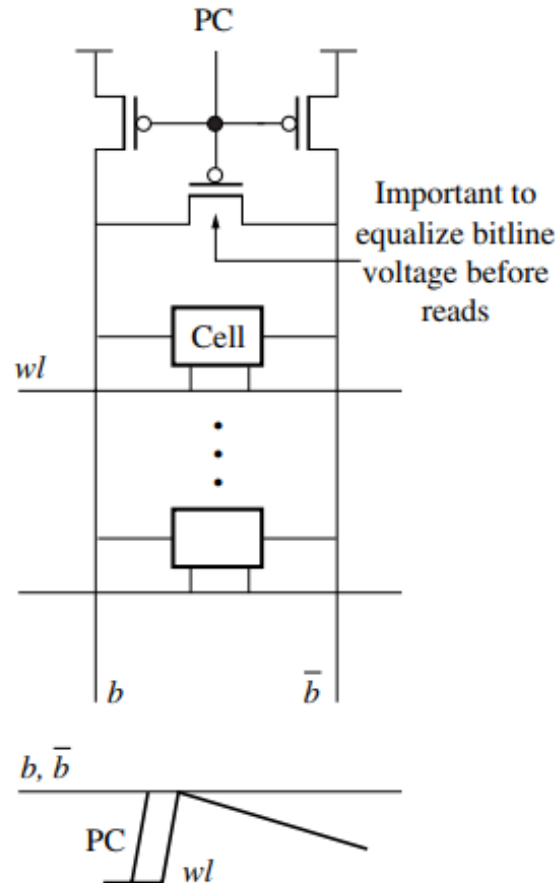- ❑ To remove all history → perform pre-charge before every read and write
- ❑ The nature of pre-charge (PC) circuit depends on the amplification (also called sense amplifier (SA)) topology



Suitable for voltage based amplifiers


❑ Sequence:

- ❑ PC is low by default (Pre-charging bit lines)
- ❑ PC goes high
- ❑ After some finite time → WL goes high
- ❑ Read operation starts
- ❑ Bitlines start developing delta voltage
- ❑ Sense amplifier (SA) enabled after finite time to amplify this delta voltage
- ❑ Once logic levels are obtained at the output, disable WL, SA and enable PC




COLUMN DECODER (COLUMN MUX)

 - ❑ After PC, the columns involved in read/write are to be enabled using MUX
- ❑ Usually this MUX is a simple TG (we looked at implementing MUX using TG earlier)





COLUMN DECODER (COLUMN MUX)

 - ❑ The read and write operation paths can be separated as shown below
- ❑ SA is enabled during read and write driver is enabled are enabled during write after selecting the required columns




COLUMN DECODER (COLUMN MUX)

  - Note that, during read all lines are V_{DD} (pre-charge), so we only really need PMOS devices during read operation
- During write, essentially, we are discharging bitlines to ground \rightarrow we need NMOS
- This automatically provides the enabling of read/write using the same column decoder





COMPLETE WRITE CIRCUIT (ONE COLUMN)

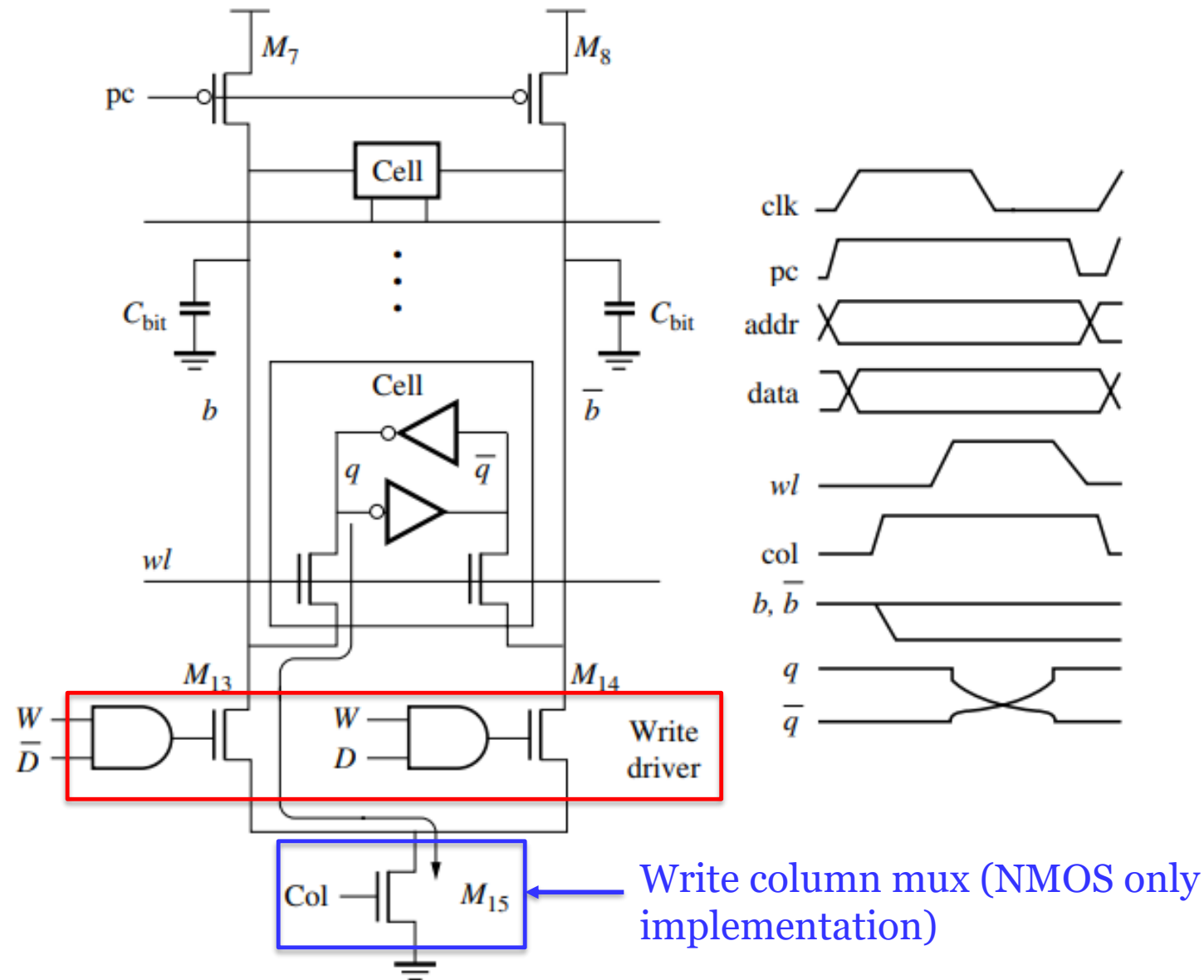




COMPLETE READ CIRCUIT (ONE COLUMN)

 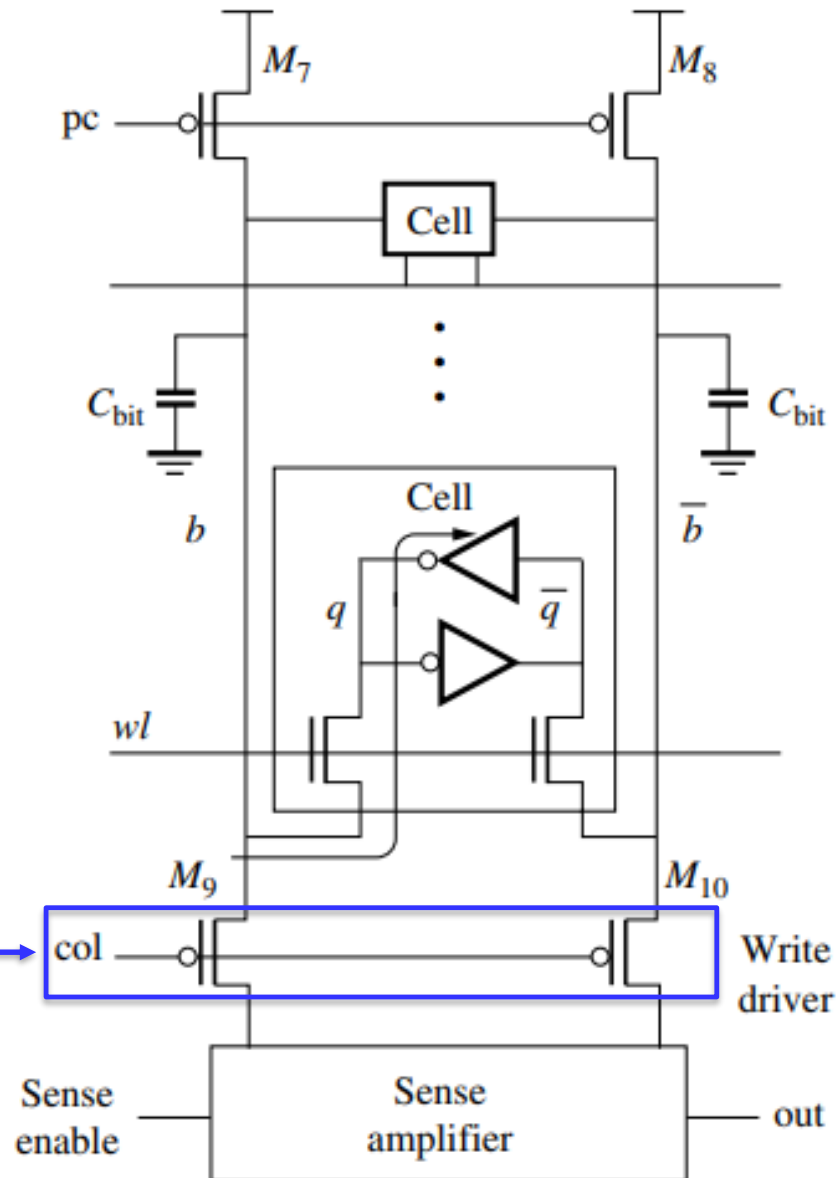Read column mux (PMOS only implementation)



SENSE AMPLIFIER

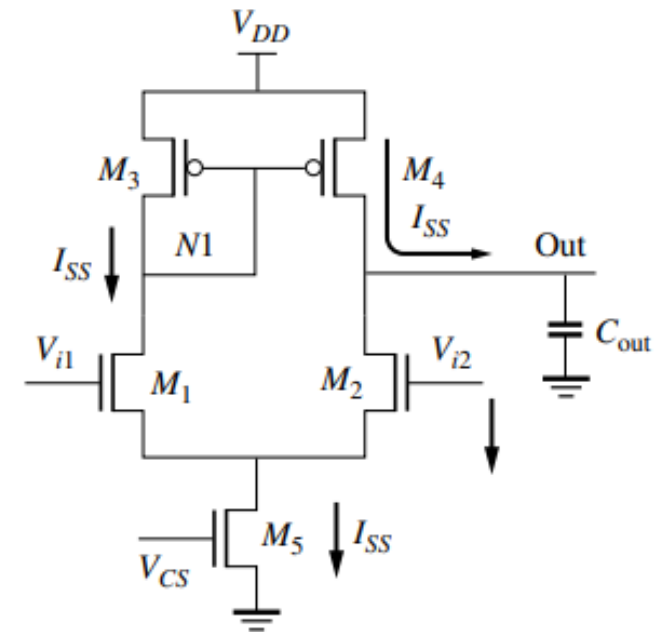 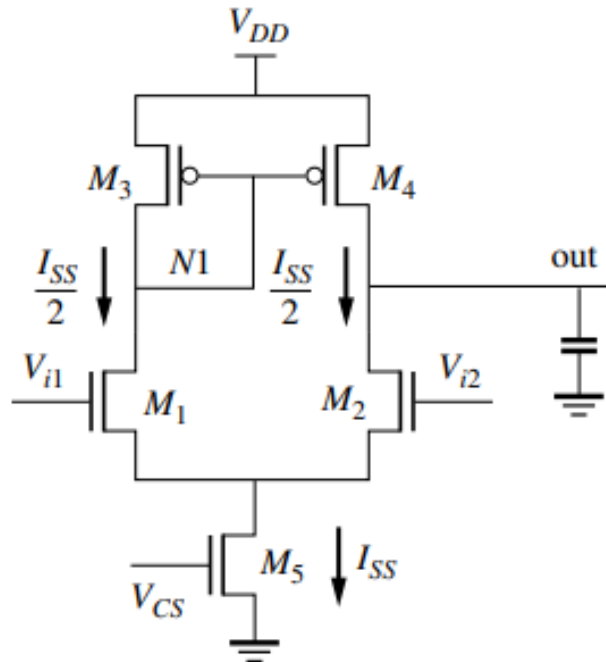- ❑ Option-1: A simple differential amplifier
 - ❑ Provides good common-mode rejection (common-mode noise)
 - ❑ Typical: 100 mV to 200 mV input voltage required
 - ❑ Static power consumption!



SENSE AMPLIFIER

- ❑ Option-1: A simple differential amplifier
 - ❑ Could also increase stages

