

# EE671: VLSI DESIGN

## SPRING 2024/25

LAXMEESHA SOMAPPA  
DEPARTMENT OF ELECTRICAL ENGINEERING  
IIT BOMBAY  
[laxmeesha@ee.iitb.ac.in](mailto:laxmeesha@ee.iitb.ac.in)



# LECTURE – 25

## LOGICAL EFFORT


# TAKEAWAYS FROM LAST CLASS

- ❑ An inverter has an intrinsic delay (due to parasitic) and external delay due to the load it is driving
- ❑ If  $C_1$  is input cap of INVX1,  $C_L$  is the load, inverter delay modelled as:

$$t_p = t_{p0} \left( 1 + \frac{C_L}{\gamma C_1} \right) \text{ and } t_{p0} = 0.69 R (\gamma C_1)$$

- ❑ Observations:

 - ❑ Total drive delay can be reduced by adding inverters




- ❑ Delay will reduce ONLY if successive inverter size increases gradually

# TAKEAWAYS FROM LAST CLASS
 
## Observations:


- Total drive delay can be reduced by adding inverters



- Delay will reduce ONLY if successive inverter size increases gradually

- Condition for minimum delay is:  $\frac{C_i}{C_{i-1}} = \frac{C_{i+1}}{C_i} = f$

 - Ratio of capacitance between successive stages increase by a factor  $f$ . i.e., inverter size must increase at every stage by a factor  $f$



# TAKEAWAYS FROM LAST CLASS

## □ Observations:

- Under the minimum delay condition, each stage offers the same delay of ( $f_{opt}$  is optimal  $f$ )

$$t_p = t_{p0} \left( 1 + \frac{f_{opt}}{\gamma} \right)$$

- The total delay of the chain of inverters will be  $[N \cdot t_{p0} (1 + \frac{f_{opt}}{\gamma})]$

- Since with each stage the strength increases by factor  $f_{opt}$ ,  $C_1 \cdot f_{opt}^N = C_L$

- If  $H = \frac{C_L}{C_1}$ ,  $f_{opt} = \sqrt[N]{H}$ , and  $N = \frac{\ln H}{\ln f_{opt}}$  relates  $N$ ,  $f_{opt}$ , and  $C_L$

- The total delay can be re-written as  $[N \cdot t_{p0} (1 + \frac{\sqrt[N]{H}}{\gamma})]$

- Under the no-parasitic (no self loading) condition,  $f_{opt} = e$  ( $\sim 2.7$ ) and  $N_{opt} = \ln H$

- Under practical conditions,  $f_{opt}$  and  $N_{opt}$  depends on  $\gamma$  (technology dependent)

- For  $\gamma = 1$ ,  $f_{opt} \approx 3.6$  (rounded off to 4)  $\rightarrow$  INVX1  $\rightarrow$  INV4x  $\rightarrow$  INV16X ... and find  $N_{opt}$



# GENERALIZING FOR ALL LOGIC GATES

- An inverter has an intrinsic delay (due to parasitic) and external delay due to the load it is driving.
- If  $C_1$  is input cap of INVX1,  $C_L$  is the load, inverter delay modelled as:

$$t_p = t_{p0} \left( 1 + \frac{C_L}{\gamma C_1} \right) \text{ and } t_{p0} = 0.69 R (\gamma C_1)$$

- The INVX1 delay  $t_{p0}$  is technology dependant (lower nodes  $\rightarrow$  lower  $t_{p0}$ )
- We represent normalized delay  $d$


$$d = \frac{t_p}{t_{p0}} = 1 + \frac{C_L}{\gamma C_1}$$

- First term represents the intrinsic (parasitic) delay and second term represents the effort to drive the load  $C_L$ . We used  $H$  for series of inverters. We will use  $h$  for a single inverter


$$d = p + h$$
 
# GENERALIZING FOR ALL LOGIC GATES


□ What about the parasitics for other gates?  $d = p + h$



 At node Y, total 3 widths  
and we took  $p = 1$



 At node Y, total 6 widths  
therefore,  $p = 2$



At node Y, total 6 widths  
therefore,  $p = 2$

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n

# GENERALIZING FOR ALL LOGIC GATES

- Recall, for INVX1, we defined delay  $d$

$$d = \frac{t_p}{t_{p0}} = 1 + \frac{C_L}{\gamma C_1}$$

$$d = p + h$$

- For gates, other than inverter, the input capacitance will be larger than  $C_1$
- To account for the increased input cap (which will increase the gate delay – since the input itself will be slowed due to increased input cap), we will add an additional term “ $g$ ”

$$d = p + gh$$


- $g = 1$  for INVX1





 
# GENERALIZING FOR ALL LOGIC GATES


□ What about the parasitics for other gates?  $d = p + gh$



 At node A, total 3 widths  
and we took  $g = 3/3 = 1$



 At node A, total 4 widths  
therefore,  $g = 4/3$



At node Y, total 5 widths  
therefore,  $g = 5/3$

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$

# GENERALIZING FOR ALL LOGIC GATES

□ Summary:  $d = p + gh$

## Parasitic delay for gates ( $p$ )

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n

## Logical effort for gates ( $g$ )

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	(n+2)/3
NOR		5/3	7/3	9/3	(2n+1)/3

□  $d$ : normalized delay

□  $p$ : parasitic delay

□  $h$ : electrical effort


□  $g$ : logical effort

□  $h = C_L/C_1$



# GENERALIZING FOR ALL LOGIC GATES

## Visualizing the gate delays

 

$$d = p + gh$$

□  **$d$** : normalized delay

□  **$p$** : parasitic delay

□  **$h$** : electrical effort


□  **$g$** : logical effort

□  **$h = C_L / C_1$**



# GENERALIZING FOR ALL LOGIC GATES

 - Example: A ring oscillator
- A typical use of ring oscillator in a digital chip:
  - Identify the process corner!



Logical Effort:  $g =$

Electrical Effort:  $h =$

Parasitic Delay:  $p =$


Stage Delay:  $d =$

Frequency:  $f_{\text{osc}} =$



# GENERALIZING FOR ALL LOGIC GATES

 - Example: A N-stage ring oscillator
- A typical use of ring oscillator in a digital chip:
  - Identify the process corner!



Logical Effort:  $g = 1$

Electrical Effort:  $h = 1$

Parasitic Delay:  $p = 1$


Stage Delay:  $d = 2$

Frequency:  $f_{\text{osc}} = 1/(2 \cdot N \cdot d) = 1/4N$



# GENERALIZING FOR ALL LOGIC GATES

 - Example: delay of a Fanout-4 (FO-4) inverter



Logical Effort:  $g =$

Electrical Effort:  $h =$


Parasitic Delay:  $p =$

Stage Delay:  $d =$



# GENERALIZING FOR ALL LOGIC GATES

 - Example: delay of a Fanout-4 (FO-4) inverter



Logical Effort:  $g = 1$

Electrical Effort:  $h = 4$

Parasitic Delay:  $p = 1$

Stage Delay:  $d = 5$



# GENERALIZING FOR MULTI GATE PATHS

- Now that we have looked at individual gates, what about a network of these gates?  $d = p + gh$        $d = p + f$
- Can we generalize a delay model for network of gates?
- We define **path** logical effort,  $G = \prod g_i$
- We define **path** effort,  $F = \prod f_i = \prod g_i \cdot h_i$ , and  $h_i = \frac{C_{out,i}}{C_{in,i}}$
- We define path electrical effort,  $H = \frac{C_{L,path}}{C_{in,path}}$
- Are we missing anything else?
  - To answer this, let's pose a question: can we write  $F = G \cdot H$  ?





 
# GENERALIZING FOR MULTI GATE PATHS

□ Consider the example:

$G =$   
 $H =$   
 $GH =$   
 $h_1 =$   
 $h_2 =$   
 $F = GH?$



$G =$   
 $H =$   
 $GH =$   
 $h_1 =$   
 $h_2 =$   
 $F =$

$$\square G = \prod g_i$$

$$\square H = \frac{C_{L,path}}{C_{in,path}}$$

$$\square F = \prod g_i \cdot h_i$$


$$\square h = C_L / C_1$$


 
# GENERALIZIZING FOR MULTI GATE PATHS

□ Consider the example:

$G =$   
 $H =$   
 $GH =$   
 $h_1 =$   
 $h_2 =$   
 $F = GH?$



$G = 1$   
 $H = 90 / 5 = 18$   
 $GH = 18$   
 $h_1 = (15 + 15) / 5 = 6$   
 $h_2 = 90 / 15 = 6$   
 $F = g_1 g_2 h_1 h_2 = 36 = 2GH$

□  $G = \prod g_i$   
 □  $H = \frac{C_{L,path}}{C_{in,path}}$   
 □  $F = \prod g_i \cdot h_i$

□  $h = C_L / C_1$


□ F is not the same as GH!! (because of the branching in the circuit)


 
# GENERALIZIZING FOR MULTI GATE PATHS

□ Consider the example:

$G =$   
 $H =$   
 $GH =$   
 $h_1 =$   
 $h_2 =$   
 $F = GH?$



$G =$   
 $H =$   
 $GH =$   
 $h_1 =$   
 $h_2 =$   
 $F =$

$$\square G = \prod g_i$$

$$\square H = \frac{C_{L,path}}{C_{in,path}}$$

$$\square F = \prod g_i \cdot h_i$$

$$\square h = C_L / C_1$$

□ F is not the same as GH!! (because of the branching in the circuit)



# GENERALIZING FOR MULTI GATE PATHS

- ❑ Need to introduce a branching effort  $\mathbf{B}$ 
  - ❑ This will account for branching between stages in a path
- ❑ We define  $\mathbf{b} = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$
- ❑ We define **path** branching effort  $\mathbf{B} = \prod \mathbf{b}_i$
- ❑ **path** logical effort,  $\mathbf{G} = \prod \mathbf{g}_i$
- ❑  $\mathbf{B} \cdot \mathbf{H} = \prod \mathbf{b}_i \mathbf{h}_i$
- ❑ **path** effort,  $\mathbf{F} = \mathbf{G} \cdot \mathbf{B} \cdot \mathbf{H}$
- ❑ The problem we are trying to tackle:
  - ❑ Given a network of logic gates, driving a load, what is the optimal sizing and number of stages to implement the logic  $\rightarrow$  for least delay



# GENERALIZING FOR MULTI GATE PATHS

- Recall that the total normalized delay has two components:
  - Parasitic delay and effort delay

$$d = p + gbh = p + f$$

- **Path** effort delay,  $D_F = \sum f_i$
- **Path** parasitic delay,  $P = \sum p_i$
- Total **path** delay,  $D = P + D_F$
- Delay is the smallest when each stage (each gate in this case) offers the same delay  $\rightarrow$  that is each stage effort increases by factor  $f_{opt}$   $\rightarrow$  this was our takeaway from inverter chain
- $f_{opt} = F^{\frac{1}{N}}$  and  $F = G \cdot B \cdot H$
- For an inverter chain,  $G = 1$  and  $B = 1$ ,  $f_{opt} = H^{\frac{1}{N}} \rightarrow$  we obtained this in the inverter chain case!



# GENERALIZING FOR MULTI GATE PATHS

- Recall that the total normalized delay has two components:
  - Parasitic delay and effort delay


$$d = p + gbh = p + f$$

- **Path** effort delay,  $D_F = \sum f_i$
- **Path** parasitic delay,  $P = \sum p_i$
- Total **path** delay,  $D = P + D_F$
- Delay is the smallest when each stage (each gate in this case) offers the same delay  $\rightarrow$  that is each stage effort increases by factor  $f_{opt} \rightarrow$  this was our takeaway from inverter chain
- $f_{opt} = F^{\frac{1}{N}}$  and  $F = G \cdot B \cdot H$
- Total **path** delay,  $D = P + N F^{\frac{1}{N}}$



# GENERALIZIZING FOR MULTI GATE PATHS

 - Example: find gate sizes for minimum delay



- Logical effort,  $G =$
- Electrical effort,  $H =$
- Branching effort,  $B =$
- Path effort,  $F = GBH =$
- Optimal stage effort,  $f_{opt} =$
- Parasitic delay =
- Total Delay =


- $f_{opt} = F^{\frac{1}{N}}$  and  $F = G \cdot B \cdot H$

- Total **path** delay,  $D = P + N F^{\frac{1}{N}}$



# GENERALIZING FOR MULTI GATE PATHS

 - Example: find gate sizes for minimum delay



- Logical effort,  $G = (4/3) * (5/3) * (5/3) = 100/9$
  - Electrical effort,  $H = 45/8$
  - Branching effort,  $B = 3 * 2 = 6$
  - Path effort,  $F = GBH = 125$
  - Optimal stage effort,  $f_{opt} = \sqrt[3]{F} = 5$
  - Parasitic delay =  $2 + 3 + 2 = 7$
  - Total Delay =  $7 + (3*5) = 22$
- $f_{opt} = F^{\frac{1}{N}}$  and  $F = G \cdot B \cdot H$
  - Total **path** delay,  $D = P + N F^{\frac{1}{N}}$






- 
- The diagram illustrates a logic circuit with a highlighted signal path from input A to output B. The path starts at input A, which is connected to an 8-input AND gate. The output of this gate is connected to a 3-input AND gate labeled 'x'. The output of the 'x' gate is then connected to a 2-input OR gate labeled 'y'. The output of the OR gate is connected to a 45V source. The highlighted path shows the signal traveling from A through the 8-input AND gate, then through the 'x' gate, and finally through the 'y' gate to output B.

- 

# GENERALIZING FOR MULTI GATE PATHS

 - Example: find gate sizes for minimum delay



- $y = (5/3) * 45/5 = 15$
- $x = (5/3) * (15 * 2)/5 = 10$
- To verify for the first gate,  $= (4/3) * (10 * 3)/5 = 8$
- Stage-1: 2-input NAND with input cap of 8  $\rightarrow$  NANDx2
- Stage-2: 3-input NAND with input cap of 10  $\rightarrow$  NANDx2
- Stage-3: 2-input NOR with input cap of 15  $\rightarrow$  NORx3



# GENERALIZING FOR MULTI GATE PATHS

## □ Summary:

Term	Stage	Path
number of stages	1	$N$
logical effort	$g$	$G = \prod g_i$
electrical effort	$h = \frac{C_{\text{out}}}{C_{\text{in}}}$	$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$
branching effort	$b = \frac{C_{\text{on-path}} + C_{\text{off-path}}}{C_{\text{on-path}}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
delay	$d = f + p$	$D = \sum d_i = D_F + P$
effort delay	$f$	$D_F = \sum f_i$
parasitic delay	$p$	$P = \sum p_i$



# GENERALIZING FOR MULTI GATE PATHS


□ Method/algorithm to size the path:

<b>Step-1</b>	<b>Compute the path effort</b>	<b><math>F = GBH</math></b>
<b>Step-2</b>	<b>If N is already chosen, proceed to step-3. If N is not given, the first estimate of N is calculated: (log base-4 since we saw that optimality is usually <math>f_{opt} = 3.6</math>)</b>	<b><math>N = \log_4 F</math></b>
<b>Step-3</b>	<b>Determine the optimal stage effort</b>	<b><math>f_{opt} = \sqrt[N]{F}</math></b>
<b>Step-4</b>	<b>Find individual gate caps (start from the output side)</b>	<b><math>C_{in} = \frac{g \text{ Cout}}{f_{opt}}</math></b>
<b>Step-5</b>	<b>Based on input cap, obtain the gate strength</b>	
<b>Step-6</b>	<b>Estimate optimal delay – go back to Step-3 and iterate “N”</b>	<b><math>D = P + NF^{\frac{1}{N}}</math></b>



# GENERALIZING FOR MULTI GATE PATHS

## Example-2:

 

Logical effort,  $G = 1 * (5/3) * (5/3) * 1 = 25/9$

Electrical effort,  $H = 5/3$

Branching effort,  $B = 1$

Path effort,  $F = GBH = 125/27$

Optimal stage effort,  $f_{opt} = \sqrt[4]{F} = 1.46$

$c = 1 * 5 / 1.46 = 3.42 \sim 3$  (INVx1)

$b = (5/3) * 3.42 / 1.46 = 3.90 \rightarrow (5/3) * 3 / 1.46 = 3.42 \sim 5$  (NORx1)

$a = (5/3) * 3.90 / 1.46 = 4.45 \rightarrow (5/3) * 5 / 1.46 = 5.7 \sim 5$  (NANDx1)

INVx1  $\rightarrow 1 * 4.45 / 1.46 = 3.0 \rightarrow 1 * 5 / 1.46 = 3.42 \sim 3$  (INVx1)

Parasitic delay:  $1 + 3 + 2 + 1 = 7$

Total delay =  $7 + 1 * (5/3) + (5/3) * (5/5) + (5/3) * (3/5) + 1 * (5/3) = 13$

Ideal delay =  $7 + 4 * 1.46 = 12.84$

$$f_{opt} = F^{\frac{1}{N}}$$

$$F = G \cdot B \cdot H$$



$$D = P + N F^{\frac{1}{N}}$$

$$C_{in} = g C_{out} / f_{opt}$$



 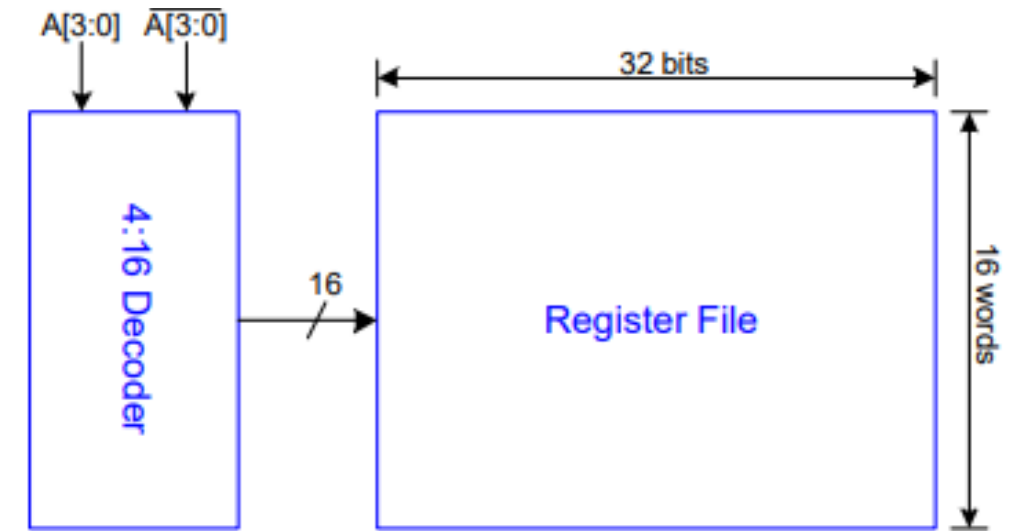
# GENERALIZING FOR MULTI GATE PATHS

- ❑ Example-3: An address decoder for memory
- ❑ Need to design a 4 to 16 decoder
- ❑ Assume address (A) and the complement are available
- ❑ Decoder specifications:
  - ❑ 16 word memory
  - ❑ Each word is 32 bits (4 bytes)
  - ❑ Each bit represents a load of 3-unit sized MOS
  - ❑ Each addr input can max drive 10-unit sized MOS
- ❑ Questions:
  - ❑ How many stages of gates required?
  - ❑ What will be the size of each gate?
  - ❑ What is the optimal decoder delay?



 
# GENERALIZING FOR MULTI GATE PATHS

- We don't know what gates to use yet → start with assuming  $G = 1$
- $H = (32 \cdot 3) / 10 = 96 / 10$
- $B = 8$  (since half of the inputs will be connected to  $A$  and other half to  $A$ -bar)
- $F = GBH = 768 / 10 = 76.8$
- $N = \log_4 F = 3.1$
- Start iteration with a 3-stage design



# GENERALIZING FOR MULTI GATE PATHS

 

- $G = 1 * 6/3 * 1 = 2$
- $B = 8, H = 9.6$
- $F = GBH = 153.6$
- $f_{opt} = \sqrt[3]{153.6} = 5.35$
- $\text{Delay} = (1 + 4 + 1) + (3 * 5.35) = 22.05$
- $z = 96 * 1/5.35 = 17.94 \sim 18$
- $y = 18 * 2/5.35 = 6.7$





# GENERALIZING FOR MULTI GATE PATHS

- To find the actual optima, you can write a script to iterate “N” and the associated logic (try the below table on pen and paper)

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

