

Lecture-7

* Several drawbacks in TTL/ECL logic:-



- * Static power consumption due to finite base-emitter current
- * Voltage swing @ the output is not rail-to-rail
- * Area consumed is higher compared to CMOS for the same logic implementation.

Static CMOS logic Gates:-


CMOS \rightarrow Complementary MOS: the implemented gate uses both NMOS & PMOS transistors

Static: unlike dynamic logic (which we will cover later in the course), in static CMOS, at any point in time, the gate output is connected to either V_{DD} or GND through a low resistance path.

  * A quick example for an inverter based on static & dynamic logic




* Revisit the static CMOS inverter.

 


* If we blindly saw the circuit from NMOS side, it looks like the output is complement of the input.

[i.e. If $A=1$, $Y=0$ since MOS is ON]

 so it looks like we can design any logic simply looking from the NMOS side

 * Consider the example below with 2 series NMOS gates.



* The output Y will be zero if both MOSFETs M1 & M2 are ON

i.e. If $A=1$ & $B=1$, $Y=0$


* This looks a lot like a NAND Gate!! $Y = \overline{A \cdot B}$

* i.e. we compute the logic from NMOS side (AND logic in this case) & invert the output Y, to obtain the complete logic

* However, we know that in static CMOS logic both NMOS & PMOS cannot be ON together, by definition

* However, we know that in static CMOS logic both NMOS & PMOS cannot be ON together, by definition

 \Rightarrow If the NMOS is in series, the corresponding PMOS must be in parallel.




* \therefore To design any logic in static CMOS:-


- Implement the logic on the NMOS side & complement the output Y.
- Add PMOS in connections opposite to NMOS [i.e if NMOS is in series, PMOS will be in parallel & vice versa]

Eg: Implement $Y = \overline{(A+B)C + D}$

 
\rightarrow First implement $(A+B)$ i.e NMOS in parallel



 
\rightarrow Next implement $(A+B) \cdot C$ i.e additional NMOS in series with



 
\rightarrow Finally implement $(A+B) \cdot C + D$ i.e an additional parallel NMOS with



\rightarrow Now add all PMOS transistors

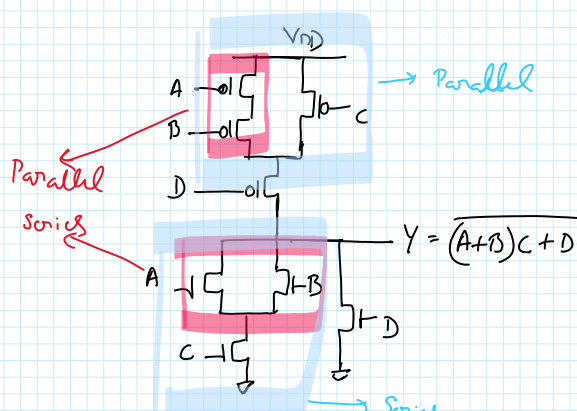


 STATIC CMOS
with "N" inputs
Need "2N" MOSFETS



Need 2N MOSFETs

 * Consider the inverter & its Voltage transfer curve (VTC)



$$\text{If } \frac{\mu_n}{\mu_p} = 2 \text{ \& } V_{TN} = |V_{TP}|$$


$$\text{For } t_r = t_f \quad \beta = 1$$

$$\Rightarrow \frac{W_p}{W_n} = \frac{2}{1}$$


i.e. NMOS Aspect ratio : $\frac{W_{min}}{L_{min}}$

PMOS Aspect ratio : $\frac{2W_{min}}{L_{min}}$

 * For quick abstraction, we take all MOS lengths as L_{min} & represent the circuit




VTC

 

* Now assume the PMOS strength (i.e. width of PMOS) increases from 2 to 2.5.


\therefore Intuitively, in-and-around V_n , both PMOS & NMOS are fighting for the off voltage

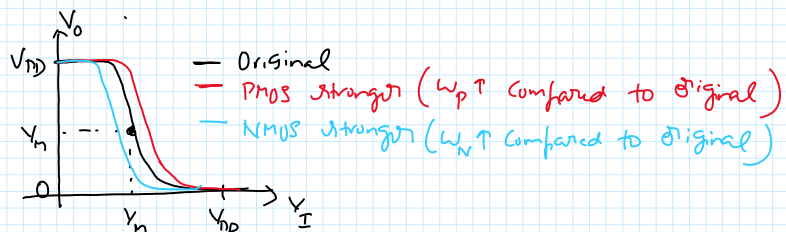However, since the PMOS strength has increased (and PMOS is connected to V_{DD}), the output tends to stay near V_{DD} for a longer time than before.




* We define logic gates with strength

For example an INVX1 \rightarrow

 

An INVX2 \rightarrow

 

i.e. strength of individual MOS increases ($W \uparrow$)



$\therefore t_r$ & t_f will reduce with higher strengths for the same cap load

$$\left[\therefore t_r = t_f \propto R_{on} \propto \frac{1}{W} \right]$$

$$A \rightarrow \begin{array}{c} \text{d} \\ \text{p} \\ \text{n} \\ \text{p} \\ \text{d} \end{array} \begin{array}{c} \text{h} \\ \text{h} \\ \text{h} \\ \text{h} \\ \text{h} \end{array} \begin{array}{c} \text{y} \\ \text{y} \\ \text{y} \\ \text{y} \\ \text{y} \end{array} \quad \left[\therefore t_r = t_f \propto R_{on} \propto \frac{1}{W} \right]$$

* A symmetric INVX1 will be taken as a reference (i.e. t_r & t_f of INVX1) to define the strength of other logic gates

  * Now consider an INVX1 and a NANDX1 side-by-side. Since both are X1 strength, the worst-case t_r and t_f of the NAND gate cannot exceed beyond that of INVX1!




* t_f : The inverter offers $R_{on,N}$ resistance

The NAND gate offers $(R_{on,N} + R_{on,N})$ resistance with the sizing shown


To get the same t_f as inverter, the NMOS ON resistance has to be halved
i.e. W has to be doubled ($R_{on} \propto 1/W$)

* For X1 strength NAND -

 

* t_r :- The inverter offers $R_{on,P}$ resistance

 Let's start with an assumption that the PMOS devices are sized exactly same as inverter



The NAND gate can offer two different effective resistance depending on input

(a) If $A=0, B=1$
or
 $A=1, B=0$ } at least ONE PMOS is ON and the effective resistance will be $R_{on,P}$


(b) If $A=0$ & $B=0 \rightarrow$ both PMOS is ON (and in parallel) and the effective resistance will be $R_{on,P}/2$

will be $R_{onp}/2$

* Notice that from t_r perspective, case (a) is the worst-case (highest delay) & case (b) is the best-case (smallest delay)


* We will design the gate for the worst-case scenario (i.e. if $A=0, B=1$ or $A=1, B=0$, the t_r will be same as that of $INV \times 1$)

NANDx1 \rightarrow

 


[Remember if μ_n/μ_p changes, sizing will change]

 * Similarly for a NOR gate, the sizing will be




work it out

 * Now, let's look at the VTC of the NANDx1



* Let's consider the condition $A=B$
The case is similar to an inverter!!
 
$$X \text{ NAND } Y \equiv X \rightarrow Y = \overline{X}$$




* Now consider the case $A=1$ & B takes input

$$B \text{ NAND } 1 \equiv B \rightarrow Y = \overline{B}$$

* Again, the VTC must be similar to an inverter!!!


However, $A=1$ means, one of the PMOS is always off

 \therefore Effectively, the PMOS strength is reduced by half & therefore VTC curve must shift left.



* The same argument holds good if $B=1$ and A is the input.

 * However, remember, in bulk CMOS technology, all NMOS bulks are grounded.



For a MOS, $V_{TH} = V_{TH0} + \gamma \left[\sqrt{|2\phi_F| + \underbrace{V_{SB}}_{\text{Source to bulk Voltage}}} - \sqrt{2\phi_F} \right]$

\therefore M2 will have a higher V_{TH} compared to M1 and hence the VTC curve will not overlap for the cases


(i) $A=1$ & B is input

(ii) $B=1$ & A is input

_____ x _____



* As the input count of the gate (Fan-in) increases, static CMOS logic will have an impact


Consider the example h input NANDX1 gate

 

* All NMOS's will have area h times that of the NMOS in the inverter.
* The capacitance (diffusion caps in Lecture-6) between drain-to-bulk & source-to-bulk will increase

+ Effectively

  

 


* Elmore Delay (quick first order way to calculate delay between 2 nodes)

- ↳ If network has one input node
- ↳ Network does not have resistive loops
- ↳ Network has all capacitors w.r.t ground



Then delay from input node V_s to node "L" is (For a N/w with "N" nodes)

$$\tau_L = \sum_{k=1}^N R_{ik} C_k$$

 

* τ from V_s to V_3 is $R_1 C_1$

* τ from V_s to V_2 is $R_1 C_1 + (R_1 + R_2) C_2$

* τ from V_s to V_1 is $R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3$

* τ from V_s to V_0 is $R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + (R_1 + R_2 + R_3 + R_4) C_4$

* In our case $R_1 = R_2 = R_3 = R_4 = R_{on}/h$ [R_{on} is resistance of NMOS in INVX1]

$$\therefore \tau = \frac{R_{on}}{h} [C_1 + 2C_2 + 3C_3 + 4C_4]$$

* C_4 is the load and in the absence of C_1, C_2, C_3 , $\tau \rightarrow \frac{R_{on}}{h} [4 \times C_4] \rightarrow$ same as INVX1

- An additional delay is contributed.

⇒ In static CMOS logic

↳ As Fan-In ↑

↳ W of either PMOS or NMOS ↑ (NOR vs NAND)

↳ Parasitic Cap ↑

↳ Delay ↑

— x —