

# EE671: VLSI DESIGN

## SPRING 2024/25

LAXMEESHA SOMAPPA  
DEPARTMENT OF ELECTRICAL ENGINEERING  
IIT BOMBAY  
[laxmeesha@ee.iitb.ac.in](mailto:laxmeesha@ee.iitb.ac.in)




# LECTURE – 19

## DIGITAL SYNTHESIS

# WHAT ARE WE LEARNING IN THIS COURSE?

EE709: TESTING  
& VERIFICATION

 

EE739: PROCESSOR DESIGN  
EE789: ALGORITHMIC DESIGN OF  
DIGITAL SYSTEMS

EE721: HARDWARE DESCRIPTION  
LANGUAGES


**EE671 – THIS COURSE!**

**PRE-MIDSEM: LIBRARY DEVELOPMENT**

**POST-MIDSEM: RTL TO FAB**

COURSE WILL NOT COVER FPGA DESIGN – THIS WILL  
BE TAKEN UP IN EE705 (VLSI DESIGN LAB)

# RTL TO GDS AND SYNTHESIS

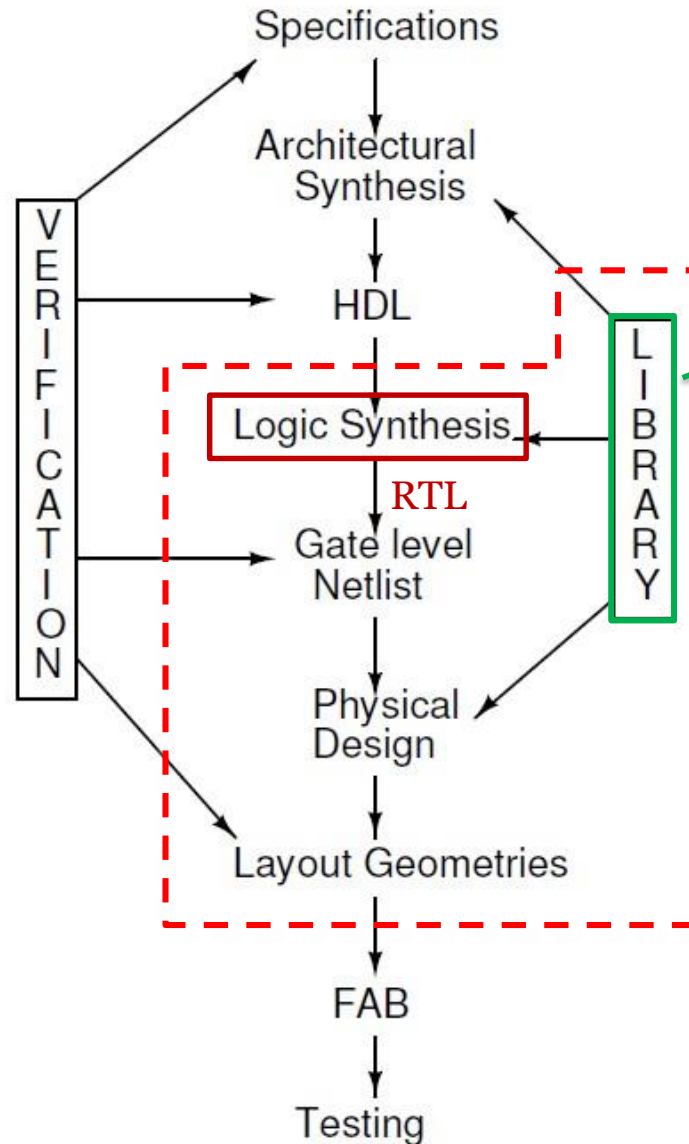

**STANDARD CELL LIBRARY:**  
.V, .LEF, .LIB, .SP, .GDSII/.MAG

## LOGIC SYNTHESIS:

- ❑ INPUT: HDL (VERILOG – BEHAVIORAL/STRUCTURAL CODE)
- ❑ OUTPUT: RTL (REGISTER TRANSFER LEVEL VERILOG)
- ❑ RTL: COULD BE OR COULD NOT BE MAPPED TO A TECHNOLOGY (STD. CELL LIBRARY)


# LOGIC SYNTHESIS

---

- ❑ Popular logic synthesis tools:
  - ❑ Synopsys: Design Compiler
  - ❑ Cadence: Genus
  - ❑ Open Source: Yosys (will be used in this course)
  
- ❑ Synthesis: process of converting a gate level netlist (RTL) from a model of a circuit described in HDL
  
- ❑ Do we always need synthesizable codes?
  - ❑ Only if we need a hardware out of the code
  - ❑ Example: a testbench need not be synthesizable since it is not going to be translated to hardware!



# LOGIC SYNTHESIS: COMBINATIONAL LOGIC

 


```
// Using a reg
// -----
wire a,b;
reg c;
always @ (a or b)
    c = a & b;
```

```
// Using a wire
// -----
wire a,b,c;
assign c = a & b;
```

```
// using a built in primitive (with instance name)
// -----
reg a,b;
wire c;
and u1 (c,a,b); // output is always first in the list
```

# LOGIC SYNTHESIS: COMBINATIONAL LOGIC

 


```
// 1. using an always
always@(a or b or sel)
    if (sel == 1'b1)
        c = a;
    else
        c = b;
```

```
// 2. using the ternary operator
wire c = sel ? a : b;
```

```
// 3. using the case statement
always @ (a or b or sel)
    case (sel)
        1'b1: c = a;
        1'b0: c = b;
    endcase
```

# LOGIC SYNTHESIS: COMBINATIONAL LOGIC

 

```
always @ (s1 or a or b or c)
    case (sel)
        2'b11:  d = a;
        2'b10:  d = b;
        default: d = c;
    endcase
```

```
always @ (s1 or a or b or c)
    if (sel == 2'b11)
        d = a;
    else if (sel == 2'b10)
        d = b;
    else
        d = c;
```

❑ Question: What is the implemented logic?






# LOGIC SYNTHESIS: BUS LOGIC

```
wire [2:0] e = {a[1],b[3:2]};
```

```
reg [2:0] e;  
always @ (a or b)  
    e = {a[1],b[3:2]};
```

**$e = \{a[1], b[3:2]\}$**

 


□ Bus concatenation


 
# LOGIC SYNTHESIS: BUS LOGIC

```
wire [3:0] d = ({4{enable}} & c);
```


```
reg [3:0] d;  
always @ (c or enable)  
    d = c & {4{enable}};
```



□ Bus Enabling
 
# LOGIC SYNTHESIS: BUS LOGIC


```
wire [1:0] a;  
wire [3:0] b;  
assign b = {2{a}};
```



□ Bus replication



# LOGIC SYNTHESIS: BUS LOGIC

 


```
wire d;  
assign d = (a == c);
```

```
reg d;  
always @ (a or c)  
    d = (a == c);
```

□ Comparator



# LOGIC SYNTHESIS:

 

```
wire d;  
assign d = (a == c);
```

```
reg d;  
always @ (a or c)  
    d = (a == c);
```


❑ Comparator



# LOGIC SYNTHESIS: SEQUENTIAL LOGIC


```
always @ (posedge clock)
```

```
q <= d;
```

 

```
always @ (negedge clock)
```

```
q <= d;
```

 

□ Use non-blocking assignments ( <= )



# LOGIC SYNTHESIS: SEQUENTIAL LOGIC


```
always @ (posedge clock)
```

```
  if (reset)
```

```
    q <= 1'b0;
```

```
  else
```

```
    q <= d;
```

 


```
always @ (posedge clock or posedge reset)
```

```
  if (reset)
```

```
    q <= 1'b0;
```


```
  else
```

```
    q <= d;
```

 

 
# LOGIC SYNTHESIS: SEQUENTIAL LOGIC

```
always @ (posedge clock)
  if (enable)
    q <= d;
```



□ Data enabled FF
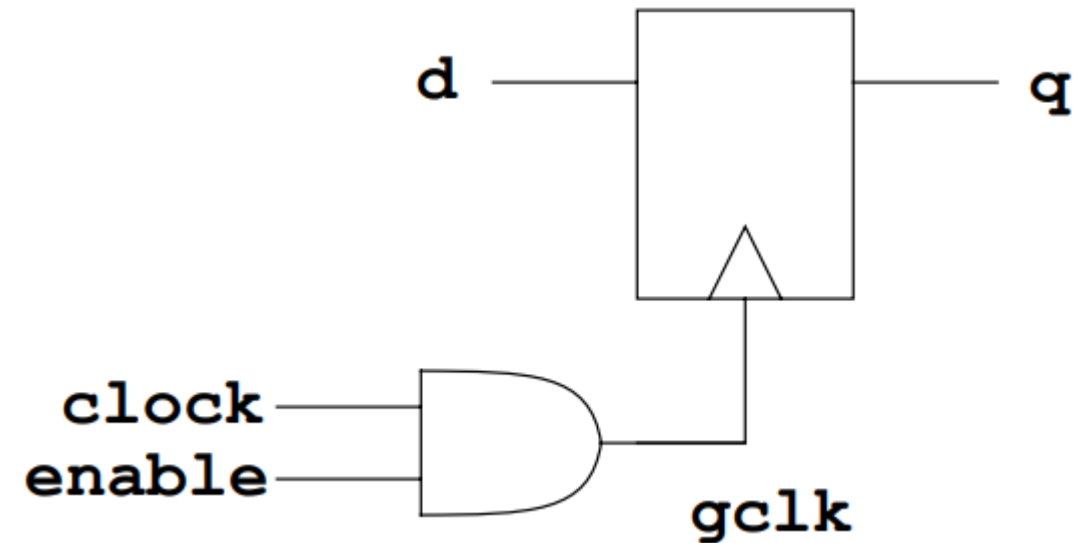
```
wire gclk = (clock && enable);
always @ (posedge gclk)
  q <= d;
```




□ Clock gated FF (EN must not have any glitches!)




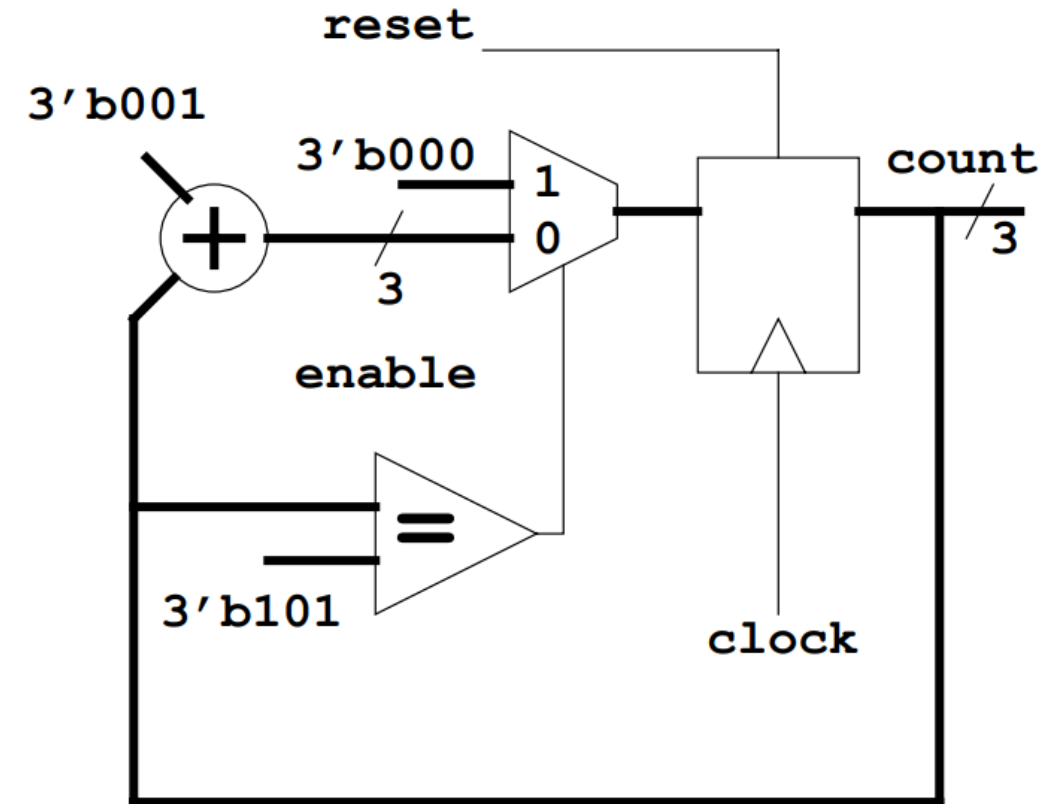
# LOGIC SYNTHESIS: SEQUENTIAL LOGIC

```
// 3 bit asynchronously resettable
// partial range counter
always @ (posedge clock or posedge reset)
    if (reset)
        count <= 3'b0;
    else
        if (count == 3'b101)
            count <= 3'b0;
        else
            count <= count + 3'b001;
```




# LOGIC SYNTHESIS: SEQUENTIAL LOGIC

```
module enabled_shift_reg (clock,enable,data_in,data_out);
input clock;
input enable;
input [3:0] data_in;
output [3:0] data_out;
```

```
reg [3:0] data_out;
reg [3:0] shift_reg_1;
reg [3:0] shift_reg_2;
reg [3:0] shift_reg_2;
```

```
always @ (posedge clock)
    if (enable)
        begin
            shift_reg_1 <= data_in;
            shift_reg_2 <= shift_reg_1;
            shift_reg_3 <= shift_reg_2;
            data_out <= shift_reg_3;
        end
```

```
endmodule
```

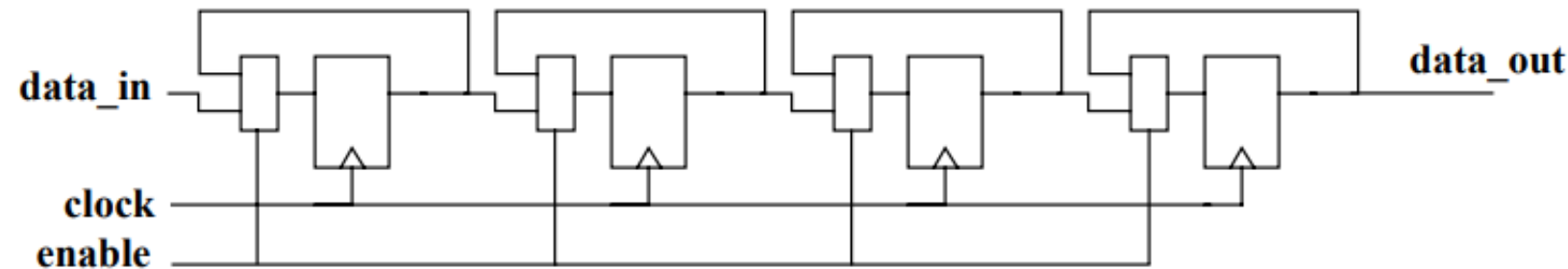

□ Bus and FFs are 4-bit wide



# LOGIC SYNTHESIS: CODING GUIDELINES

- Use non-blocking assignments ( $\leq$ ) in clocked procedures. Don't use blocking assignments ( $=$ ).

```
always @ (posedge clock)
    q <= d;
```

- Use blocking assignments ( $=$ ) in combinational procedures:

```
always @ (a or b or s1)
    if (s1)
        d = a;
    else
        d = b;
```

- Make sure that the event lists are complete

```
always @ (a or b) // this event list is missing signal s1
    if (s1)
        d = a;
    else
        d = b;
```



# LOGIC SYNTHESIS: CODING GUIDELINES

- Use named port mapping when instantiating.

```
state_machine u1 (  
    .sm_in      (in1),  
    .sm_clock   (clk),  
    .reset      (reset),  
    .sm_out     (data_mux)  
);
```

- Take care of indentation. Develop your own indentation guidelines and stick to them. Make sure others can read them. It helps readability and debugging greatly if it is done properly.
- Comment code properly. The theory about good commenting is that you should be able to remove all functional code and the comments remaining should almost document the block you are designing.
- Don't make the code any more complicated than it needs to be. Your priorities should be correctness, then readability and finally code efficiency.

