
 


Lecture-10

* Recall that NMOS passes strong '0' and weak '1' (vice versa for PMOS)

 
* Consider a combination of NMOS and PMOS:-



* This is termed as a "Transmission Gate" (TG) and a TG passes a strong 1 & strong 0.


* A TG acts as a "switch" (without inversion unlike an inverter).

 ↳ It is easy to implement a 2to1 MUX using 2 switches (TG):-





* This is not a static gate since by definition, the output node 'Y' is not tied to V_{DD} or V_{SS} through a low resistance path (i.e. ON PMOS or ON NMOS).

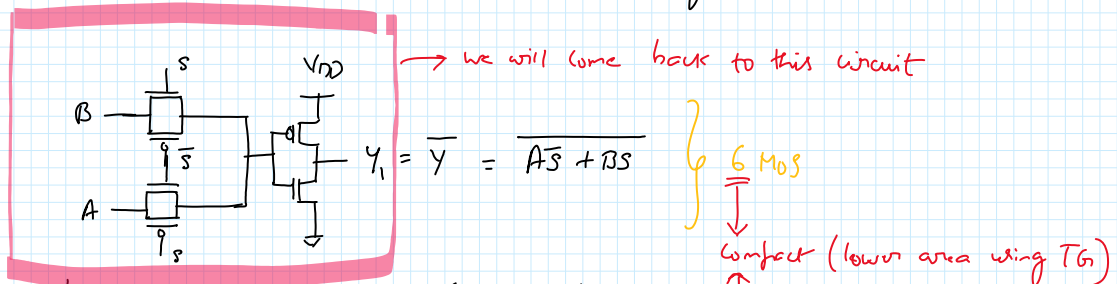* To convert this into a static gate, we can simply add an inverter at the output.






 * A similar logic using our earlier CMOS implementation -




 

   * Consider two inverters I_1 & I_2 & their VTC



 
* We make a "back-to-back" inverter connection -




i.e. $V_{i2} = V_{o1}$ and $V_{i1} = V_{o2}$

* To get the operating point of this new circuit, we need to find intersection on VTC curves.


 
* First let's transform the VTC curve of I_2 (swap axes)



transform

 

  
Combine the two to find the operating points




* only three possible operating points

- $V_{o1} = V_{DD}, V_{o2} = 0$
- $V_{o1} = 0, V_{o2} = V_{DD}$
- $V_{o1} = V_{o2} = V_M$

 * Now consider the following - at Power ON, $V_{i1} = V_{o1} = V_{i2} = V_{o2} = V_M$



 

Now there is a small perturbation @ V_{i1} , i.e. $V_{i1} = V_M - \delta$ (δ is a very very small voltage)

Follow the following -

a) $V_{i1} = V_M - \delta$ is applied

↳ $V_{o1} = V_1$ (for this new input) [Yellow traces]

b) V_1 will be the new input to I_2 ($V_{i2} = V_1$)

↳ $V_{o2} = V_2$ (for this new input) [Blue traces]

c) V_2 will be the new input to I_1 ($V_{i1} = V_2$)

↳ $V_{o1} = V_{DD}$ (for this new input) [Green traces]

d) V_{DD} will be the new input to I_2 ($V_{i2} = V_{DD}$)

↳ $V_{o2} = 0$ (for this new input) [Purple traces]

⇒ Given that the back to back inverter happens to be biased at V_M ,

↳ A small $-\delta$ change @ V_{i1} drives V_{i1} to 0 and V_{i2} node to V_{DD}

↳ Similarly small $+\delta$ change @ V_{i1} will drive V_{i1} to V_{DD} and V_{i2} node to 0

* In reality a small circuit noise will act like this δ voltage and take the output nodes to V_{DD} or 0

∴ In reality (practical scenarios), the back to back inverter has only 2 states


→ either V_{DD} or 0

* Once the output nodes have reached V_{DD} or 0, any small δ change will not have any impact since in this region (in the VTC), the slope is always < 1 and no noise is amplified (recall our discussion on NM, slope = ± 1 points).

∴ A back-to-back inverter can act like a 1-bit memory


↳ To change the data to be stored in this 1-bit memory cell we need to

(a) open the back to back connection

 


(b) Apply new data to be stored




 

 (c) Close the connection, to preserve the state



 * 1-bit register (D FF) has following timing characteristic



T_s Setup time : Time for which D must be stable before the clock edge


T_H Hold time : Time for which D must be held after the clock edge.

T_{cq} : CLK-to-Q delay : Delay from clock edge to output changing state.

* Similar definitions for both +ve & -ve edge triggered DFF

Latch:

 
* +ve Latch (G is gate input) : Latch is transparent (o/p = i/p) when G is high.




* -ve latch is transparent when G is low.

* Now follow the sequence of implementation :-

a) Latches using MUX:-

 


b) Flip Flop using Latches:-

 

- * CLK = 0 \rightarrow Latch-1 : transparent ($Y_{int} = D$)
 \rightarrow Latch-2 : Holds prev state ($Q = D^-$)
 - * CLK = 1 \rightarrow Latch-1 : Holds current state ($Y_{int} = D$)
 \rightarrow Latch-2 : transparent ($Q = D$)
- clock edge bit there two


Flip Flop at the gate level (evolution) :-

1) Latch using MUX :-

 

* $G=0$, $Y = \bar{D}$ BUT WE NEED $Y = D$

 * $G=1$, we need to preserve prev. state (i.e. need 1-bit memory)
 \rightarrow we already discussed, 1-bit memory \rightarrow 2 back to back inverters.




3) +ve edge triggered FF (-ve Latch followed by +ve Latch)



Master -ve Latch

Slave +ve Latch.



 

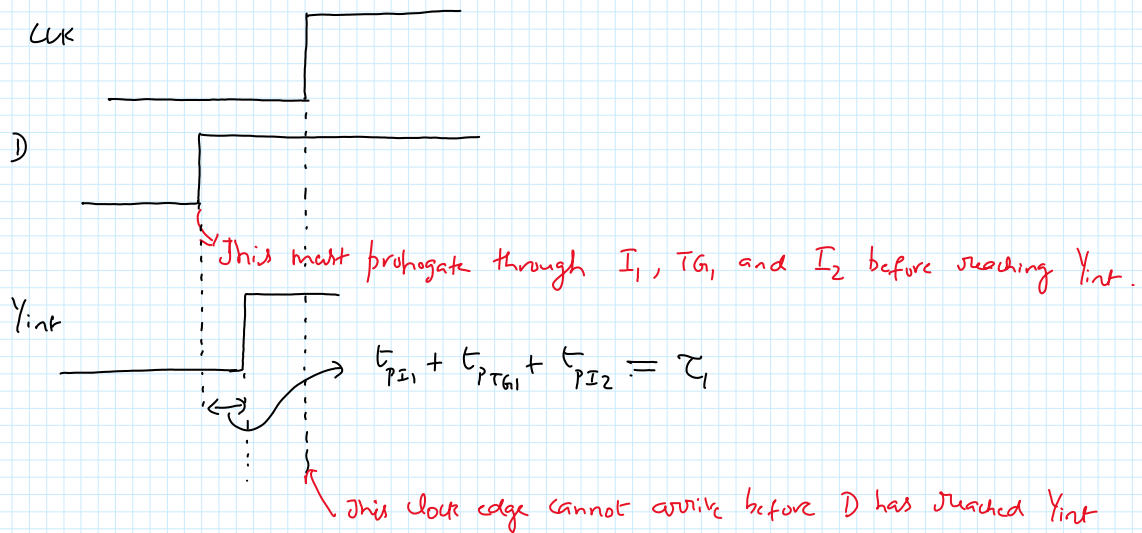 
* Now consider finite propagation delay of inverters and transmission gates.



\Rightarrow D must arrive atleast τ_1 before the clock edge!!! (Setup-time??)

* Note that before making CLK high TG_{2L} must see same logic states at either sides!!

 i.e the D input must propagate through I_1 , TG_{1L} , I_2 and I_3 BEFORE the CLK is made high!!




$$\therefore T_s = t_{PI1} + t_{PTG1} + t_{PI2} + t_{PI3}$$

SETUP TIME OF DFF

* Notice that when $CLK=0$, T_{G1} is OFF and the D -input is already latched. Hence no additional time is required to hold the data 'D' after CLK going high.

$$\Rightarrow T_H = 0$$

 

* Consider the CLK going from low to high. $\Rightarrow Y_{int}$ will reach Q as latch-2 is transparent
 \Rightarrow From the CLK edge, Y_{int} has to travel through I_4 , T_{G3} and I_5 to reach Q (T_{cq})

* However note that I_3 and I_4 are similar and

(a) the delay associated for Y_{int} to reach I_3 output = delay associated for Y_{int} to reach I_4 output.

(b) Since the delay of I_3 is already in the setup time, the T_{cq} should not include I_4 delay (i.e. data has already reached output of I_4 before clock edge because of setup time restriction)

$$\Rightarrow T_{cq} = t_{PTG3} + t_{PI5}$$